
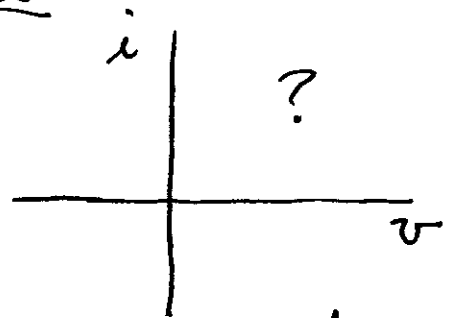


ECE 211 - Fall 2000


Exercise set E2 - selected solutions

E 2.8

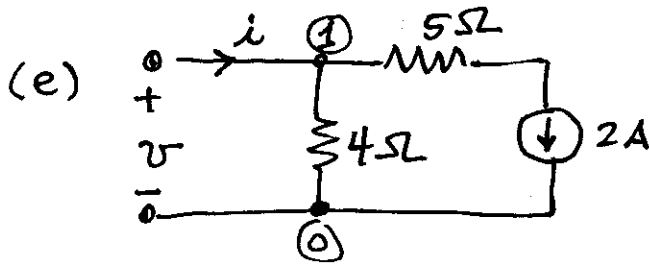

Since this is a linear circuit (no non-linear elements) we know that the $i-v$ graph will be a straight line. If we can locate 2 points on that line, we can construct the $i-v$ graph.

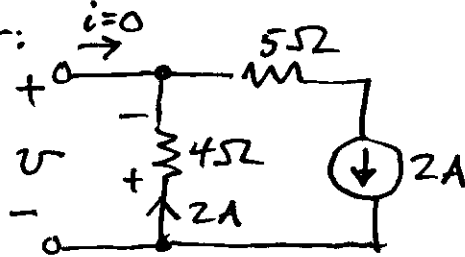
For the first point, suppose that $i=0$ (no current flowing into node ①). Then the 2A constant current source causes a 2A current to flow up through the 4Ω resistor:



By Ohm's Law, $v = IR = (-2)(4) = -8 \text{ V}$

so our first point on the line is $(i=0, v=-8)$

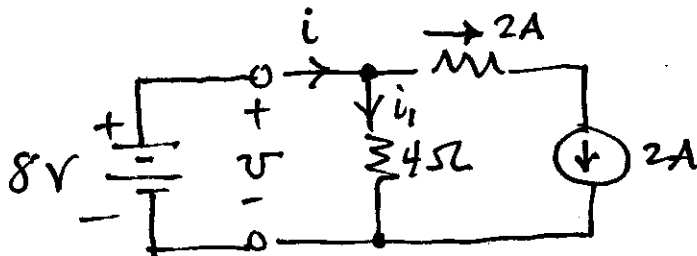
To get another point, imagine that we apply some voltage, e.g. $v = +8 \text{ Volts}$ to the circuit:



By Ohm's law,
 $v = +8 = i_1 \times 4 \Rightarrow i_1 = 2 \text{ A}$

By KCL,
 $i = i_1 + 2 = 2 + 2 = 4 \text{ A}$

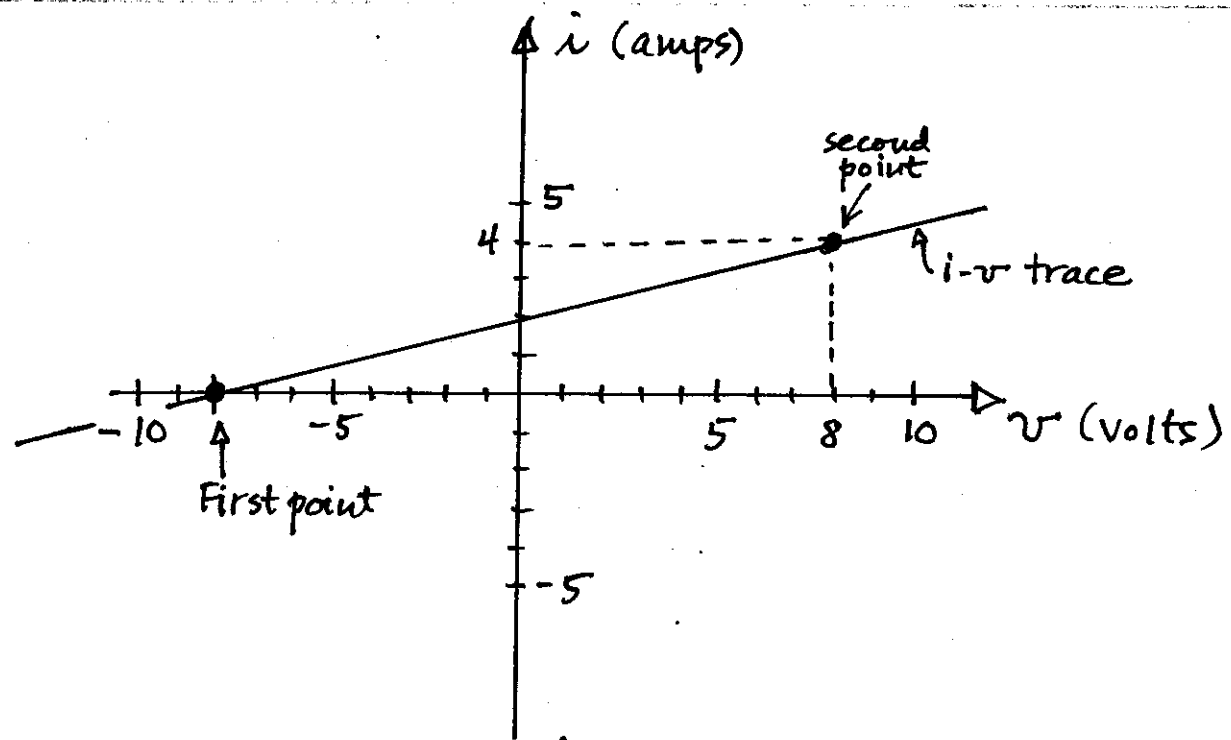Thus the second point on the line is $(i=4, v=+8)$



Note that when $v=0$, $i=2\text{ A}$. This means that $v=0$ indicates a short circuit across the input, so all the 2 A from the constant current source flows through the input.