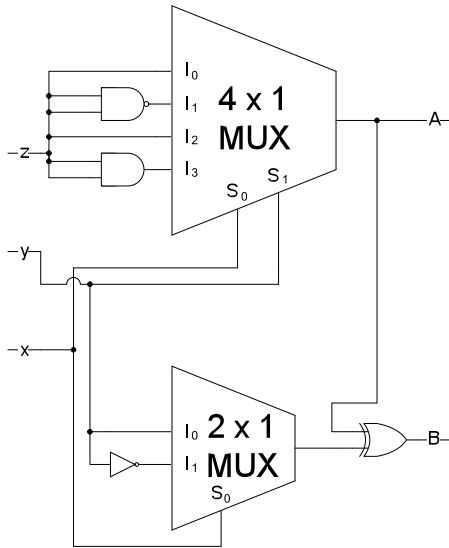


Question 2 (15 points):

Analyze the following combinational logic circuit.

- a) Determine the outputs functions A and B as sums of minterms. You may use any process to determine the result, but show your work. (10 points)



- b) Implement the same circuit using a decoder circuit and external logic gates. Show the block-level diagram of your design (5 points)

Question 3 (15 points):

Design a combinational circuit with three binary inputs: H, S, I and three binary outputs: x, y, z . Each input represents an item that a person may order at a fast food place:

- H stands for hot dog, cost = \$3
- S stands for soda, cost = \$1
- I stands for ice cream, cost = \$2

Each input can only be 0 or 1, which means that a customer can order each item only once (or none at all, for $H=0, S=0, I=0$).

The outputs x, y, z represent a 3-bit encoding $(xyz)_2$ of the total cost of the order. For example, for $H=1, S=0, I=0$ (which evaluates to \$3), the output should be $x=0, y=1, z=1$.

- a) Show the truth table for this combinational circuit. (10 points)

- b) Determine the minimized functions x, y, z in a sum of products form. (5 points)

Question 4 (10 points):

Answer the following questions regarding latches.

- a) Draw the circuit of a NAND-based SR latch.
Fill in the function table below that shows the value of the outputs for different combinations of inputs S and R. (5 points)

R	S	Q	Q'

- b) Draw the circuit of a D-latch using the SR latch designed in problem (a) (5 points).
(Hint: provide the D and EN inputs, properly wiring them to the S, R inputs)

EN	D	Q