

The background features a series of overlapping, wavy lines in shades of blue and green, creating a sense of motion and depth. Interspersed among these lines are several semi-transparent circles of varying sizes, some in blue and some in green, adding to the abstract, digital aesthetic.

# E-Space

Spencer Pietryka, Steve Bevacqua, Jonathan Scharf

# Revised System Requirements

- Changed minimum output power from 3.3W to 2.5W based on minimum USB charging requirements
- Changed final range to 10 cm

Input Specifications	120 VAC at 60Hz
Frequency	6.78 MHz
Distance/Range	10 cm
Minimum Output Power	2.5W
Minimum Wireless Transfer Efficiency	≥40%
Minimum Total System Efficiency	≥10%
Maximum Receiver Size	4.54 in X 2.31 in

# Team Responsibilities


	December	January	February	March	April
Jon Scharf	Coil Redesign				
		Impedance Matching			
				PCB Design/Case Design	
Steve Bevacqua	Increase Power				
	Oscillator Design/Integration				
			Rectifier, Voltage Regulation		
Spencer Pietryka	SWR Measure, Control Algorithms				
				Repeater	
		Control Circuitry			

Gantt Chart from MDR

# Projected Block Diagram





## Transmitter

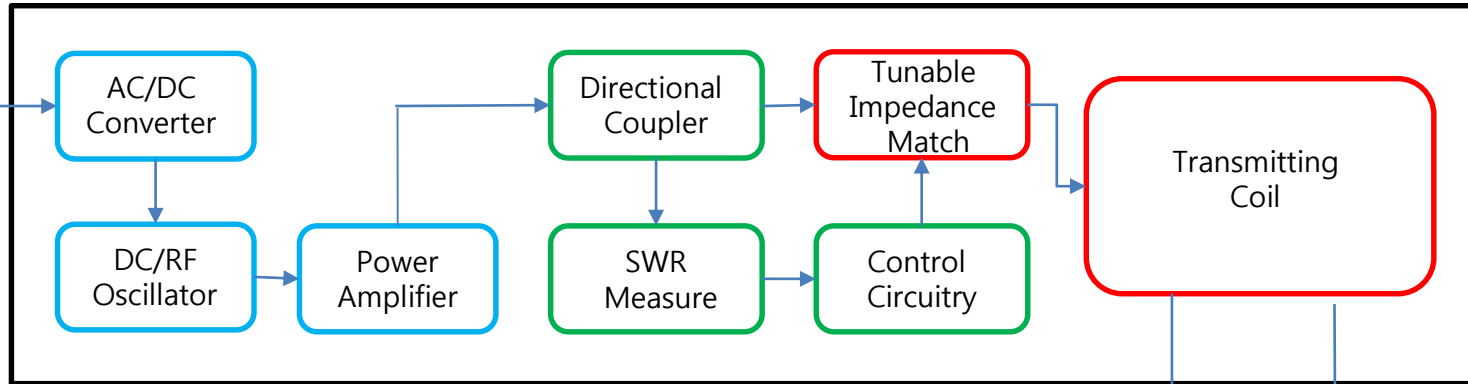

Gap/Distance: 0.25m



6.78 MHz  
Resonant Signal

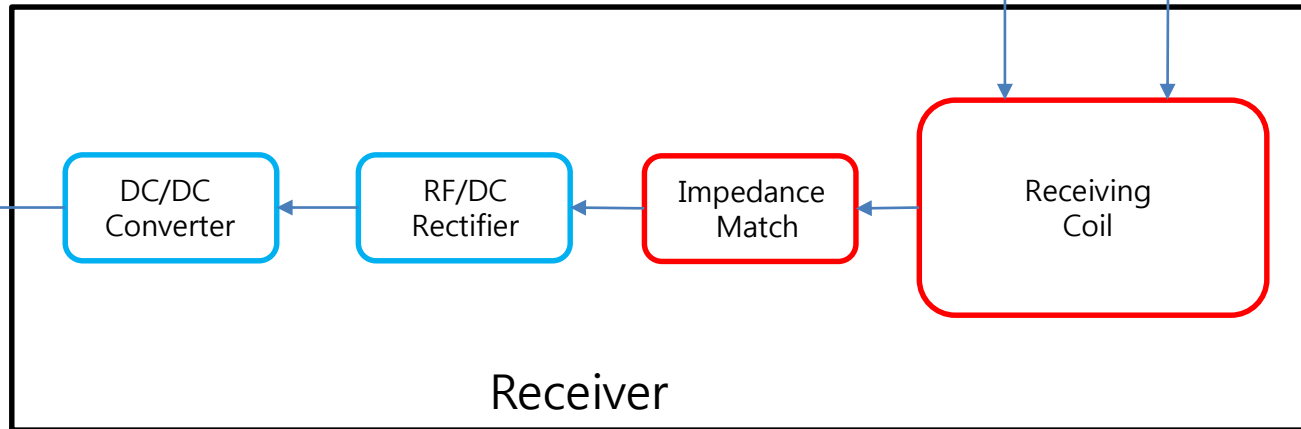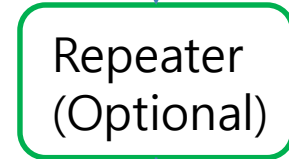

## Receiver

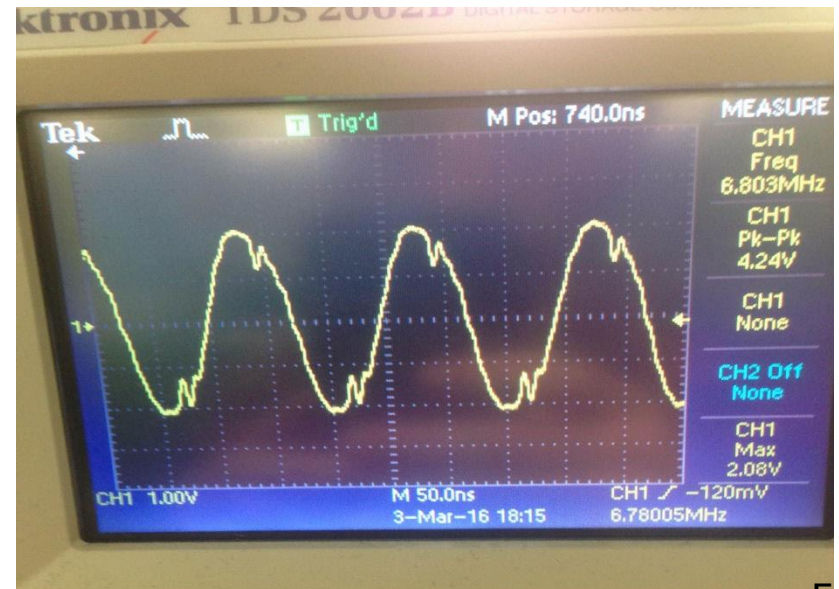
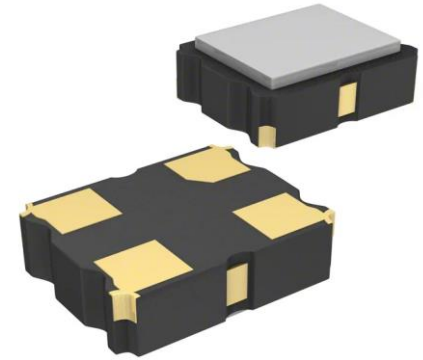
# Oscillator

- Epson SG-210STF 6.7800ML Crystal Oscillator
- Stable 6.78 MHz frequency of oscillation
- Supply of 1.6V-3.6V and 1.8mA
- Output amplitude is directly proportional to supply voltage



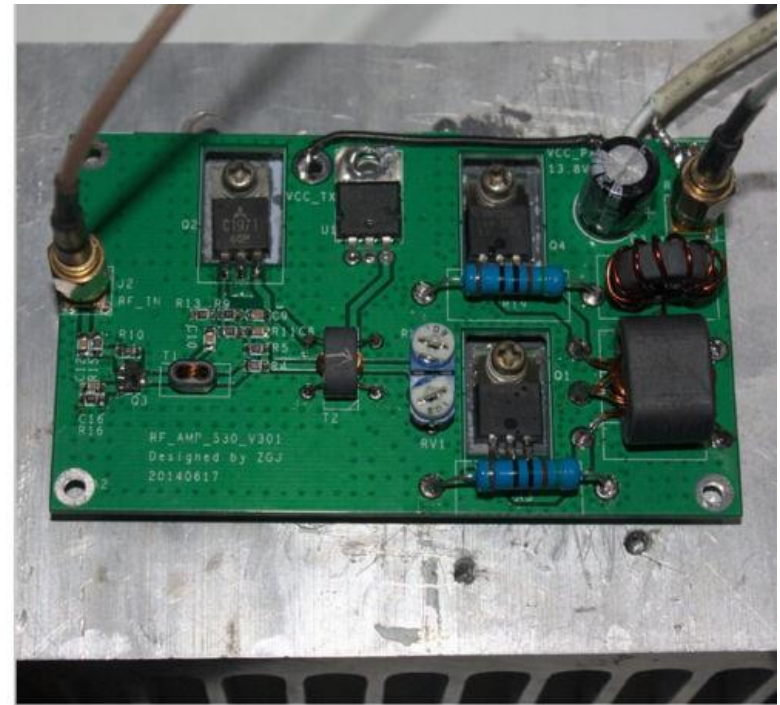
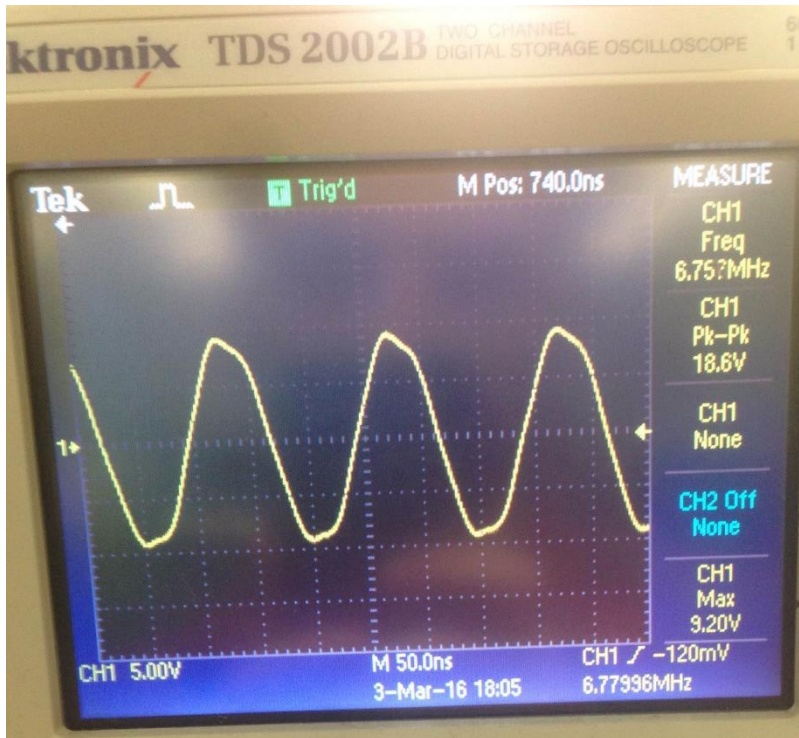
# Power Amplifier

- Linear power amplifier
- Input 1mW-5mW
- 40dB gain, 45W max output power
- 3MHz-30MHz input frequency range
- SMA connectors on input and output



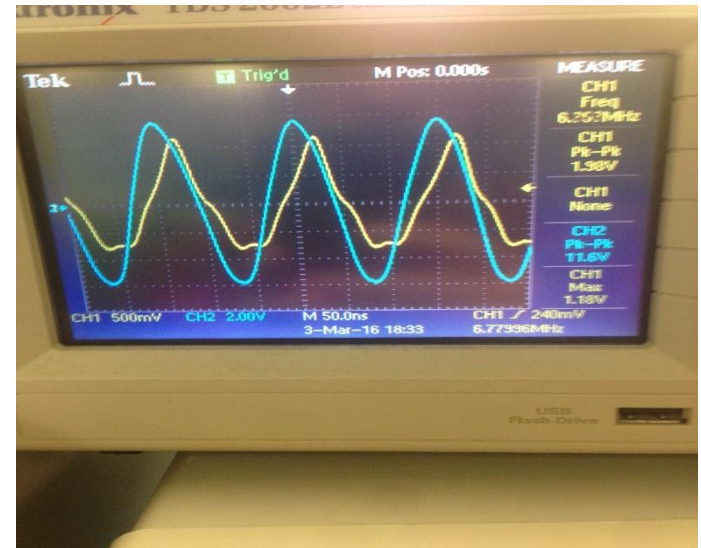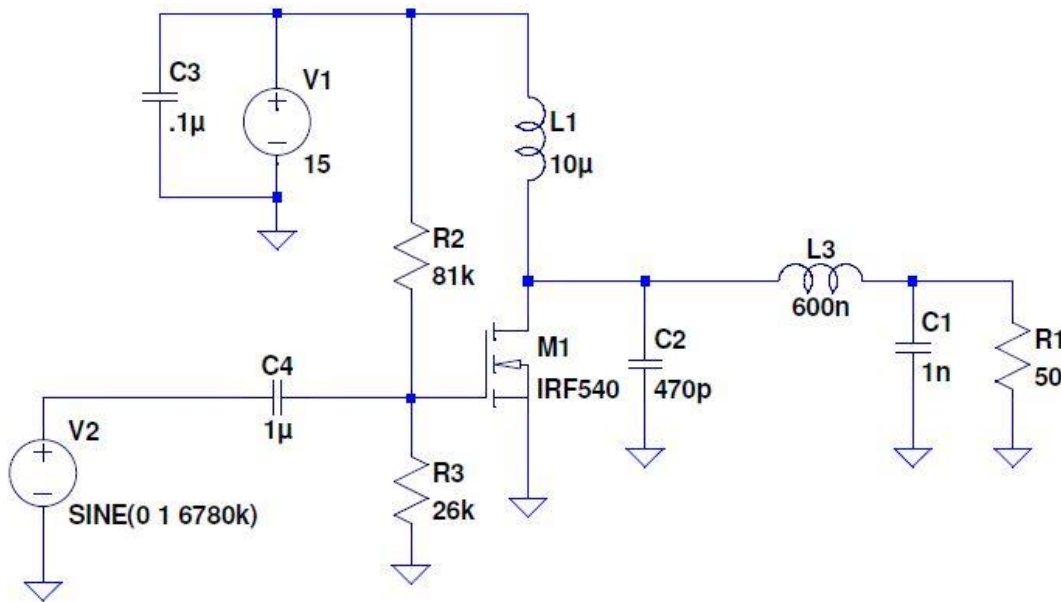
# Power Amplifier

- Class E amplifier design
- ~15dB voltage gain
- Up to 40W output


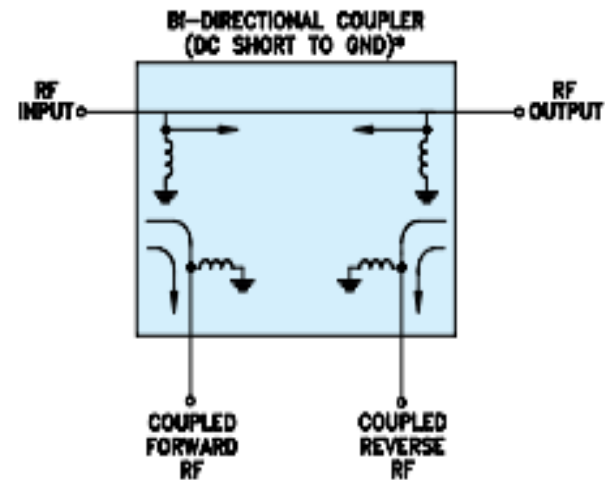
# Directional Coupler


- Goal: Measure incident and reflected power from transmitting coil to quantify match
- Mini-Circuits SYDC-20-31HP+ Bi-directional Coupler
- 0.07 dB mainline loss
- 50 W power handling capability
- >41 dB directivity
- 20.4 dB coupling
- 36 dB return loss




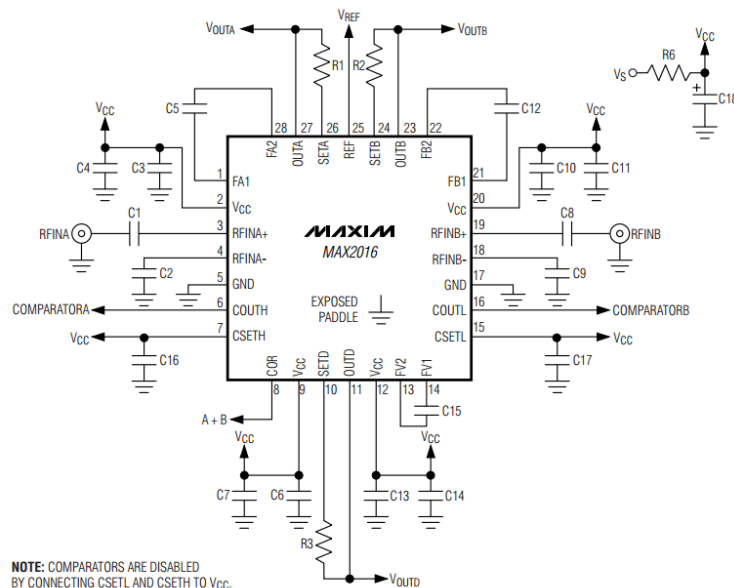
# SWR Measure

- Goal: Use coupled ports from bi-directional coupler to measure incident and reflected powers and provide proportional DC voltage
- Maxim Integrated MAX2016 LF-to-2.5GHz Dual Logarithmic Detector
- RF Input Power Range: -70 to +10 dBm



$$P_{RFIN\_} = \frac{V_{OUT\_}}{SLOPE} + P_{INT}$$

$$R_L = P_{RFINA} - P_{RFINB}$$

$$V_{SWR} = \frac{1 + 10^{-\left(\frac{R_L}{20}\right)}}{1 - 10^{-\left(\frac{R_L}{20}\right)}}$$

# Coil Design

Recall Transmitter Limitation Due To Receiver Size:

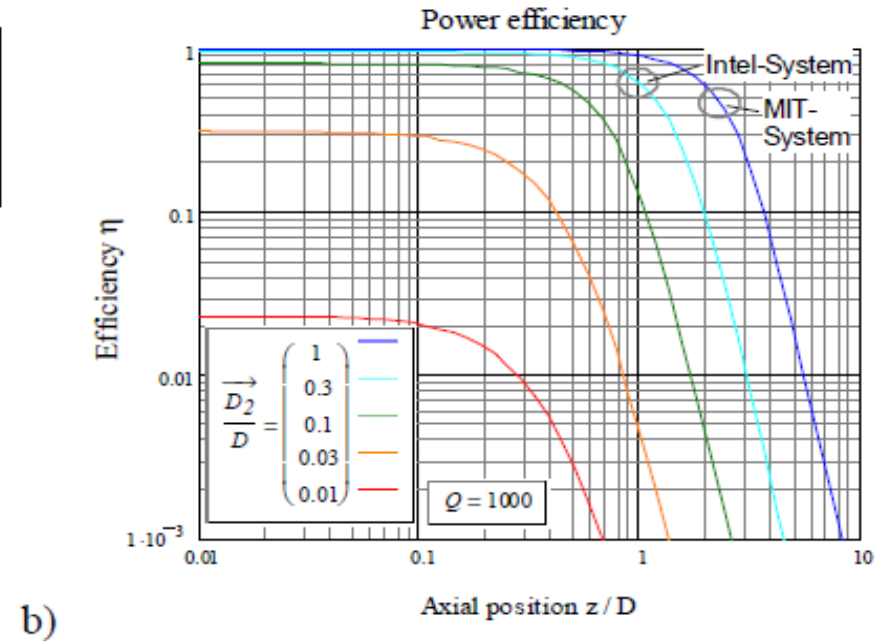
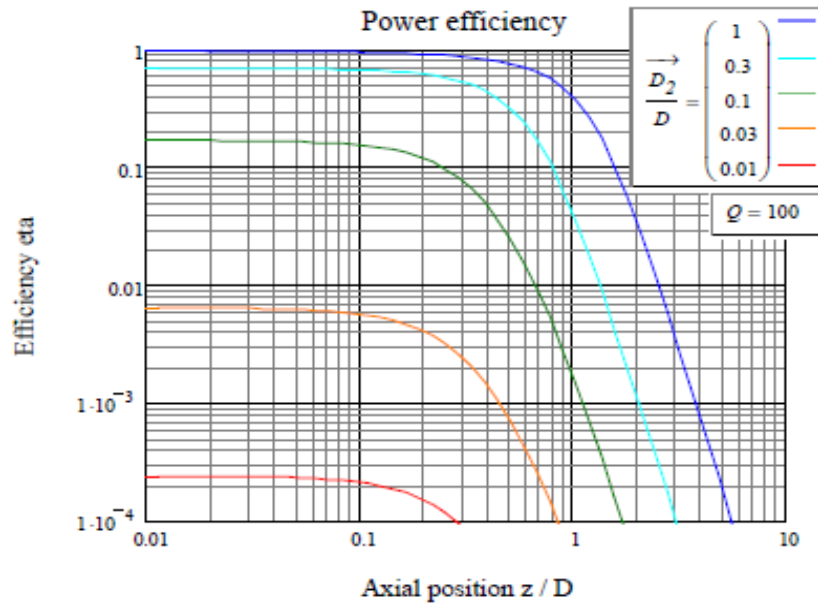


Figure 7: Power efficiency for an inductive power transfer system consisting of loop inductors in dependence on their axial distance  $z$  with size ratio as parameter. Calculated for a quality factor of a)  $Q = 100$ , b)  $Q = 1000$


Waffenschmidt, Eberhard, and Toine Staring. "Limitation of inductive power transfer for consumer applications." In *Power Electronics and Applications, 2009. EPE'09. 13th European Conference on*, pp. 1-10. IEEE, 2009.

# Coil Design

Coil Design Limited to ~175 mm Outer Diameter

Purchased Coil:

Dimensions: [mm]

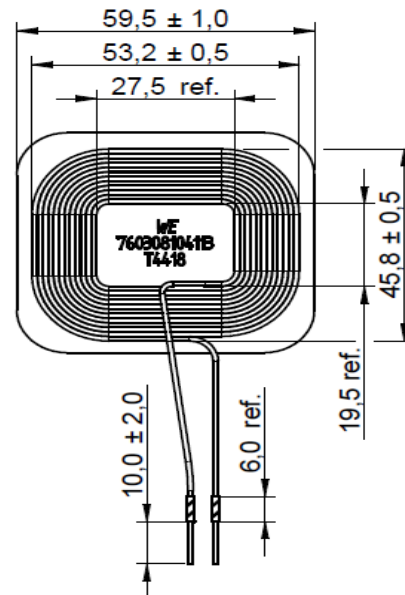

## Electrical Properties

Properties	Test conditions		Value	Unit	Tol.
Inductance	125 kHz/ 10 mA	L	12	μH	±10%
Q-factor	125 kHz/ 10 mA	Q	120		
Rated Current	ΔT = 40 K	I <sub>R</sub>	8	A	max.
Saturation Current		I <sub>SAT</sub>	10	A	typ.
DC Resistance	@ 20°C	R <sub>DC</sub>	0.06	Ω	typ.
DC Resistance	@ 20°C	R <sub>DC</sub>	0.072	Ω	max.
Self Resonant Frequency		f <sub>res</sub>	16	MHz	

# Coil Design

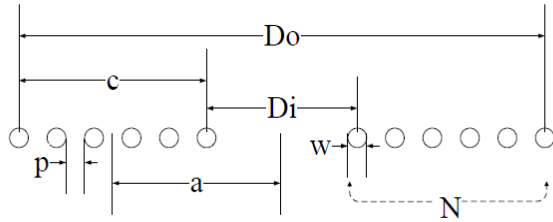


Fig. 1. Cross-sectional view of flat spiral coil.

$$D_i = D_o - 2N(w + p), \quad l = \frac{1}{2}N\pi(D_o + D_i) \quad (1)$$

$$a = \frac{1}{4}(D_o + D_i), \quad c = \frac{1}{2}(D_o - D_i) \quad (2)$$

N, number of turns

$D_o$ , Outer Diameter

p, Spacing between turns

w, Wire Diameter

$D_i$ , Inner Diameter

l, total wire length

a, winding radius

c, radial depth

f, Resonant Frequency

$$L(H) = \frac{N^2(D_o - N(w + p))^2}{16D_o + 28N(w + p)} \times \frac{39.37}{10^6} \quad (3)$$

$$R_{DC} = \frac{l}{\sigma\pi(w/2)^2}, \quad \delta = \frac{1}{\sqrt{\pi f\sigma\mu_o}} \quad (5)$$

$$R = R_{DC} \frac{w}{4\delta} = \sqrt{\frac{f\pi\mu_o}{\sigma}} \frac{N(D_o - N(w + p))}{w} \quad (6)$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{39.37}{10^6} \sqrt{\frac{f\pi\sigma}{\mu_o}} \frac{wN(D_o - N(w + p))}{8D_o + 14N(w + p)} \quad (7)$$

B. H. Waters, B. J. Mahoney, Gunbok Lee and J. R. Smith, "**Optimal coil size ratios for wireless power transfer applications**," Circuits and Systems (ISCAS), 2014 IEEE International Symposium on, Melbourne VIC, 2014, pp. 2045-2048.

# Coupling Factor and Coefficient Calculation

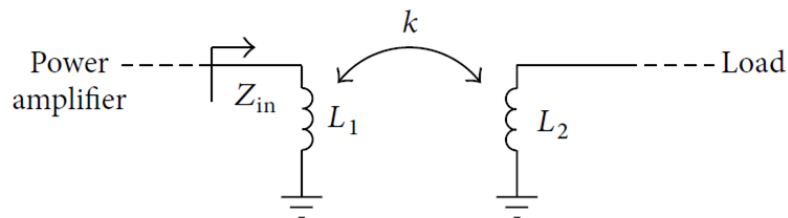


FIGURE 1: Inductive link schematic.

$$M = \frac{\mu\pi n_1 n_2 a^2 b^2}{\sqrt{(a+b)^2 + d^2} [(a-b)^2 + d^2]} \quad (14)$$


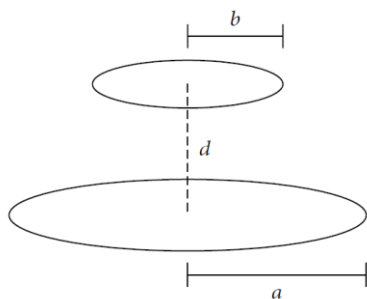


FIGURE 2: Two coaxial coils with radii  $a$  and  $b$ .


$$k = \frac{M}{\sqrt{L_i L_j}}$$
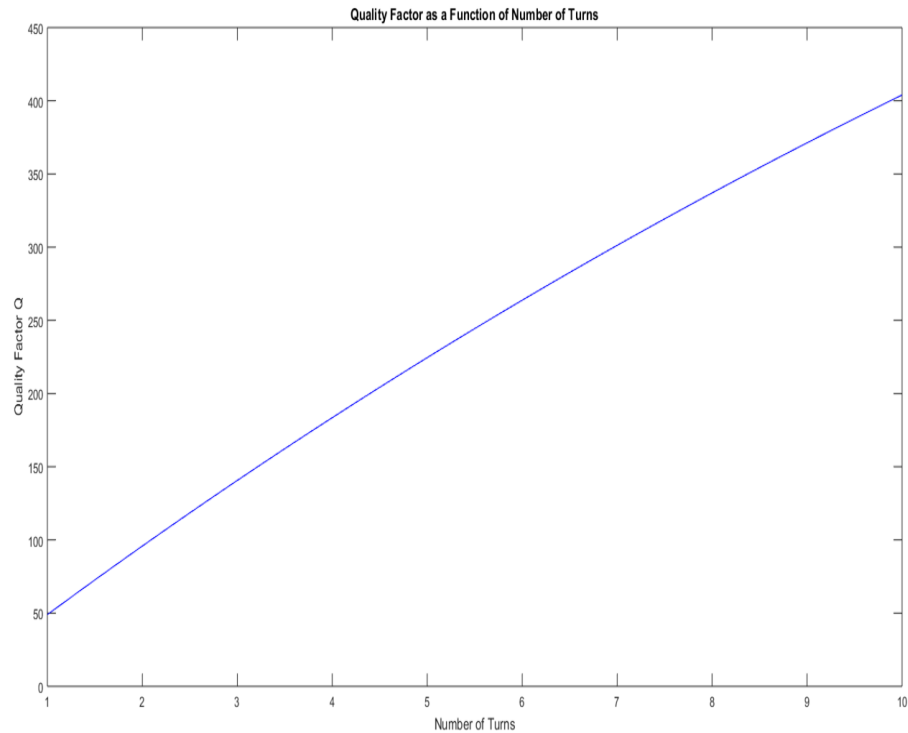
# Variable Effects

Quality Factor as a Function of Number of Turns




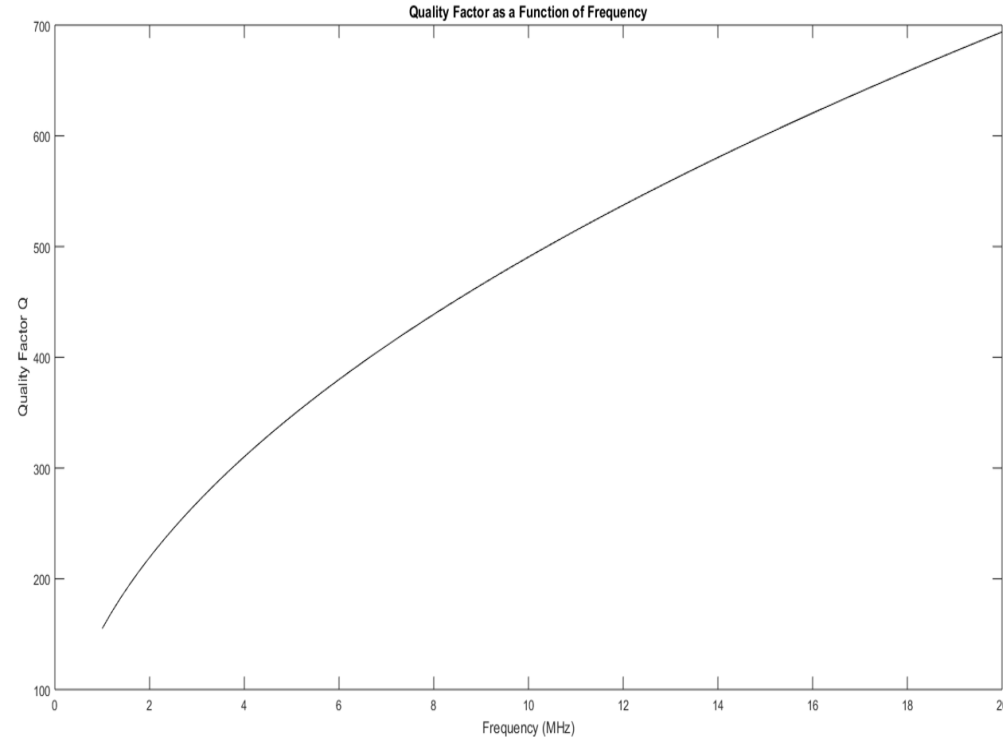Quality Factor as a Function of Frequency



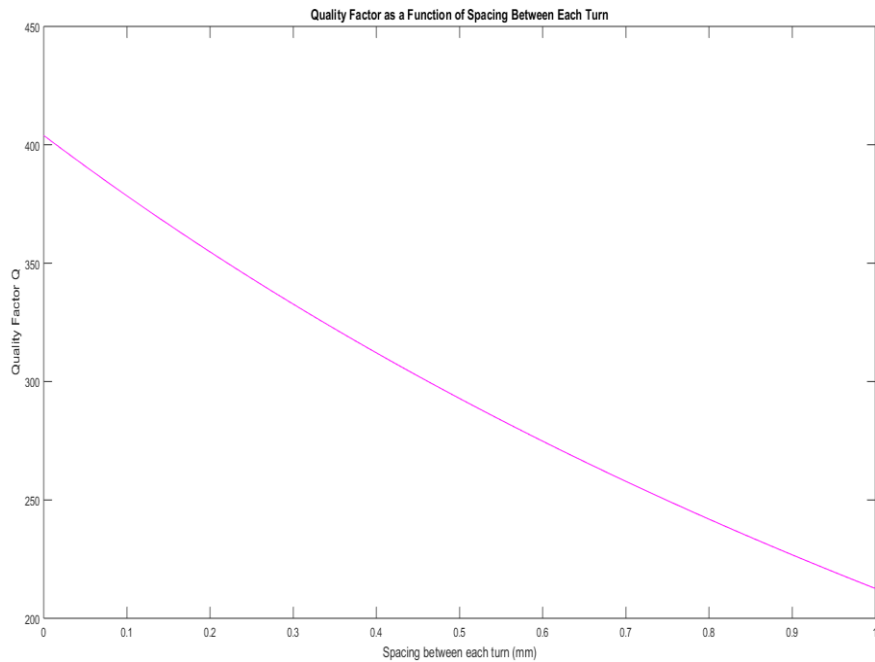
# Variable Effects

Quality Factor as a Function of Turn Spacing




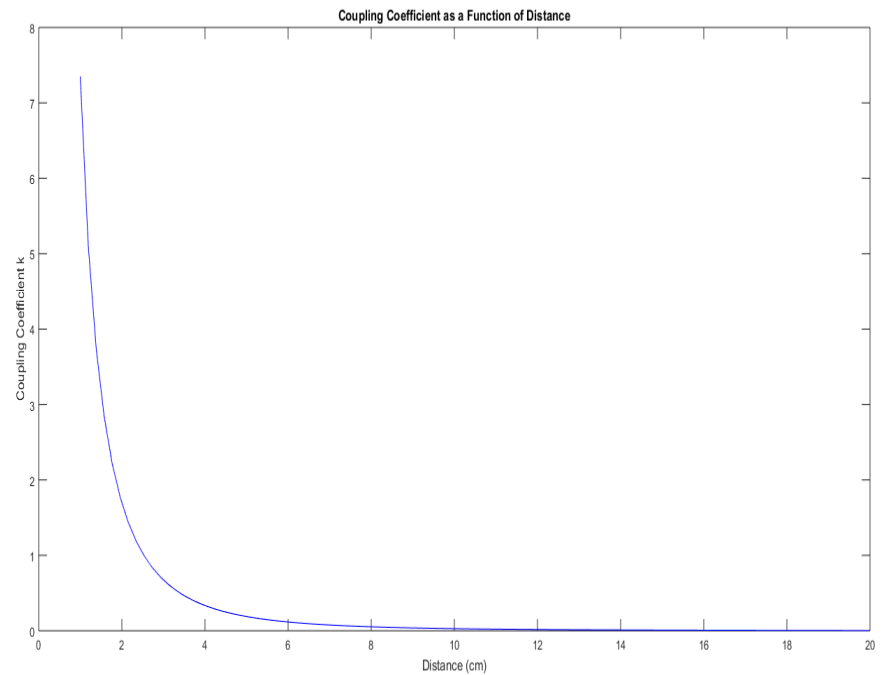Coupling Coefficient as a Function of Distance



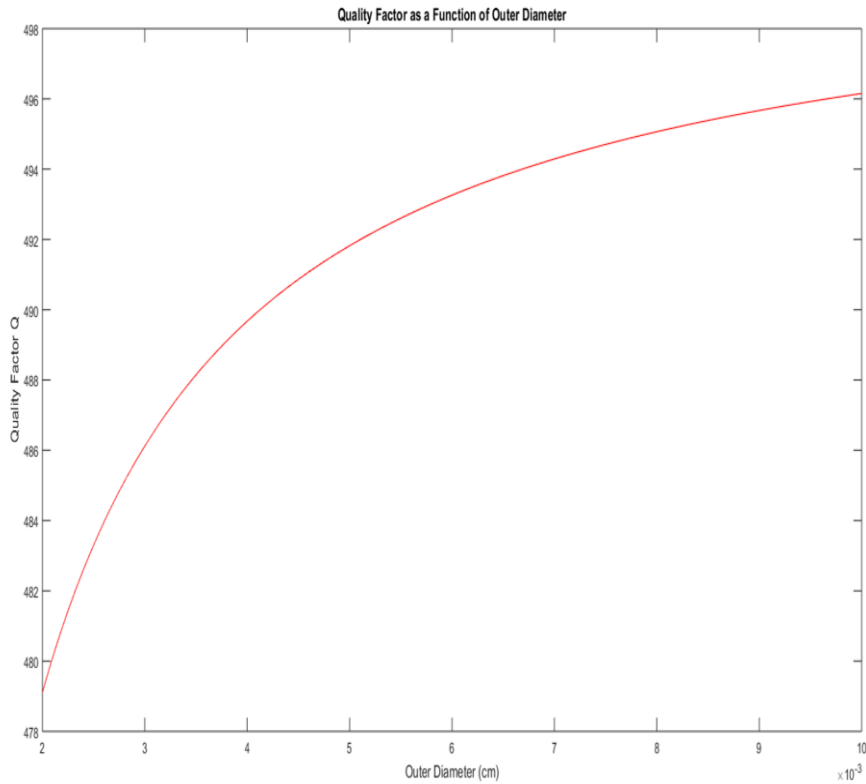
# Variable Effects

Quality Factor as Function of Outer Diameter



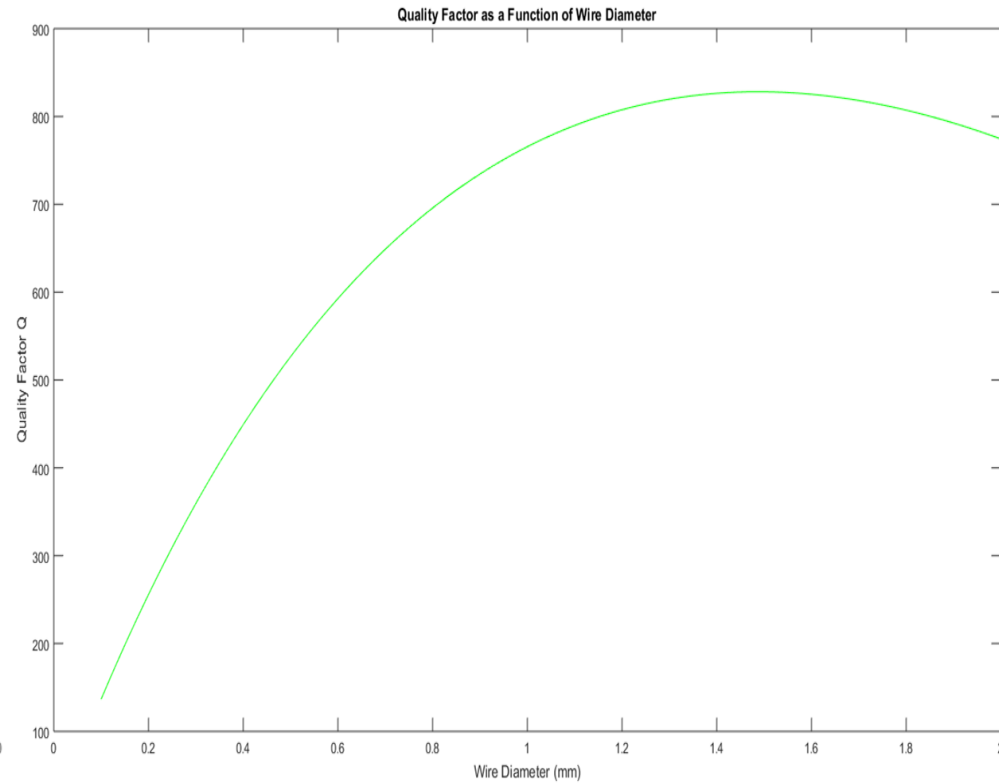
Quality Factor as Function of Wire Diameter





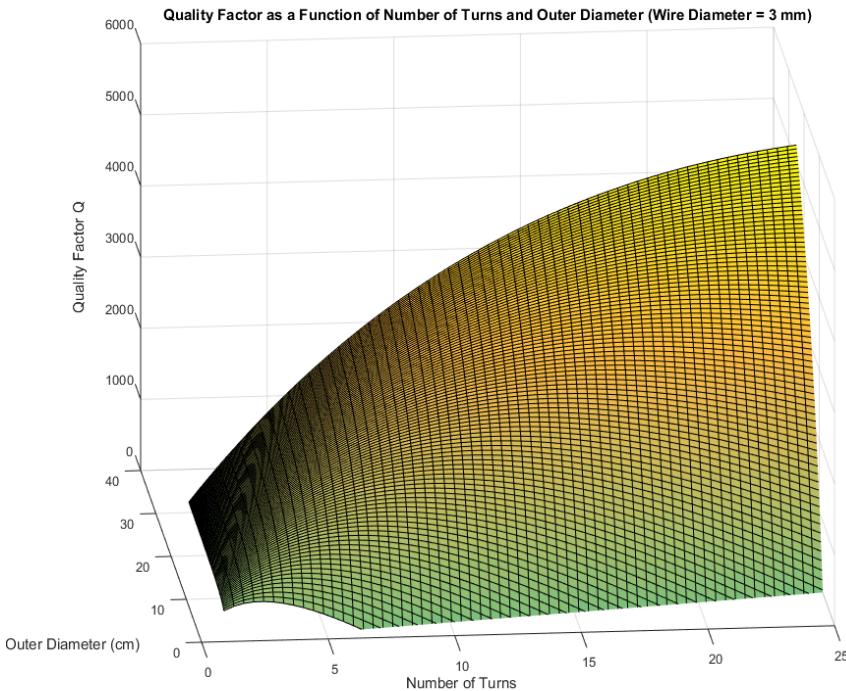
# 3 Dimensional Analysis on Variables

Quality Factor as Function of Turns and Outer Diameter




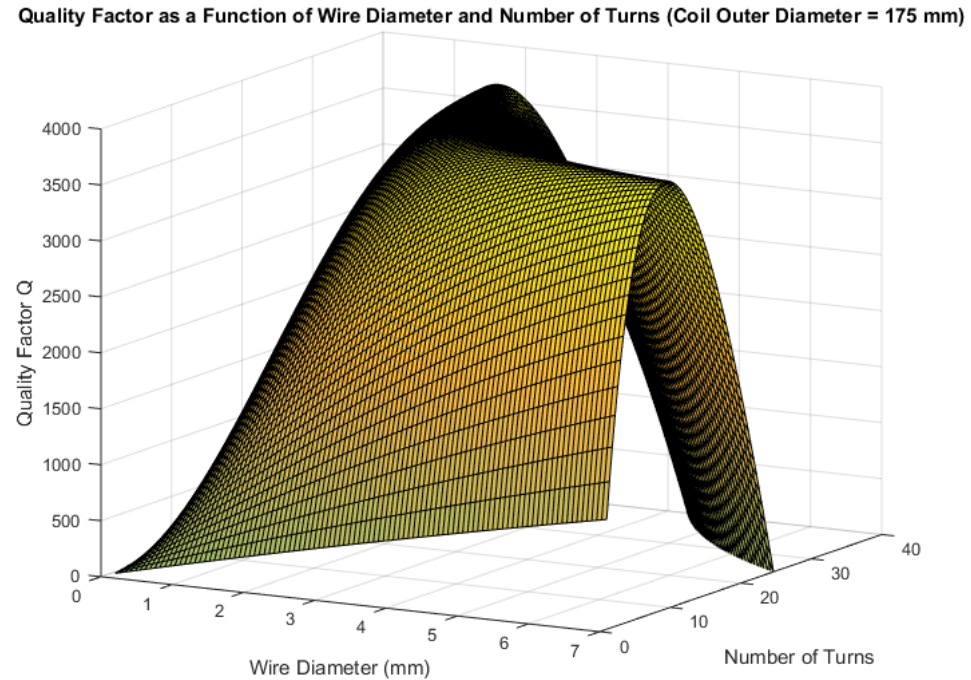Quality Factor as Function of Turns and Wire Diameter



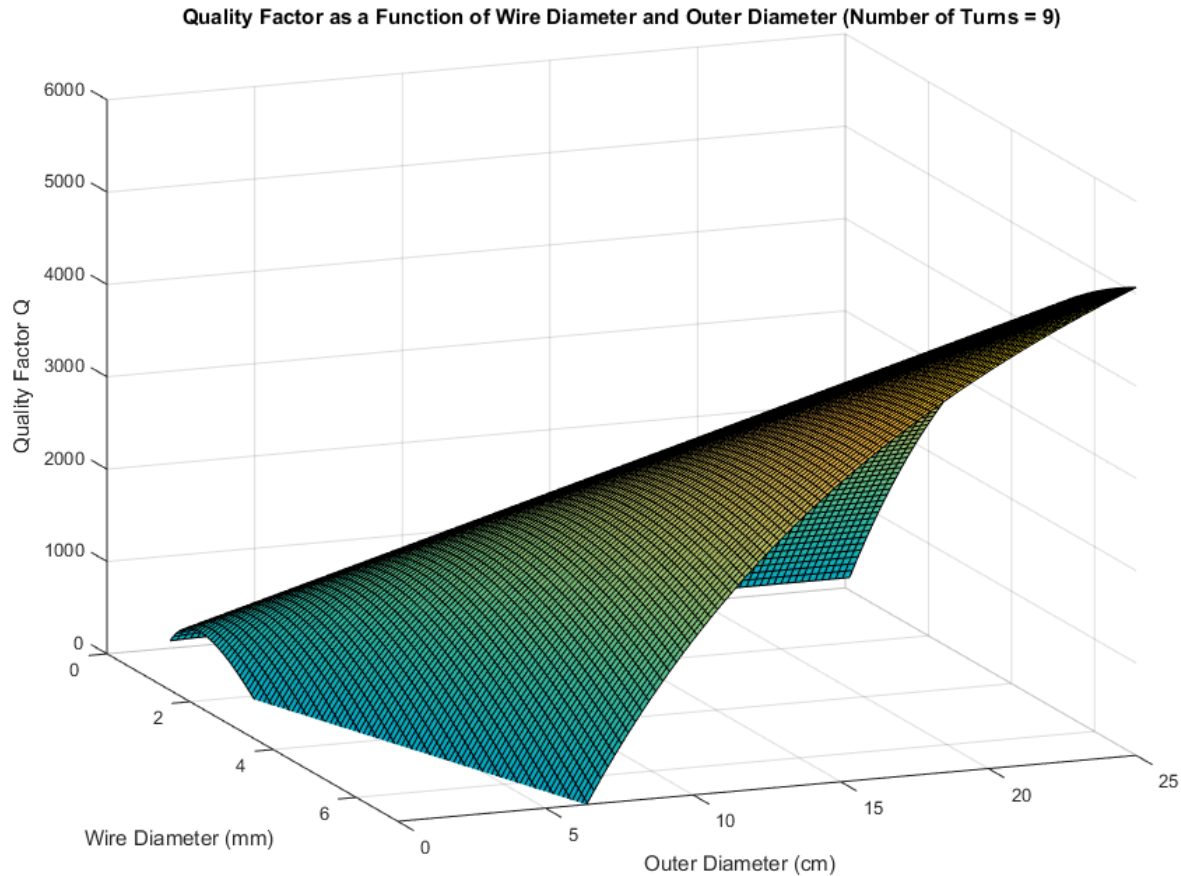
# 3 Dimensional Analysis on Variables

Quality Factor as Function of Outer Diameter and Wire Diameter



# Real Vs. Theoretical (Transmitter)

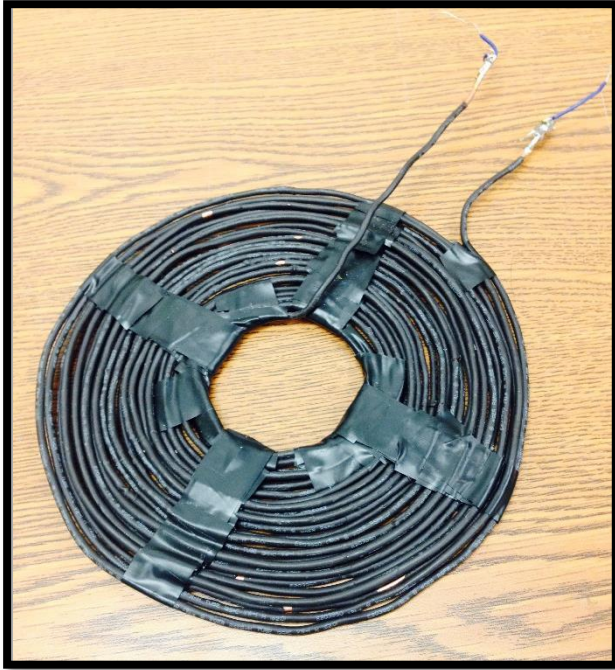

## Picked Values for Transmitting Coil

- $D_0 = 175\text{mm}$
- $w = 2.05\text{ mm (12AWG)}$
- $N = 23\text{ turns}$
- $s = \text{As close to zero as possible}$

## Theoretical Values:

$$Q_{\text{Factor}} = 3544 \quad C = 6.602\text{ pF}$$

$$L = 83.233\text{ uH} \quad R(\text{AC}) = .9440\text{ ohms}$$

## Measured Values

$$Q_{\text{Factor}} = 5137.058 \quad C = \text{assumed } 0\text{ F}$$

$$L = 61.5\text{ uH} \quad R(\text{AC}) = .51\text{ ohms}$$

# Impedance Matching

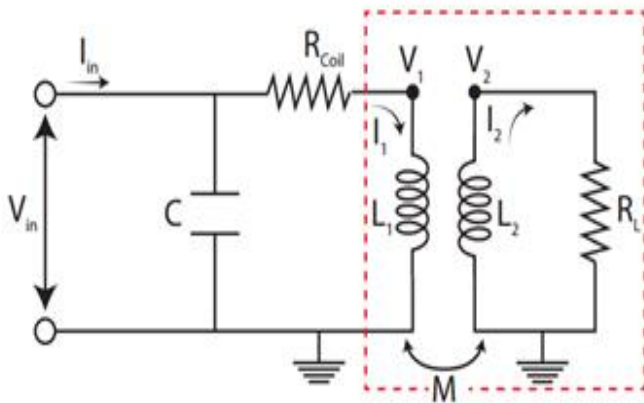


FIGURE 4. Circuit diagram of the driving coil and receiving coil

From  $Z_{in}$ , we calculated the impedance matching network values by setting  $Z_{in}$  to be our load ( $R_L + jX_L$ ).

Where,


$$M = \frac{\mu_0}{4\pi} \oint_{C_{emitter}} \oint_{C_{receiver}} \frac{ds_{receiver} \cdot ds_{emitter}}{|R_{emitter,receiver}|} = k\sqrt{L_1 L_2},$$

$$\frac{V_1}{I_1} = Z_{ind} = i\omega L_1 - \frac{\omega^2 M^2}{R_L - i\omega L_2}, \quad Z_{eq} = \left[ i\omega C + \frac{1}{R_C + Z_{ind}} \right]^{-1}$$

Bhutada, Manasi, Vikaram Singh, and Chirag Warty. "Transmission of Wireless Power in two-coil and four-coil systems using couple d mode theory." In Aerospace Conference, 2015 IEEE, pp. 1-8. IEEE, 2015.


$$Z_{in} = R_{1S} + j\omega L_1 + \frac{\omega^2 M^2}{j\omega L_2 R_{2S} + Z_L},$$

## PI Network Impedance Matching

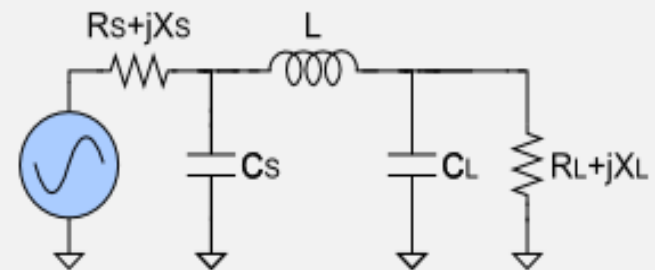


# Impedance Matching Networks

## L-Model Networks

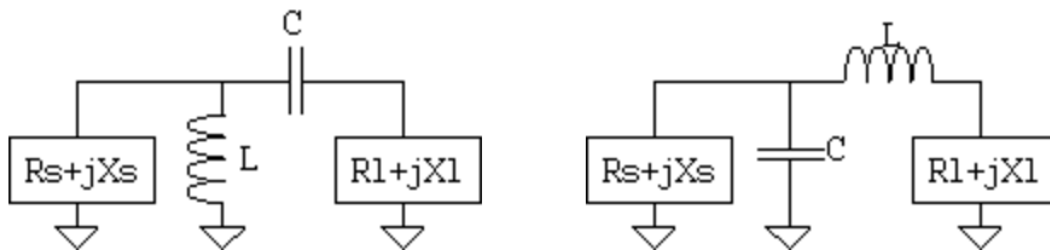

Several Impedance Matching Networks were created and the values determined through online calculators and matlab scripts.

## Pi-Model Network

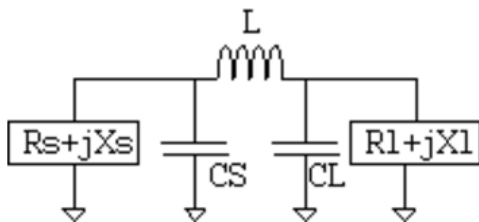

# Self Capacitance of Transmitter Coil

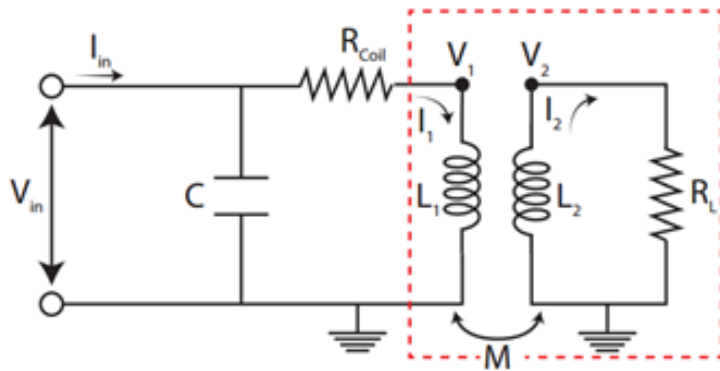


FIGURE 4. Circuit diagram of the driving coil and receiving coil

## Receiver Coil Change



- Transmitting Coil Self Resonating Frequency is at 320 KHz

- C is actually 4.77 nF

- Impedance @6.78 MHz = -5.8492j

- Series inductance needed to tune to resonance

At Resonance

- $L = 4.5 \mu\text{H}$

- $R = .1422$

- Q Factor = 1359.2

# Driving Coil

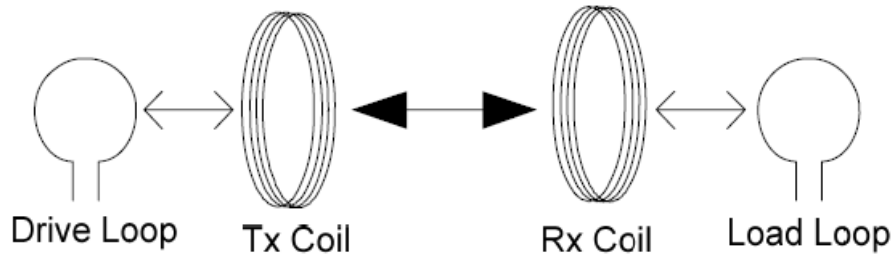


Figure 1. Magnetically coupled resonant wireless power system.

Zhao, Qiang, Anna Wang, and Hao Wang. "Structure Analysis of Magnetic Coupling Resonant for Wireless Power Transmission System." (2015).

- Used a 3 Coil System to better improve Matching
- Steps down voltage
- Driving Coil:  
55 turns & 22 AWG

**Future:** Impedance match to driving coil

# Demonstration

- CDR Deliverables Met:
  - Implement impedance match network for 10 cm
  - Final coil sizes constructed
  - Effectively measure SWR on line
- CDR Deliverables Not Met:
  - Demonstrate system output: 2.5 W over 10 cm





**Demo**

# FDR Goals

- Deliver 2.5W over 10 cm distance
- Deliver power through USB to phone's charging port
- Package transmitting circuitry and house receiving circuitry in a phone case
- Switchable impedance matching network dependent on SWR measurements
- Oscillator fully integrated
- Power supply selected and implemented



# Questions and Comments