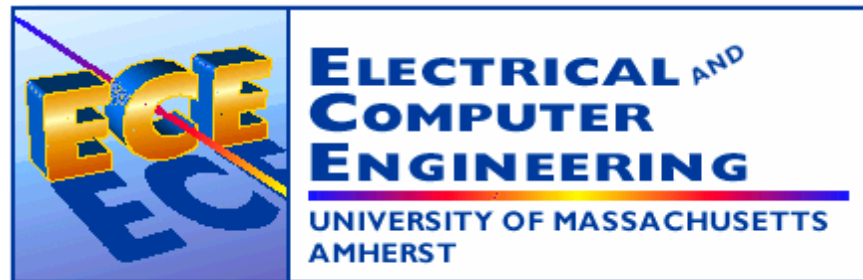

ENGIN 112

Intro to Electrical and Computer Engineering

Lecture 5

Boolean Algebra




Overview

- **Logic functions with 1's and 0's**
 - Building digital circuitry
- **Truth tables**
- **Logic symbols and waveforms**
- **Boolean algebra**
- **Properties of Boolean Algebra**
 - Reducing functions
 - Transforming functions

Digital Systems


- **Analysis problem:**

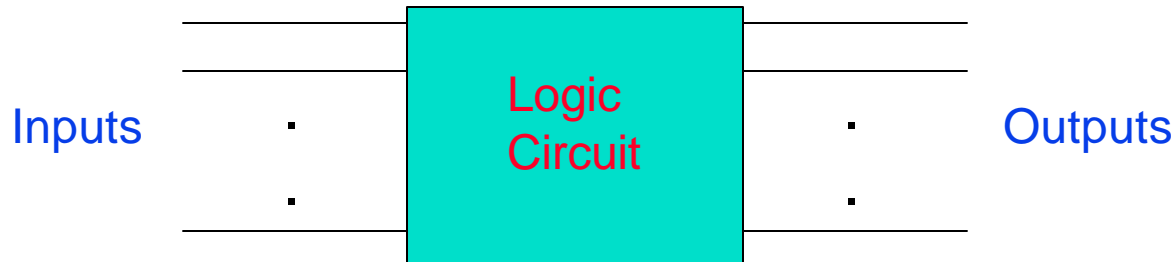


- **Determine binary outputs for each combination of inputs**
- **Design problem: given a task, develop a circuit that accomplishes the task**
 - **Many possible implementation**
 - **Try to develop “best” circuit based on some criterion (size, power, performance, etc.)**

Toll Booth Controller

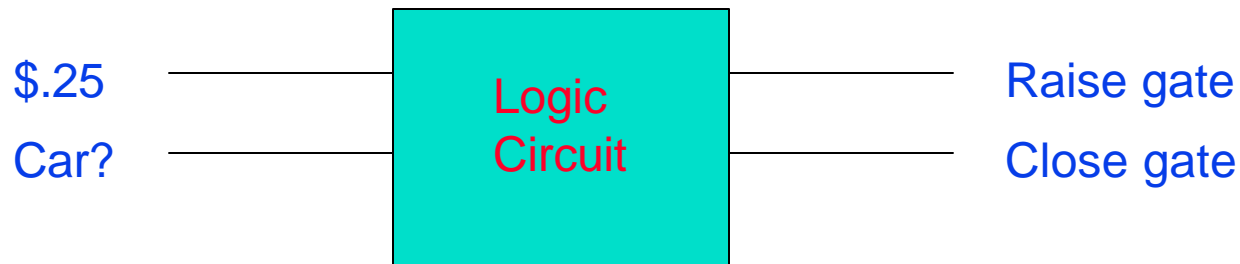
- Consider the design of a toll booth controller
- Inputs: quarter, car sensor
- Outputs: gate lift signal, gate close signal



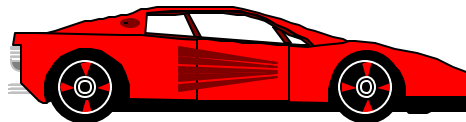- If driver pitches in quarter, raise gate.
- When car has cleared gate, close gate.



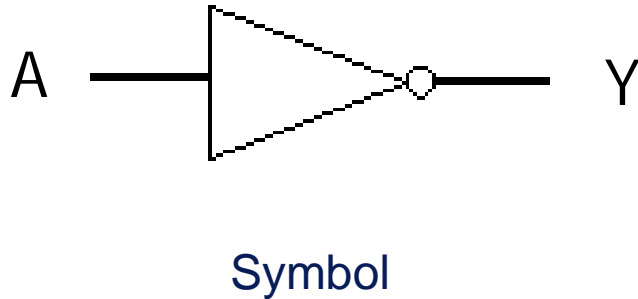Describing Circuit Functionality: Inverter



Truth Table

A	Y
0	1
1	0

Input

Output

- Basic logic functions have symbols.
- The same functionality can be represented with **truth tables**.
 - Truth table completely specifies outputs for all input combinations.
- The above circuit is an inverter.
 - An input of 0 is inverted to a 1.
 - An input of 1 is inverted to a 0.

The AND Gate




- This is an AND gate.
- So, if the two inputs signals are asserted (high) the output will also be asserted. Otherwise, the output will be deasserted (low).

Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


The OR Gate

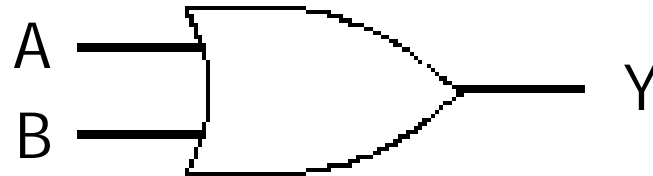

- **This is an OR gate.**
- **So, if either of the two input signals are asserted, or both of them are, the output will be asserted.**

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

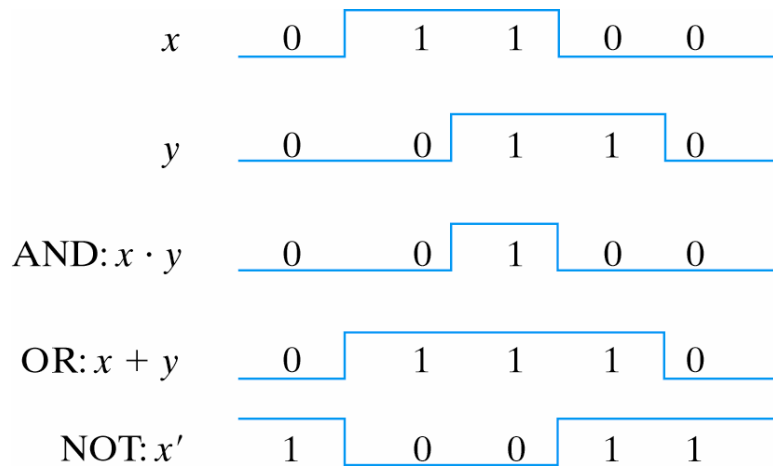Describing Circuit Functionality: Waveforms





AND Gate

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


Fig. 1-5 Input-output signals for gates

- **Waveforms provide another approach for representing functionality.**
- **Values are either high (logic 1) or low (logic 0).**
- **Can you create a truth table from the waveforms?**

Consider three-input gates

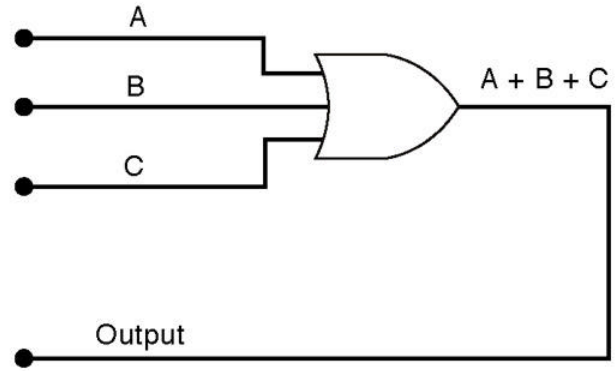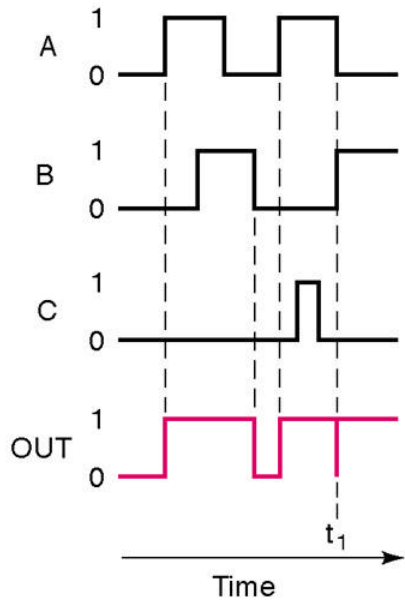


3 Input OR Gate

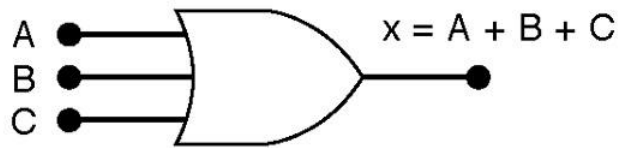

A	B	C	$x = A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Ordering Boolean Functions

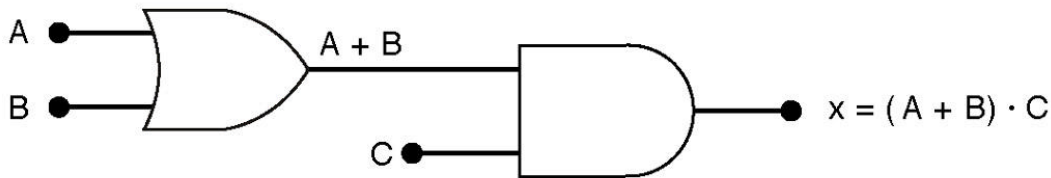- How to interpret $A \cdot B + C$?
 - Is it $A \cdot B$ ORed with C ?
 - Is it A ANDed with $B + C$?
- Order of precedence for Boolean algebra: **AND before OR.**
- Note that parentheses are needed here :



Boolean Algebra

- A *Boolean algebra* is defined as a closed algebraic system containing a set K or two or more elements and the two operators, $.$ and $+$.
- Useful for identifying and *minimizing* circuit functionality
- Identity elements
 - $a + 0 = a$
 - $a . 1 = a$
- 0 is the identity element for the $+$ operation.
- 1 is the identity element for the $.$ operation.

Commutativity and Associativity of the Operators

◦ **The Commutative Property:**

For every a and b in K,

- $a + b = b + a$
- $a \cdot b = b \cdot a$

◦ **The Associative Property:**

For every a, b, and c in K,

- $a + (b + c) = (a + b) + c$
- $a \cdot (b \cdot c) = (a \cdot b) \cdot c$

Distributivity of the Operators and Complements

- **The Distributive Property:**

For every a, b, and c in K,

- $a + (b \cdot c) = (a + b) \cdot (a + c)$
- $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$

- **The Existence of the Complement:**

For every a in K there exists a unique element called a' (*complement of a*) such that,

- $a + a' = 1$
- $a \cdot a' = 0$

- **To simplify notation, the \cdot operator is frequently omitted. When two elements are written next to each other, the AND (\cdot) operator is implied...**

- $a + b \cdot c = (a + b) \cdot (a + c)$
- $a + bc = (a + b)(a + c)$

Duality

- The principle of *duality* is an important concept. This says that if an expression is valid in Boolean algebra, the dual of that expression is also valid.
- To form the dual of an expression, replace all + operators with . operators, all . operators with + operators, all ones with zeros, and all zeros with ones.
- Form the dual of the expression
$$a + (bc) = (a + b)(a + c)$$
- Following the replacement rules...
$$a(b + c) = ab + ac$$
- Take care not to alter the location of the parentheses if they are present.

Involution

◦ **This theorem states:**

$$a'' = a$$

◦ **Remember that $aa' = 0$ and $a+a'=1$.**

- **Therefore, a' is the complement of a and a is also the complement of a' .**
- **As the complement of a' is unique, it follows that $a''=a$.**

◦ **Taking the double inverse of a value will give the initial value.**

Absorption

- **This theorem states:**

$$a + ab = a$$

$$a(a+b) = a$$

- **To prove the first half of this theorem:**

$$a + ab = a \cdot 1 + ab$$

$$= a (1 + b)$$

$$= a (b + 1)$$

$$= a (1)$$

$$a + ab = a$$

DeMorgan's Theorem

- A key theorem in simplifying Boolean algebra expression is DeMorgan's Theorem. It states:

$$(a + b)' = a'b'$$

$$(ab)' = a' + b'$$

- Complement the expression $a(b + z(x + a'))$ and simplify.

$$\begin{aligned}(a(b+z(x + a')))' &= a' + (b + z(x + a'))' \\ &= a' + b'(z(x + a'))' \\ &= a' + b'(z' + (x + a'))' \\ &= a' + b'(z' + x'a'') \\ &= a' + b'(z' + x'a)\end{aligned}$$

Summary

- **Basic logic functions can be made from AND, OR, and NOT (invert) functions**
- **The behavior of digital circuits can be represented with waveforms, truth tables, or symbols**
- **Primitive gates can be combined to form larger circuits**
- **Boolean algebra defines how binary variables can be combined**
- **Rules for associativity, commutativity, and distribution are similar to algebra**
- **DeMorgan's rules are important.**
 - **Will allow us to reduce circuit sizes.**