


---

# ENGIN 112

## Intro to Electrical and Computer Engineering

### Lecture 6

### *More Boolean Algebra*

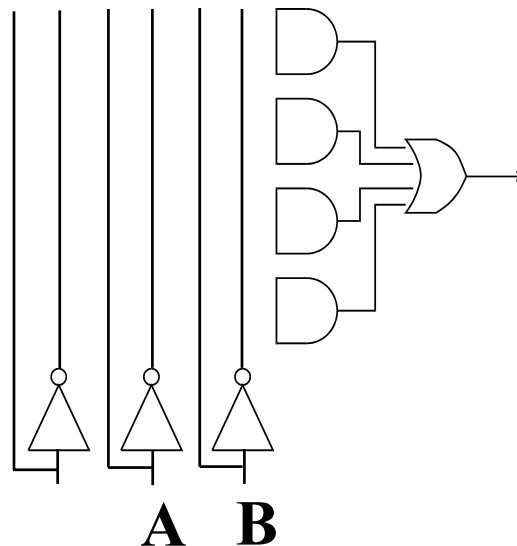

# Overview


---

- **Expressing Boolean functions**
- **Relationships between algebraic equations, symbols, and truth tables**
- **Simplification of Boolean expressions**
- **Minterms and Maxterms**
- **AND-OR representations**
  - **Product of sums**
  - **Sum of products**

# Boolean Functions

- Boolean algebra deals with binary variables and logic operations.
- Function results in binary 0 or 1

x	y	z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

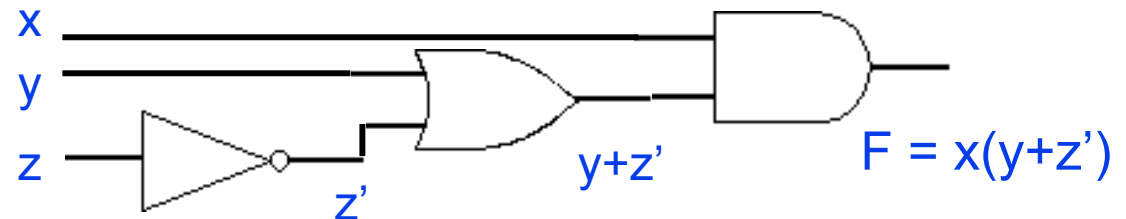


$$F = x(y+z')$$

# Boolean Functions

- Boolean algebra deals with binary variables and logic operations.
- Function results in binary 0 or 1

x	y	z	xy	yz	G
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	1	1
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	1	0	1
1	1	1	1	1	1

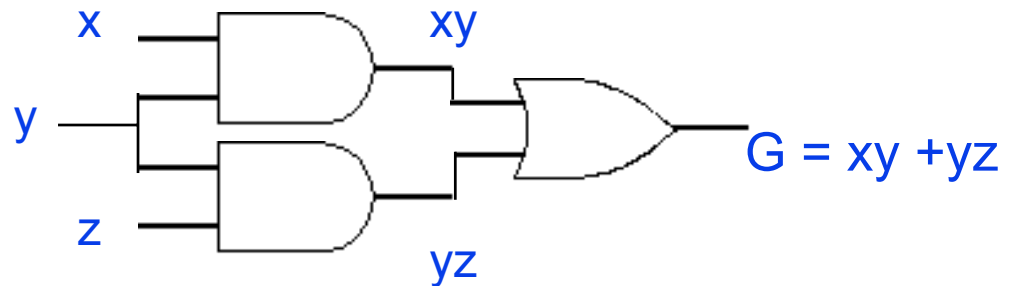


We will learn how to transition between equation, symbols, and truth table.
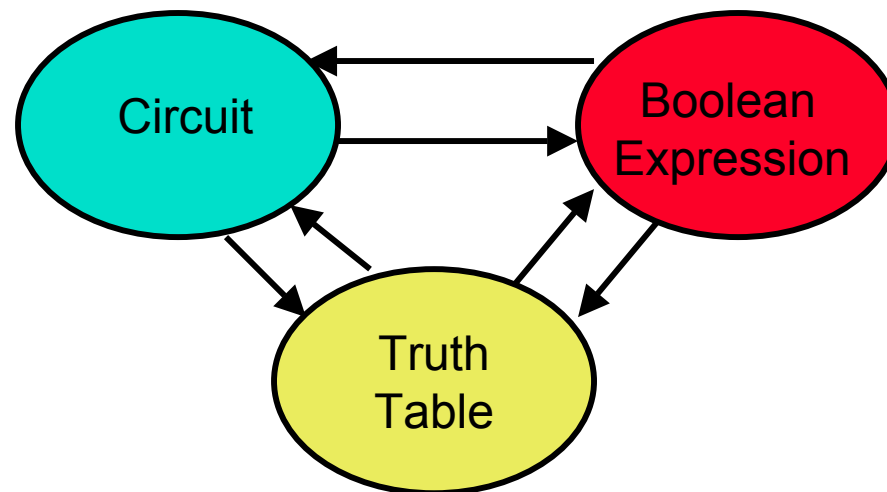
# Representation Conversion

---

- Need to transition between boolean expression, truth table, and circuit (symbols).
- Converting between truth table and expression is easy.
- Converting between expression and circuit is easy.
- More difficult to convert to truth table.



# Truth Table to Expression

- **Converting a truth table to an expression**
  - Each row with output of **1** becomes a **product term**
  - **Sum** product terms together.

x	y	z	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$xyz + xyz' + x'yz$


*Any Boolean Expression can be represented in sum of products form!*

# Equivalent Representations of Circuits

- All three formats are equivalent
- Number of 1's in truth table output column equals AND terms for Sum-of-Products (SOP)

x	y	z	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$G = xyz + xyz' + x'yz$$

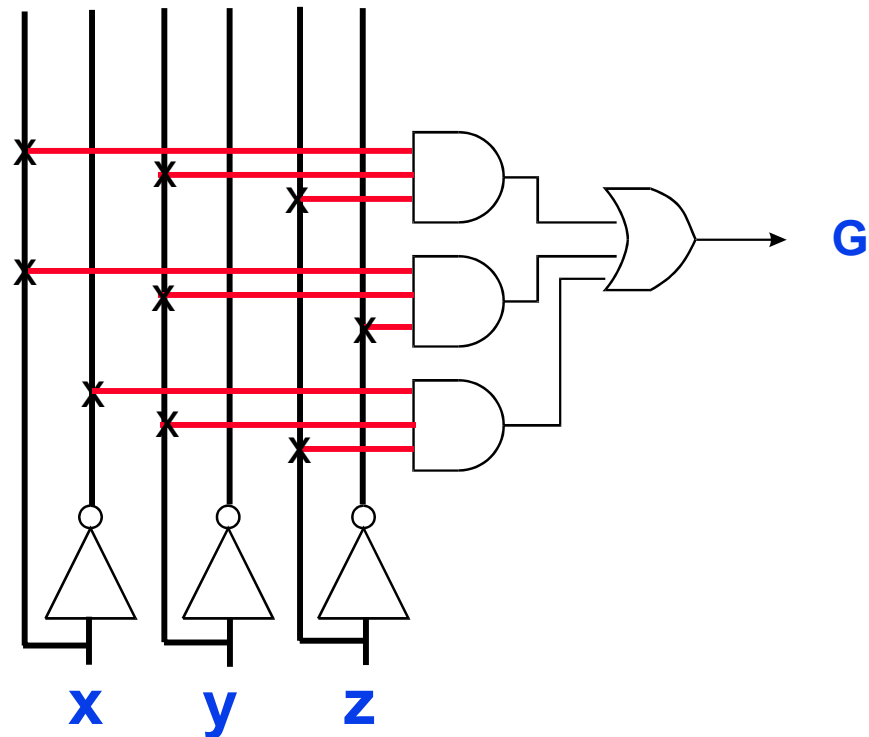

# Reducing Boolean Expressions

---


- Is this the smallest possible implementation of this expression? **No!**  $G = xyz + xyz' + x'yz$
- Use Boolean Algebra rules to reduce complexity while preserving functionality.
- **Step 1: Use Theorem 1 ( $a + a = a$ )**
  - So  $xyz + xyz' + x'yz = xyz + xyz + xyz' + x'yz$
- **Step 2: Use distributive rule  $a(b + c) = ab + ac$** 
  - So  $xyz + xyz + xyz' + x'yz = xy(z + z') + yz(x + x')$
- **Step 3: Use Postulate 3 ( $a + a' = 1$ )**
  - So  $xy(z + z') + yz(x + x') = xy.1 + yz.1$
- **Step 4: Use Postulate 2 ( $a . 1 = a$ )**
  - So  $xy.1 + yz.1 = xy + yz = xyz + xyz' + x'yz$



# Reduced Hardware Implementation

- Reduced equation requires less hardware!
- Same function implemented!

x	y	z	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

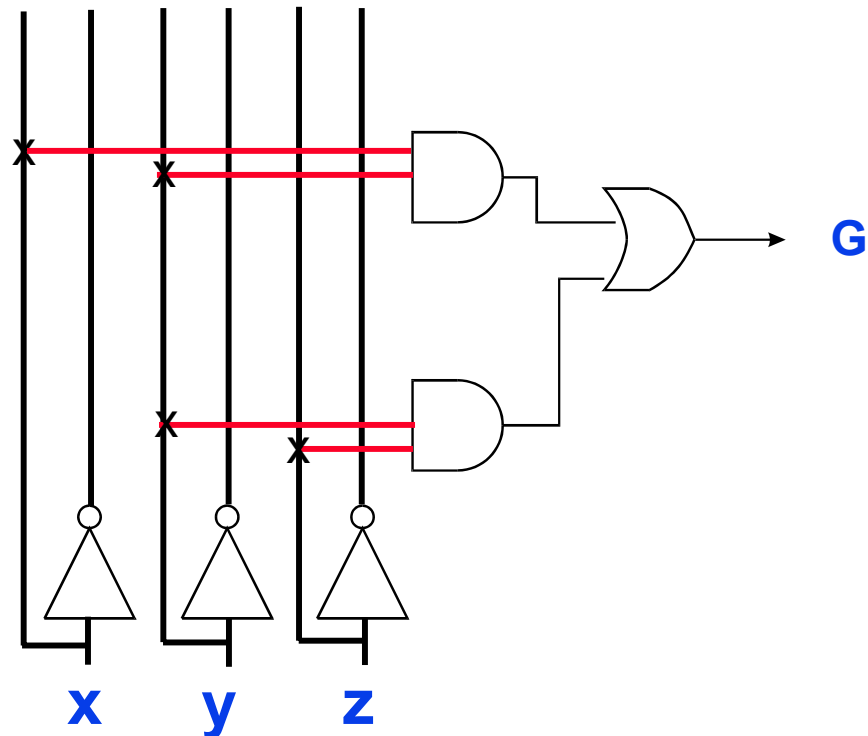

$$G = xyz + xyz' + x'yz = xy + yz$$

# Minterms and Maxterms

---

- Each variable in a Boolean expression is a **literal**
- Boolean variables can appear in normal (**x**) or complement form (**x'**)
- Each AND combination of terms is a minterm
- Each OR combination of terms is a maxterm

For example:  
Minterms

x	y	z	Minterm	
0	0	0	$x'y'z'$	$m_0$
0	0	1	$x'y'z$	$m_1$
...				
1	0	0	$xy'z'$	$m_4$
...				
1	1	1	$xyz$	$m_7$

For example:  
Maxterms

x	y	z	Maxterm	
0	0	0	$x+y+z$	$M_0$
0	0	1	$x+y+z'$	$M_1$
...				
1	0	0	$x'+y+z$	$M_4$
...				
1	1	1	$x'+y'+z'$	$M_7$

# Representing Functions with Minterms

---

- Minterm number same as row position in truth table (starting from top from 0)
- Shorthand way to represent functions

x	y	z	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$G = xyz + xyz' + x'yz$$



$$G = m_7 + m_6 + m_3 = \Sigma(3, 6, 7)$$

# Complementing Functions

---

- Minterm number same as row position in truth table (starting from top from 0)
- Shorthand way to represent functions

x	y	z	G	G'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	1	0

$$G = xyz + xyz' + x'yz$$

$$G' = (xyz + xyz' + x'yz)' =$$

Can we find a simpler representation?

# Complementing Functions

---

- **Step 1: assign temporary names**

- $b + c \rightarrow z$

$$G = a + b + c$$

- $(a + z)' = G'$

$$G' = (a + b + c)'$$

- **Step 2: Use DeMorgans' Law**

- $(a + z)' = a' \cdot z'$

- **Step 3: Resubstitute  $(b+c)$  for  $z$**

- $a' \cdot z' = a' \cdot (b + c)'$

- **Step 4: Use DeMorgans' Law**

$$G = a + b + c$$

- $a' \cdot (b + c)' = a' \cdot (b' \cdot c')$

$$G' = a' \cdot b' \cdot c' = a'b'c'$$

- **Step 5: Associative rule**

- $a' \cdot (b' \cdot c') = a' \cdot b' \cdot c'$

# Complementation Example

---

- Find complement of  $F = x'z + yz$ 
  - $F' = (x'z + yz)'$
- DeMorgan's
  - $F' = (x'z)' (yz)'$
- DeMorgan's
  - $F' = (x''+z')(y'+z')$
- Reduction -> eliminate double negation on x
  - $F' = (x+z')(y'+z')$



This format is called product of sums

# Conversion Between Canonical Forms

- Easy to convert between minterm and maxterm representations
- For maxterm representation, select rows with **0's**

x	y	z	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$G = xyz + xyz' + x'yz$$



$$G = m_7 + m_6 + m_3 = \Sigma(3, 6, 7)$$




$$G = M_0M_1M_2M_4M_5 = \Pi(0, 1, 2, 4, 5)$$




$$G = (x+y+z)(x+y+z')(x+y'+z)(x'+y+z)(x'+y+z')$$
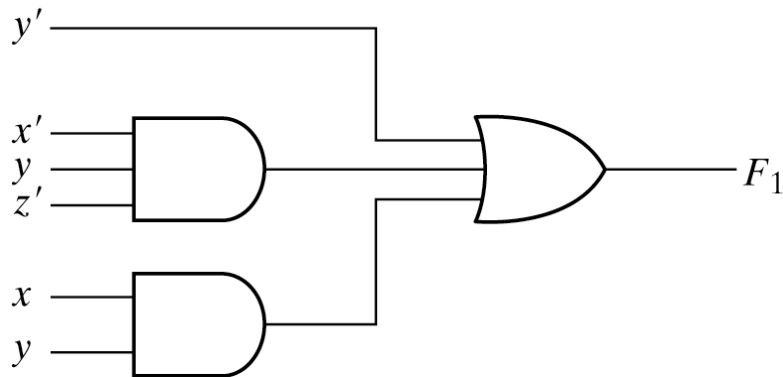
# Representation of Circuits

- All logic expressions can be represented in 2-level format
- Circuits can be reduced to minimal 2-level representation
- Sum of products representation most common in industry.



(a) Sum of Products

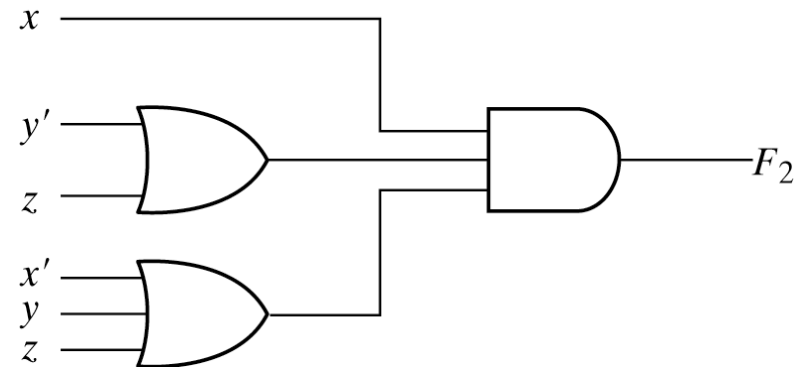

(b) Product of Sums

Fig. 2-3 Two-level implementation



# Summary

---

- Truth table, circuit, and boolean expression formats are equivalent
- Easy to translate truth table to SOP and POS representation
- Boolean algebra rules can be used to reduce circuit size while maintaining function
- All logic functions can be made from AND, OR, and NOT
- Easiest way to understand: **Do examples!**
- Next time: More logic gates!