


---

# ENGIN 112

## Intro to Electrical and Computer Engineering

### Lecture 7
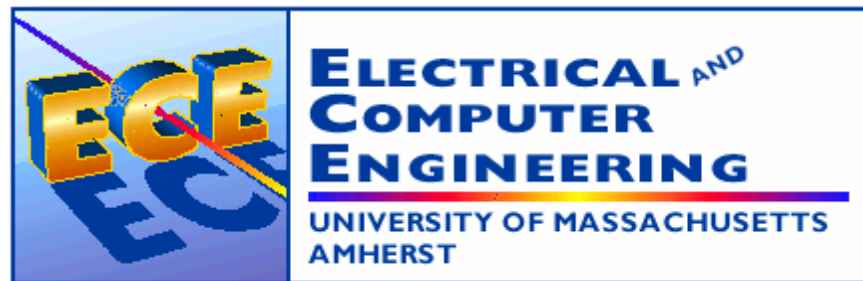
### *More Logic Functions: NAND, NOR, XOR*



# Overview

---

- **More 2-input logic gates (NAND, NOR, XOR)**
- **Extensions to 3-input gates**
- **Converting between sum-of-products and NANDs**
  - SOP to NANDs
  - NANDs to SOP
- **Converting between sum-of-products and NORs**
  - SOP to NORs
  - NORs to SOP
- **Positive and negative logic**
  - We use primarily positive logic in this course.

# Logic functions of **N** variables


---

- Each truth table represents one possible function (e.g. AND, OR)
- If there are  $N$  inputs, there are  $2^N$
- For example, if  $N$  is **2** then there are **16** possible truth tables.
- So far, we have defined 2 of these functions
  - 14 more are possible.
- Why consider new functions?
  - Cheaper hardware, more flexibility.

x	y	G
0	0	0
0	1	0
1	0	0
1	1	1

# The NAND Gate

---

 

- This is a NAND gate. It is a combination of an AND gate followed by an inverter. Its truth table shows this...
- NAND gates have several interesting properties...
  - $\text{NAND}(a,a)=(aa)' = a' = \text{NOT}(a)$
  - $\text{NAND}'(a,b)=(ab)'' = ab = \text{AND}(a,b)$
  - $\text{NAND}(a',b')=(a'b')' = a+b = \text{OR}(a,b)$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

# The NAND Gate


---

- These three properties show that a NAND gate with both of its inputs driven by the same signal is equivalent to a NOT gate
- A NAND gate whose output is complemented is equivalent to an AND gate, and a NAND gate with complemented inputs acts as an OR gate.
- Therefore, we can use a NAND gate to implement all three of the *elementary operators* (AND,OR,NOT).
- **Therefore**, ANY switching function can be constructed using only NAND gates. **Such a gate is said to be *primitive or functionally complete*.**


# NAND Gates into Other Gates

---


(what are these circuits?)

 

NOT Gate

 


AND Gate

 

OR Gate

# The NOR Gate

---

 

- This is a NOR gate. It is a combination of an OR gate followed by an inverter. It's truth table shows this...
- NOR gates also have several interesting properties...
  - $\text{NOR}(a,a)=(a+a)' = a' = \text{NOT}(a)$
  - $\text{NOR}'(a,b)=(a+b)'' = a+b = \text{OR}(a,b)$
  - $\text{NOR}(a',b')=(a'+b')' = ab = \text{AND}(a,b)$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

# Functionally Complete Gates

---


- **Just like the NAND gate, the NOR gate is functionally complete...any logic function can be implemented using just NOR gates.**
- **Both NAND and NOR gates are very valuable as any design can be realized using either one.**
- **It is easier to build an IC chip using all NAND or NOR gates than to combine AND, OR, and NOT gates.**
- **NAND/NOR gates are typically faster at switching and cheaper to produce.**




# NOR Gates into Other Gates

---


(what are these circuits?)

 

NOT Gate

 


OR Gate

 

AND Gate

# The XOR Gate (Exclusive-OR)

---

 


- This is a XOR gate.
- XOR gates assert their output when exactly one of the inputs is asserted, hence the name.
- The switching algebra symbol for this operation is  $\overset{\circ}{A}$ , i.e.  
 $1 \overset{\circ}{A} 1 = 0$  and  $1 \overset{\circ}{A} 0 = 1$ .

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

# The XNOR Gate

---

 



- This is a **XNOR** gate.
- This functions as an **exclusive-NOR** gate, or simply the complement of the **XOR** gate.
- The switching algebra symbol for this operation is  $\odot$ , i.e.

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$1 \odot 1 = 1 \text{ and } 1 \odot 0 = 0.$$

# NOR Gate Equivalence
  
## ° NOR Symbol, Equivalent Circuit, Truth Table



A	B	OR	NOR
		$A + B$	$\overline{A + B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

(c)

# DeMorgan's Theorem

---

- A key theorem in simplifying Boolean algebra expression is DeMorgan's Theorem. It states:

$$(a + b)' = a'b'$$

$$(ab)' = a' + b'$$


- Complement the expression  $a(b + z(x + a'))$  and simplify.

$$\begin{aligned}(a(b+z(x + a')))' &= a' + (b + z(x + a'))' \\ &= a' + b'(z(x + a'))' \\ &= a' + b'(z' + (x + a'))' \\ &= a' + b'(z' + x'a'') \\ &= a' + b'(z' + x'a)\end{aligned}$$

 
# Example

---


- Determine the output expression for the below circuit and simplify it using DeMorgan's Theorem



# Universality of NAND and NOR gates

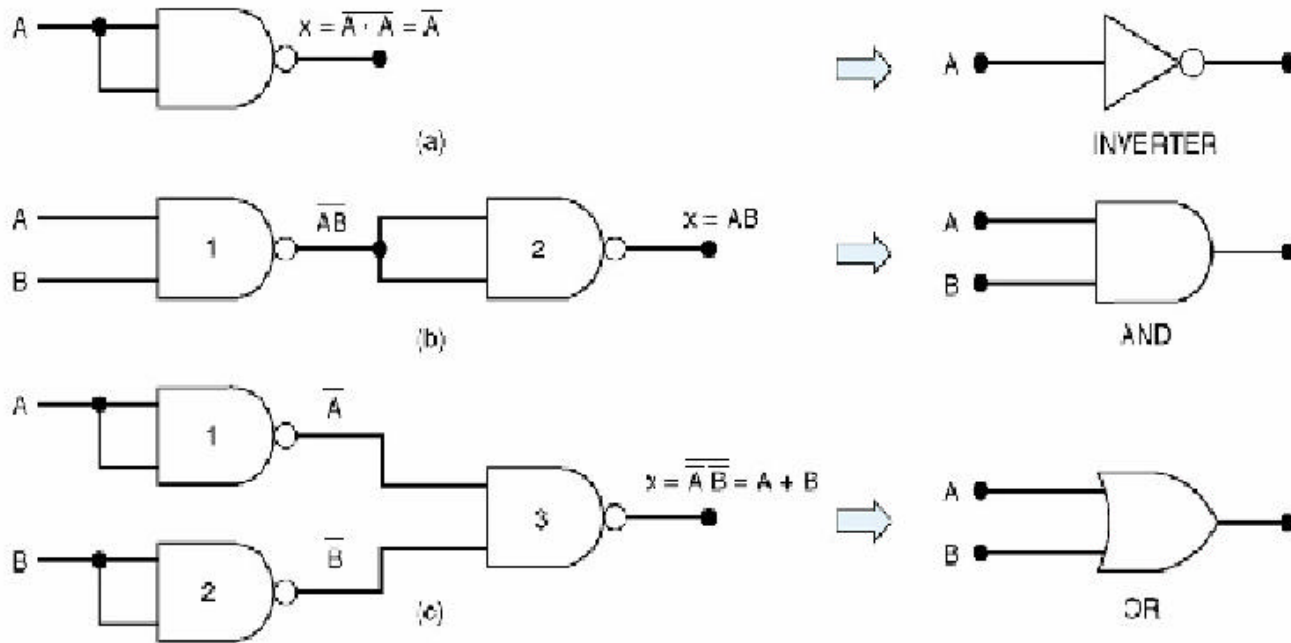




# Universality of NOR gate

 


- Equivalent representations of the AND, OR, and NOT gates




# Example

 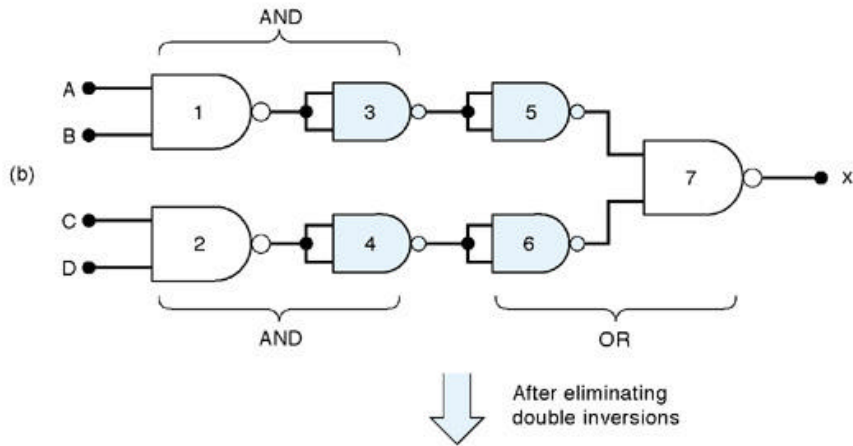 
 
# Interpretation of the two NAND gate symbols



 
Output goes LOW only when all inputs are HIGH.



Output is HIGH when any input is LOW.


- Determine the output expression for circuit via DeMorgan's Theorem
 
# Interpretation of the two OR gate symbols



(a)

Output goes HIGH when any input is HIGH.

 

(b)

Output goes LOW only when all inputs are LOW.

- Determine the output expression for circuit via DeMorgan's Theorem

# Summary

---

- **Basic logic functions can be made from NAND, and NOR functions**
- **The behavior of digital circuits can be represented with waveforms, truth tables, or symbols**
- **Primitive gates can be combined to form larger circuits**
- **Boolean algebra defines how binary variables with NAND, NOR can be combined**
- **DeMorgan's rules are important.**
  - **Allow conversion to NAND/NOR representations**