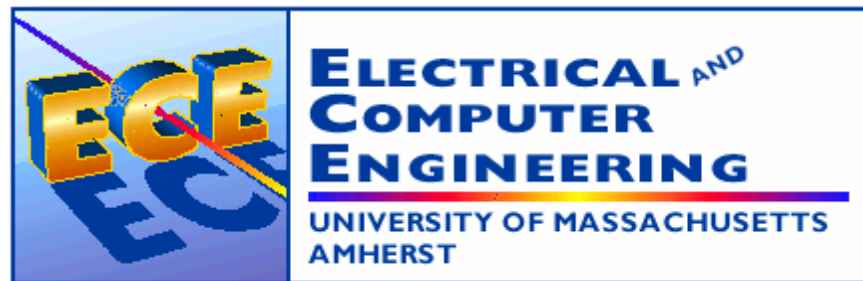

ENGIN 112

Intro to Electrical and Computer Engineering

Lecture 9

More Karnaugh Maps and Don't Cares



Overview

- **Karnaugh maps with four inputs**
 - Same basic rules as three input K-maps
- **Understanding prime implicants**
 - Related to minterms
- **Covering all implicants**
- **Using Don't Cares to simplify functions**
 - Don't care outputs are undefined
- **Summarizing Karnaugh maps**

Karnaugh Maps for Four Input Functions

- Represent functions of 4 inputs with 16 minterms
- Use same rules developed for 3-input functions
- Note bracketed sections shown in example.

 




Fig. 3-8 Four-variable Map

Karnaugh map: 4-variable example

° $F(A,B,C,D) = \Sigma m(0,2,3,5,6,7,8,10,11,14,15)$


$F =$

$$C + A'BD + B'D'$$

  


Solution set can be considered as a coordinate System!


Design examples

 

K-map for LT

 

K-map for EQ

 

K-map for GT


$$LT = A' B' D + A' C + B' C D$$

$$EQ = A' B' C' D' + A' B C' D + A B C D + A B' C D'$$

$$GT = B C' D' + A C' + A B D'$$

Can you draw the truth table for these examples?

Physical Implementation

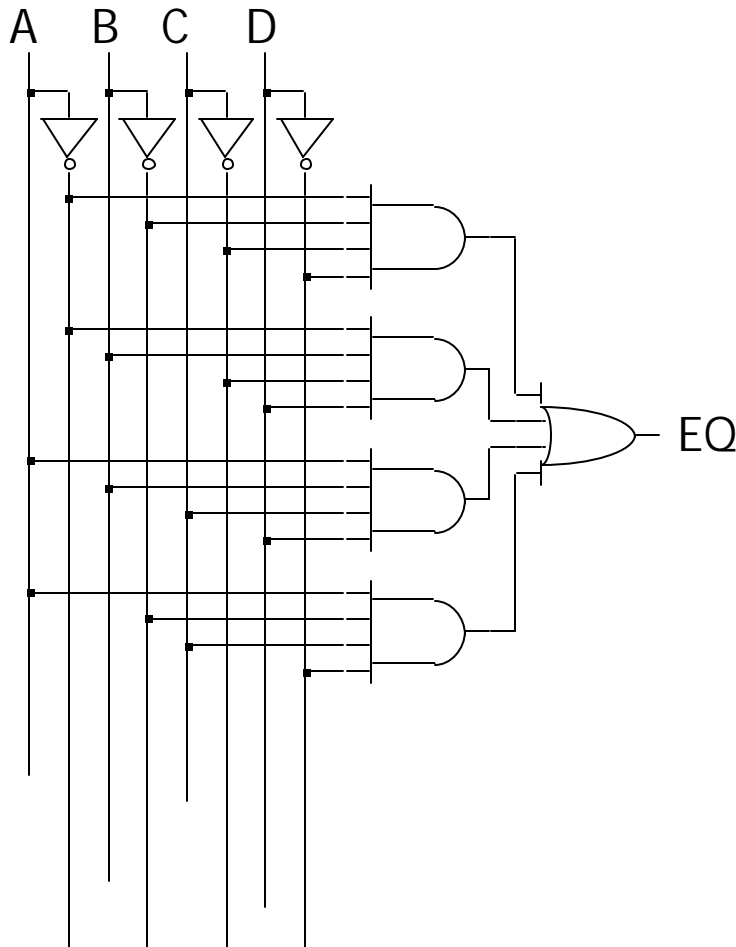

- Step 1: Truth table
- Step 2: K-map
- Step 3: Minimized sum-of-products
- Step 4: Physical implementation with gates

		A		
	1	0	0	0
	0	1	0	0
	0	0	1	0
C	0	0	0	1
		B		

K-map for EQ

September 22, 2003

Karnaugh Maps

- Four variable maps.

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00	0	0	0	1
	01	1	1	0	1
	11	1	1	1	1
	10	1	0	1	1

$$F = A'BC' + A'CD' + ABC + AB'C'D' + ABC' + AB'C$$

$$F = BC' + CD' + AC + AD'$$

- Need to make sure all 1's are covered
- Try to minimize total product terms.
- Design could be implemented using NANDs and NORs

Karnaugh maps: Don't cares


- In some cases, outputs are undefined
- We “don't care” if the logic produces a 0 or a 1
- This knowledge can be used to simplify functions.

		AB		A	
		00	01	11	10
C	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0

- Treat X's like either 1's or 0's
- Very useful
- OK to leave some X's uncovered

Karnaugh maps: Don't cares

 - $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$
 - without don't cares
 - $f =$



A	B	C	D	f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	X
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	X
1	1	0	1	X
1	1	1	0	0
1	1	1	1	0

Don't Care Conditions

- **In some situations, we don't care about the value of a function for certain combinations of the variables.**
 - these combinations may be impossible in certain contexts
 - or the value of the function may not matter in when the combinations occur
- **In such situations we say the function is *incompletely specified* and there are multiple (completely specified) logic functions that can be used in the design.**
 - so we can select a function that gives the simplest circuit
- **When constructing the terms in the simplification procedure, we can choose to either cover or not cover the don't care conditions.**

Map Simplification with Don't Cares

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00	0	1	0	0
	01	x	x	x	1
	11	1	1	1	x
	10	x	0	1	1

$$F = A' C' D + B + AC$$

◦ Alternative covering.

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00	0	1	0	0
	01	x	x	x	1
	11	1	1	1	x
	10	x	0	1	1

$$F = A' B' C' D + ABC' + BC + AC$$

Karnaugh maps: don't cares (cont'd)

◦ $f(A,B,C,D) = \sum m(1,3,5,7,9) + \sum d(6,12,13)$

- $f = A'D + B'C'D$

without don't cares

- $f =$

with don't cares

$$A'D + C'D$$

		A		
	0	0	X	0
	1	1	X	1
	1	1	0	0
C	0	X	0	0
		B		

D

by using don't care as a "1" a 2-cube can be formed rather than a 1-cube to cover this node

don't cares can be treated as 1s or 0s depending on which is more advantageous

Definition of terms for two-level simplification

◦ Implicant

- Single product term of the **ON-set** (terms that create a logic 1)

◦ Prime implicant

- Implicant that can't be combined with another to form an implicant with fewer literals.


◦ Essential prime implicant

- Prime implicant is essential if it alone covers a minterm in the K-map
- Remember that all squares marked with 1 must be covered

◦ Objective:

- Grow implicant into prime implicants (minimize literals per term)
- Cover the K-map with as few prime implicants as possible (minimize number of product terms)

Examples to illustrate terms

 

6 prime implicants:

$A'B'D$, BC' , AC , $A'C'D$, AB , $B'CD$

essential


minimum cover: $AC + BC' + A'B'D$

5 prime implicants:

BD , ABC' , ACD , $A'BC$, $A'C'D$

essential

minimum cover: 4 essential implicants

 


Prime Implicants

Any single 1 or group of 1s in the Karnaugh map of a function F is an implicant of F .

A product term is called a prime implicant of F if it cannot be combined with another term to eliminate a variable.

Example:

 

If a function F is represented by this Karnaugh Map. Which of the following terms are implicants of F , and which ones are prime implicants of F ?

- (a) $AC'D'$
- (b) BD
- (c) $A'B'C'D'$
- (d) AC'
- (e) $B'C'D'$

Implicants:
(a),(c),(d),(e)

Prime Implicants:
(d),(e)

Essential Prime Implicants

A product term is an essential prime implicant if there is a minterm that is only covered by that prime implicant.

- The minimal sum-of-products form of F must include all the essential prime implicants of F .

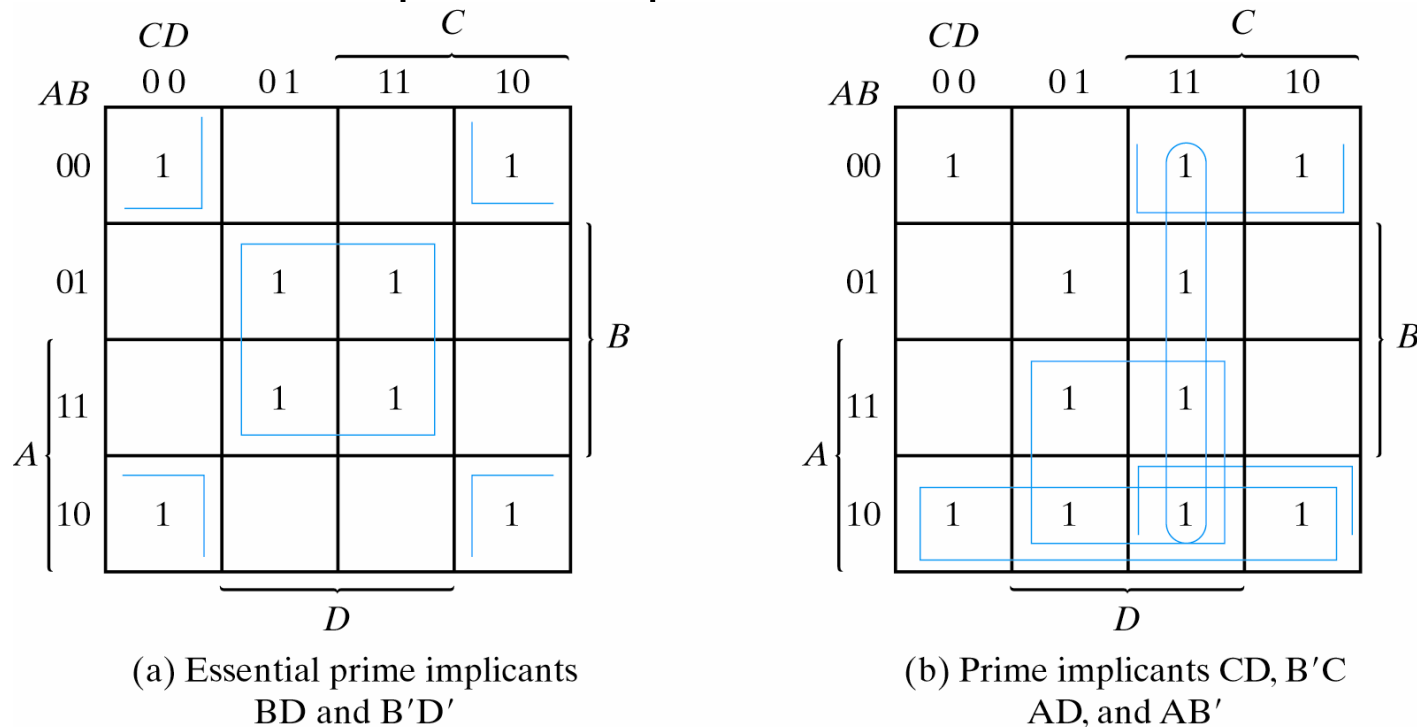


Fig. 3-11 Simplification Using Prime Implicants

Summary

- **K-maps of four literals considered**
 - **Larger examples exist**
- **Don't care conditions help minimize functions**
 - **Output for don't cares are undefined**
- **Result of minimization is minimal sum-of-products**
- **Result contains prime implicants**
- **Essential prime implicants are required in the implementation**