


---

# ENGIN 112

## Intro to Electrical and Computer Engineering

### Lecture 11

### *NAND and XOR Implementations*

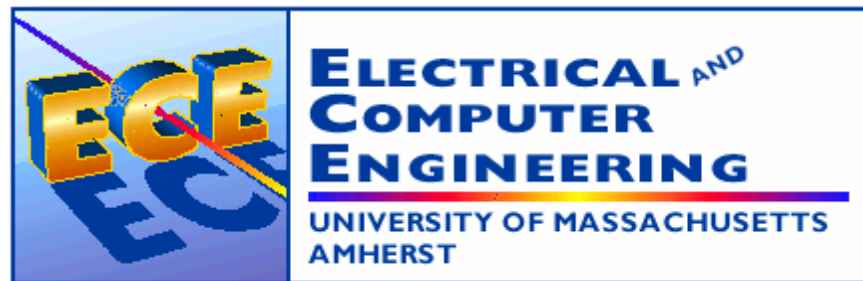

# Overview

---

- **Developing NAND circuits from K-maps**
- **Two-level implementations**
  - Convert from AND/OR to NAND (again!)
- **Multi-level NAND implementations**
  - Convert from a network of AND/ORs
- **Exclusive OR**
  - Comparison with SOP
- **Parity checking and detecting circuitry**
  - Efficient with XOR gates!


# NAND-NAND & NOR-NOR Networks

---

DeMorgan's Law:

$$(a + b)' = a' b' \quad (a b)' = a' + b'$$
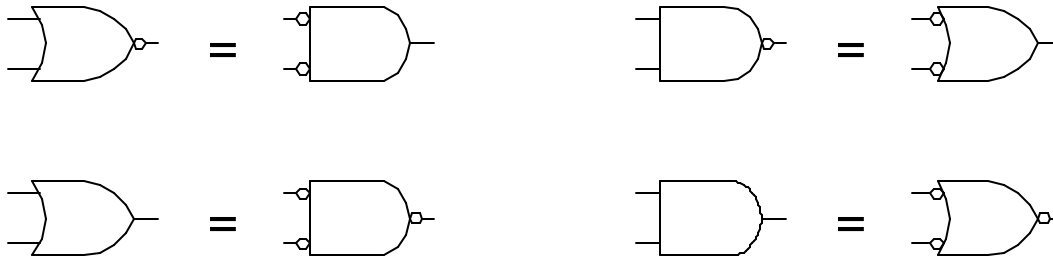
$$a + b = (a' b')' \quad (a b) = (a' + b')'$$







*push bubbles or introduce in pairs or remove pairs.*

# NAND-NAND Networks

---


## ° Mapping from AND/OR to NAND/NAND

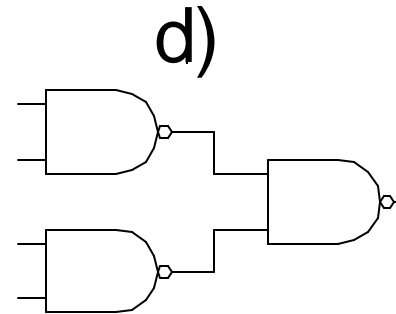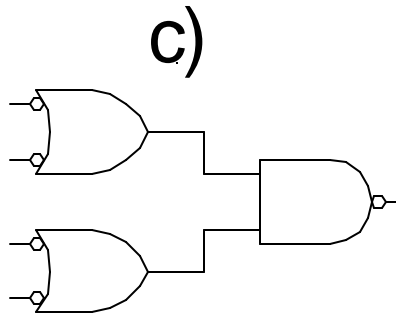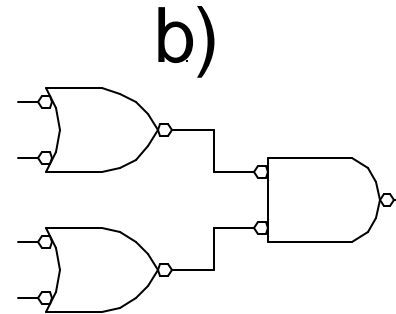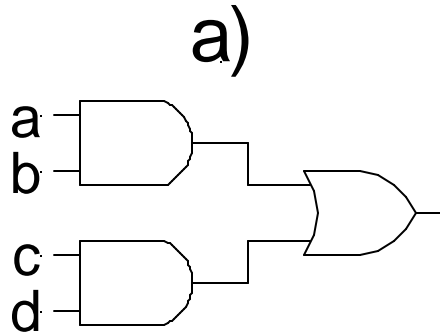

# Implementations of Two-level Logic

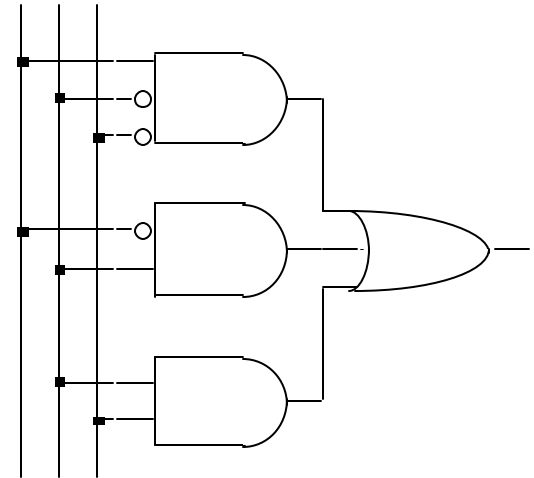
## ◦ Sum-of-products

- AND gates to form product terms (minterms)
- OR gate to form sum


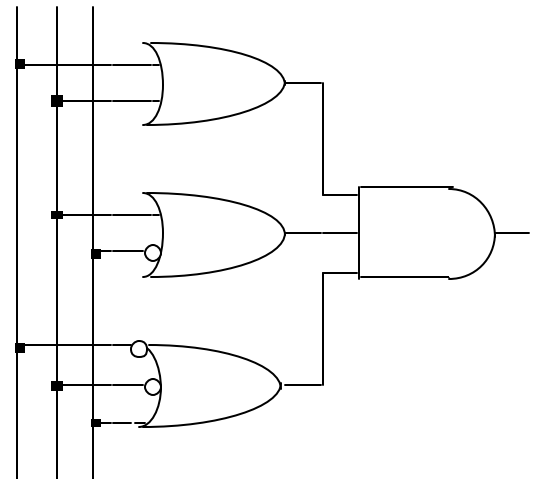
## ◦ Product-of-sums



- OR gates to form sum terms (maxterms)
- AND gates to form product


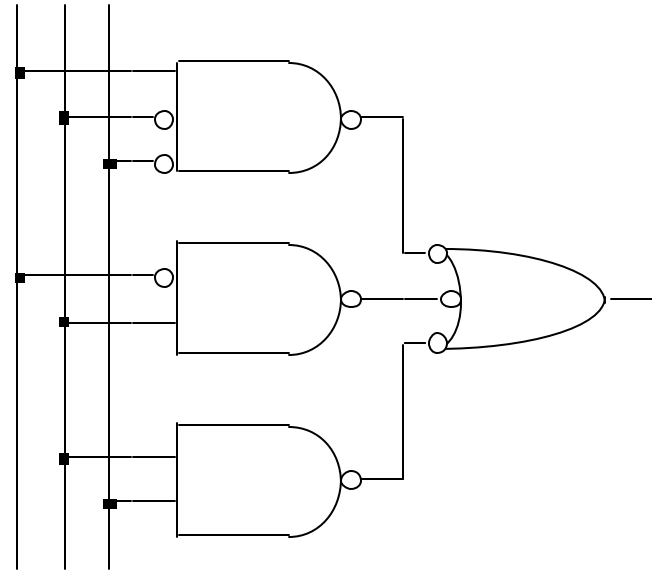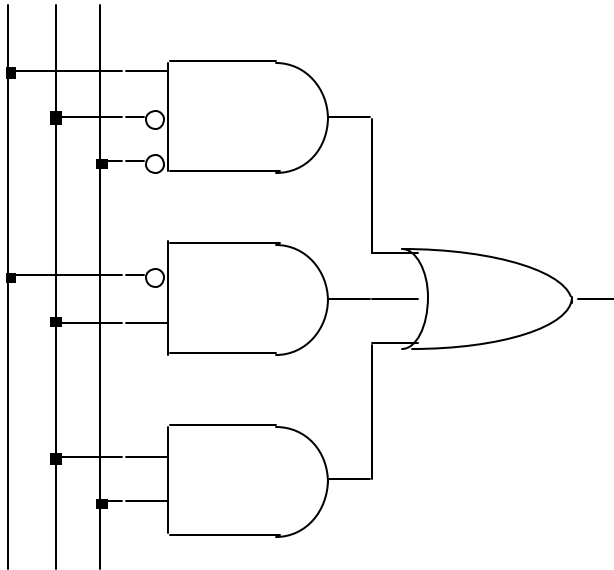
# Two-level Logic using NAND Gates

---

- Replace minterm AND gates with NAND gates
- Place compensating inversion at inputs of OR gate




# Two-level Logic using NAND Gates (cont'd)

- **OR gate with inverted inputs is a NAND gate**

- de Morgan's:  $A' + B' = (A \cdot B)'$



- **Two-level NAND-NAND network**

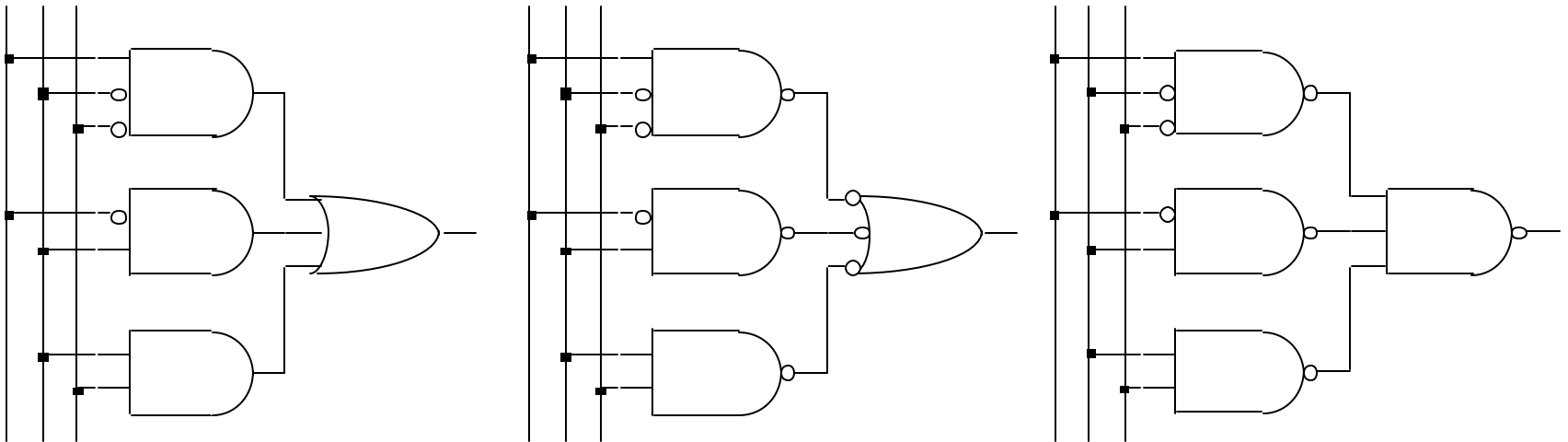- Inverted inputs are not counted
- In a typical circuit, inversion is done once and signal distributed


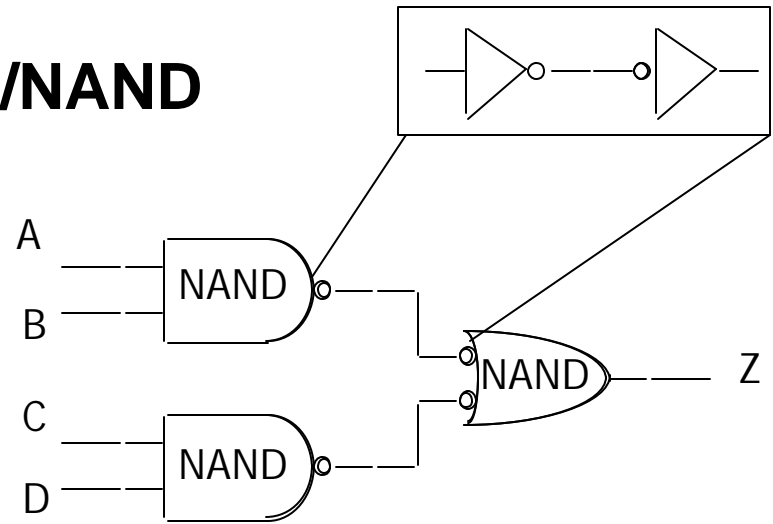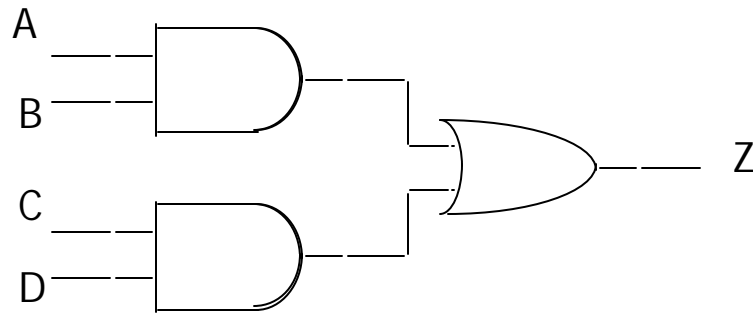
# Conversion Between Forms



- **Convert from networks of ANDs and ORs to networks of NANDs and NORs**
  - Introduce appropriate inversions ("bubbles")
- **Each introduced "bubble" must be matched by a corresponding "bubble"**
  - Conservation of inversions
  - Do not alter logic function
- **Example: AND/OR to NAND/NAND**





# Conversion Between Forms (cont'd)

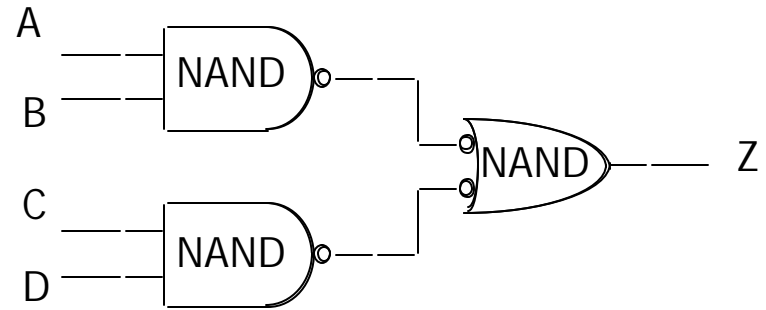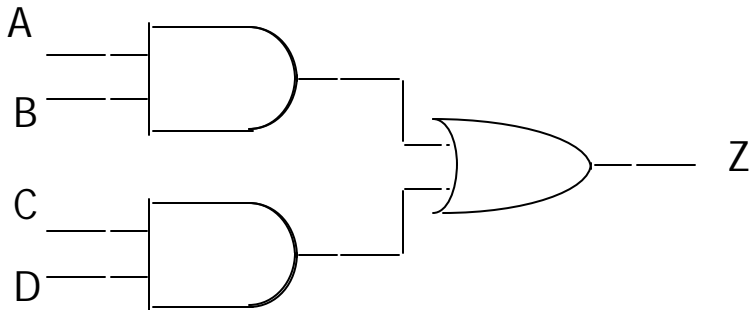
- Example: verify equivalence of two forms




$$\begin{aligned} Z &= [ (A \cdot B)' \cdot (C \cdot D)' ]' \\ &= [ (A' + B') \cdot (C' + D') ]' \\ &= [ (A' + B')' + (C' + D')' ] \\ &= (A \cdot B) + (C \cdot D) \checkmark \end{aligned}$$
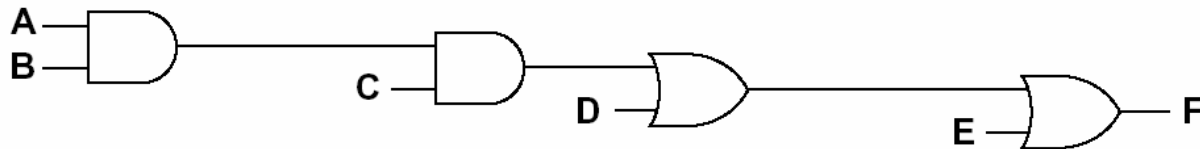
# Conversion to NAND Gates


- Start with SOP (Sum of Products)
  - circle 1s in K-maps
- Find network of OR and AND gates



(a) AND\_OR network

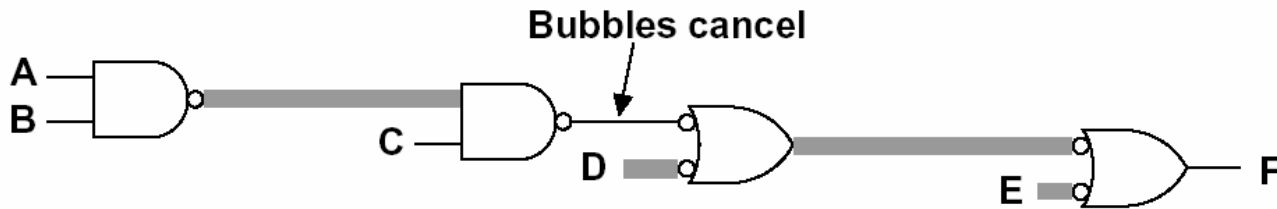


(b) First step in NAND conversion

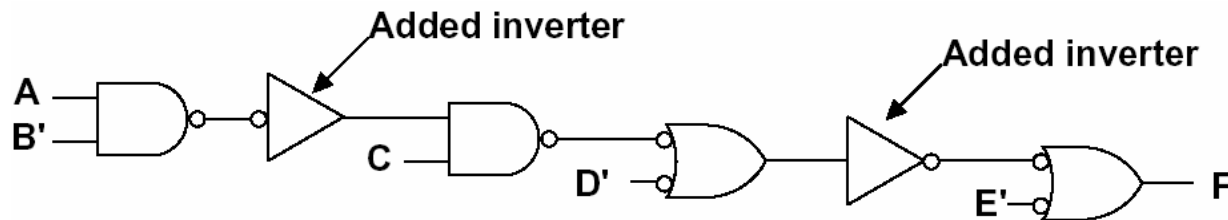

(c) Completed conversion

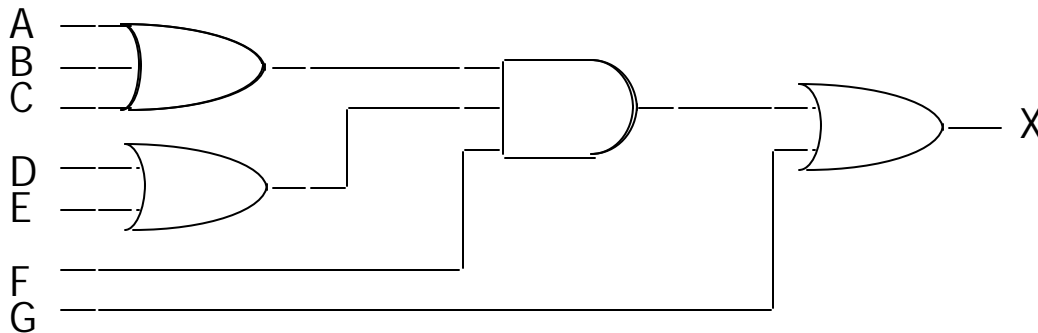
# Multi-level Logic

- $x = A D F + A E F + B D F + B E F + C D F + C E F + G$ 
  - Reduced sum-of-products form – already simplified
  - 6 x 3-input AND gates + 1 x 7-input OR gate (may not exist!)
  - 25 wires (19 literals plus 6 internal wires)
- $x = (A + B + C) (D + E) F + G$ 
  - Factored form – not written as two-level S-o-P
  - 1 x 3-input OR gate, 2 x 2-input OR gates, 1 x 3-input AND gate
  - 10 wires (7 literals plus 3 internal wires)







# Conversion of Multi-level Logic to NAND Gates

°  $F = A (B + C D) + B C'$

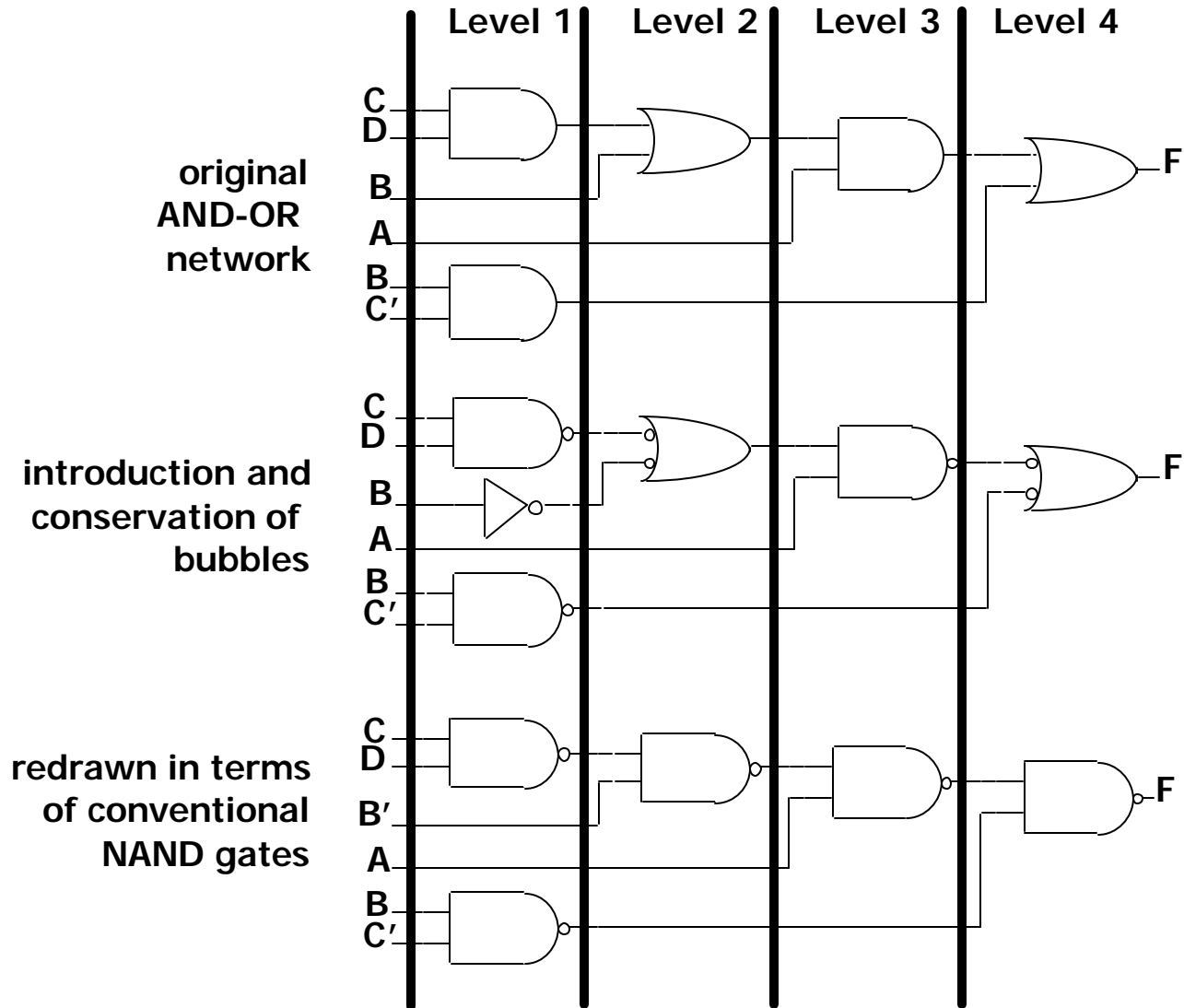


# Conversion Between Forms

## ◦ Example

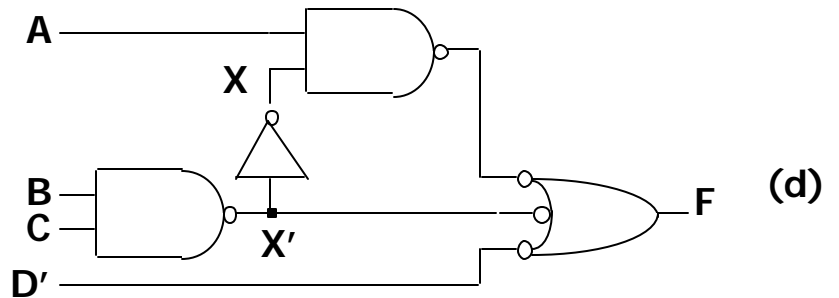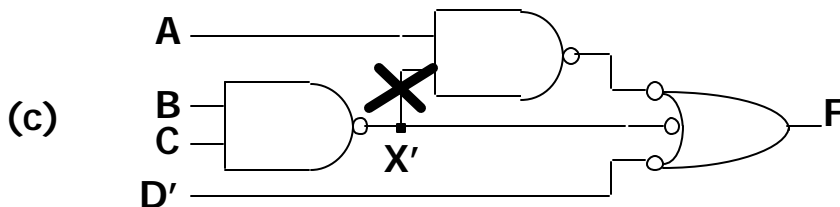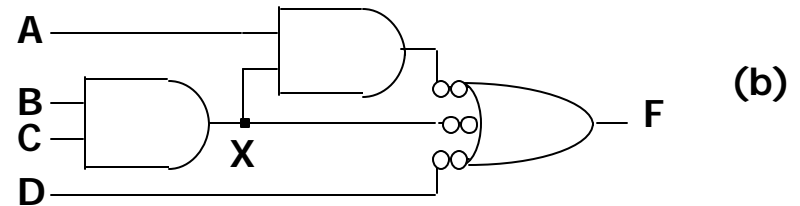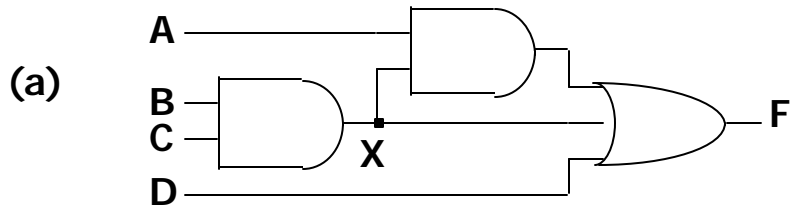


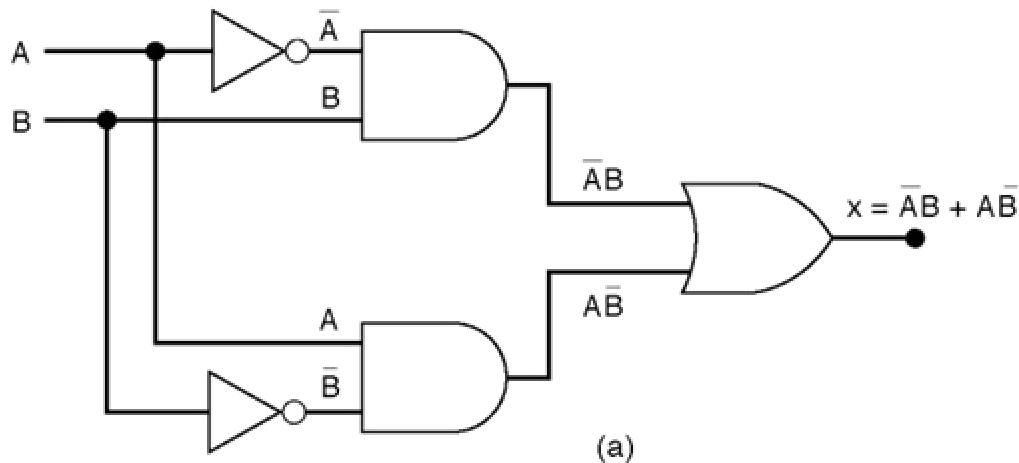
# Exclusive-OR and Exclusive-NOR Circuits

Exclusive-OR (XOR) produces a HIGH output whenever the two inputs are at opposite levels.



A	B	x
0	0	0
0	1	1
1	0	1
1	1	0


XOR gate symbols

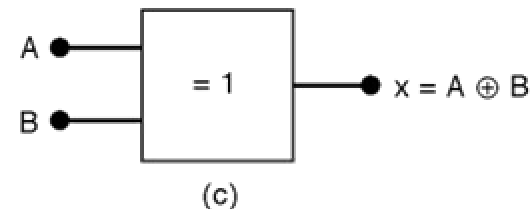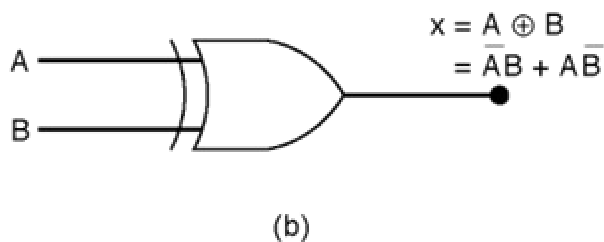

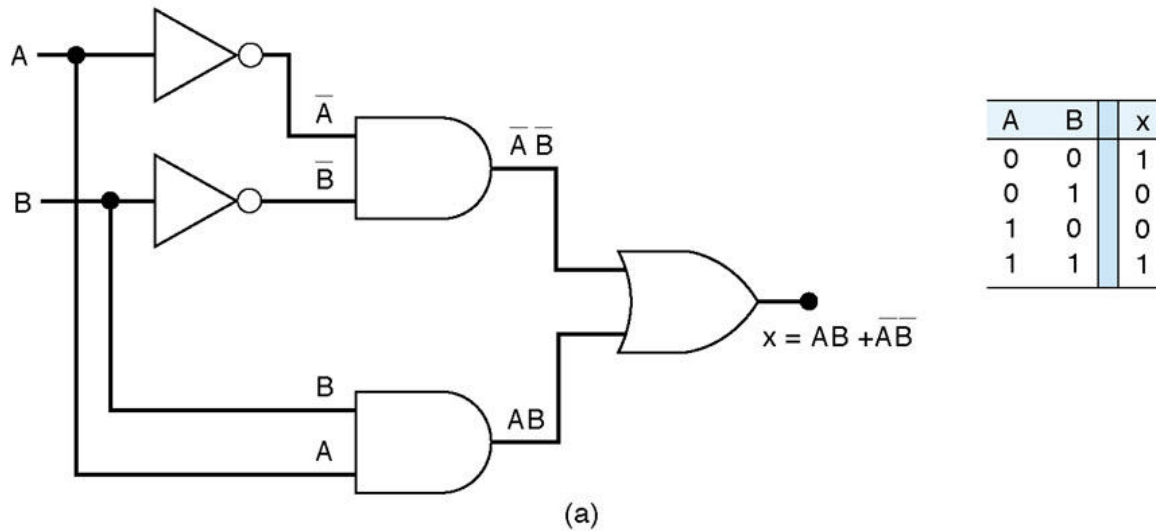
# Exclusive-NOR Circuits

Exclusive-NOR (XNOR) :


Exclusive-NOR (XNOR) produces a HIGH output whenever the two inputs are at the same level.



XNOR gate symbols

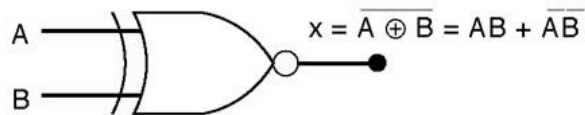


(b)

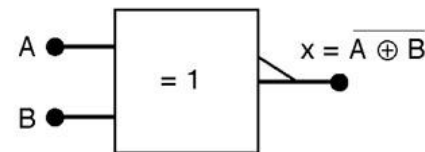


(c)
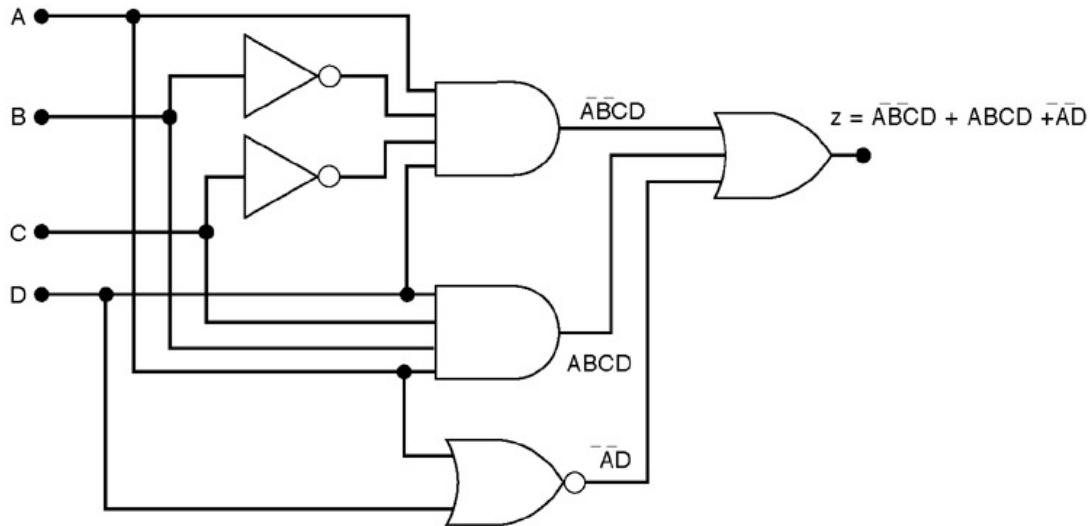
# Exclusive-NOR Circuits

XNOR gate may be used to simplify circuit implementation.



(a)

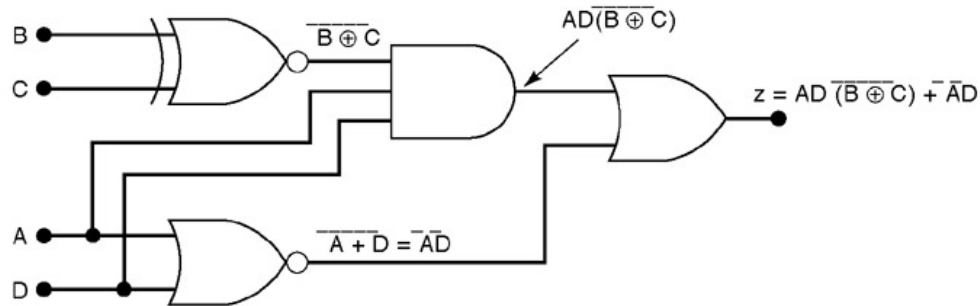


(b)



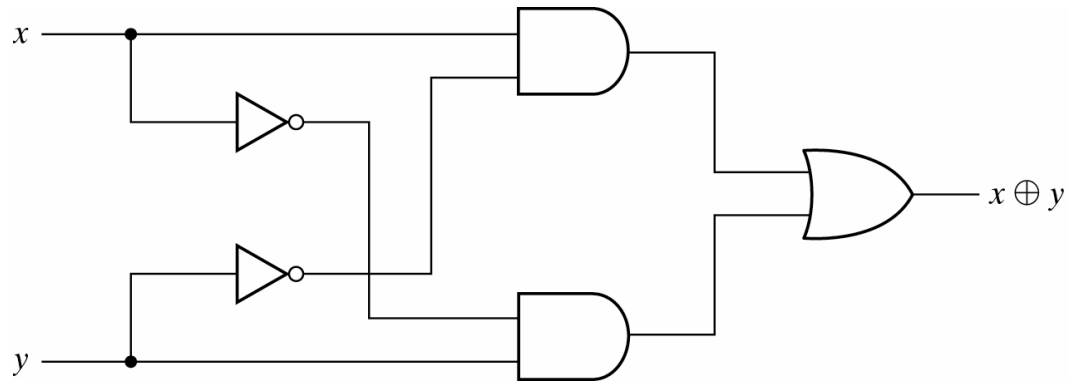
# XOR Function

- XOR function can also be implemented with AND/OR gates (also NANDs).



(a) With AND-OR-NOT gates

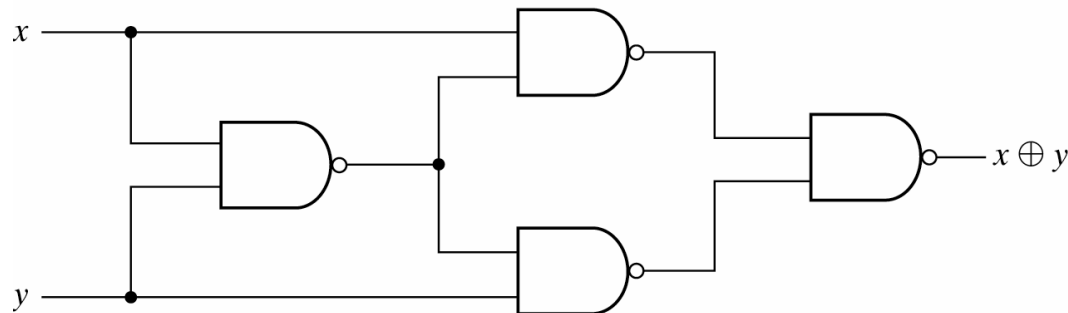

(b) With NAND gates

Fig. 3-32 Exclusive-OR Implementations

# XOR Function

- Even function – even number of inputs are 1.
- Odd function – odd number of inputs are 1.

		BC		B	
		00	01	11	10
A	0		1		1
	1	1		1	

C

(a) Odd function  
 $F = A \oplus B \oplus C$

		BC		B	
		00	01	11	10
A	0	1		1	
	1		1		1


C

(a) Even function  
 $F = (A \oplus B \oplus C)'$

Fig. 3-33 Map for a Three-variable Exclusive-OR Function

# Parity Generation and Checking

**FIGURE 4-25** XOR gates used to implement the parity generator and the parity checker for an even-parity system.

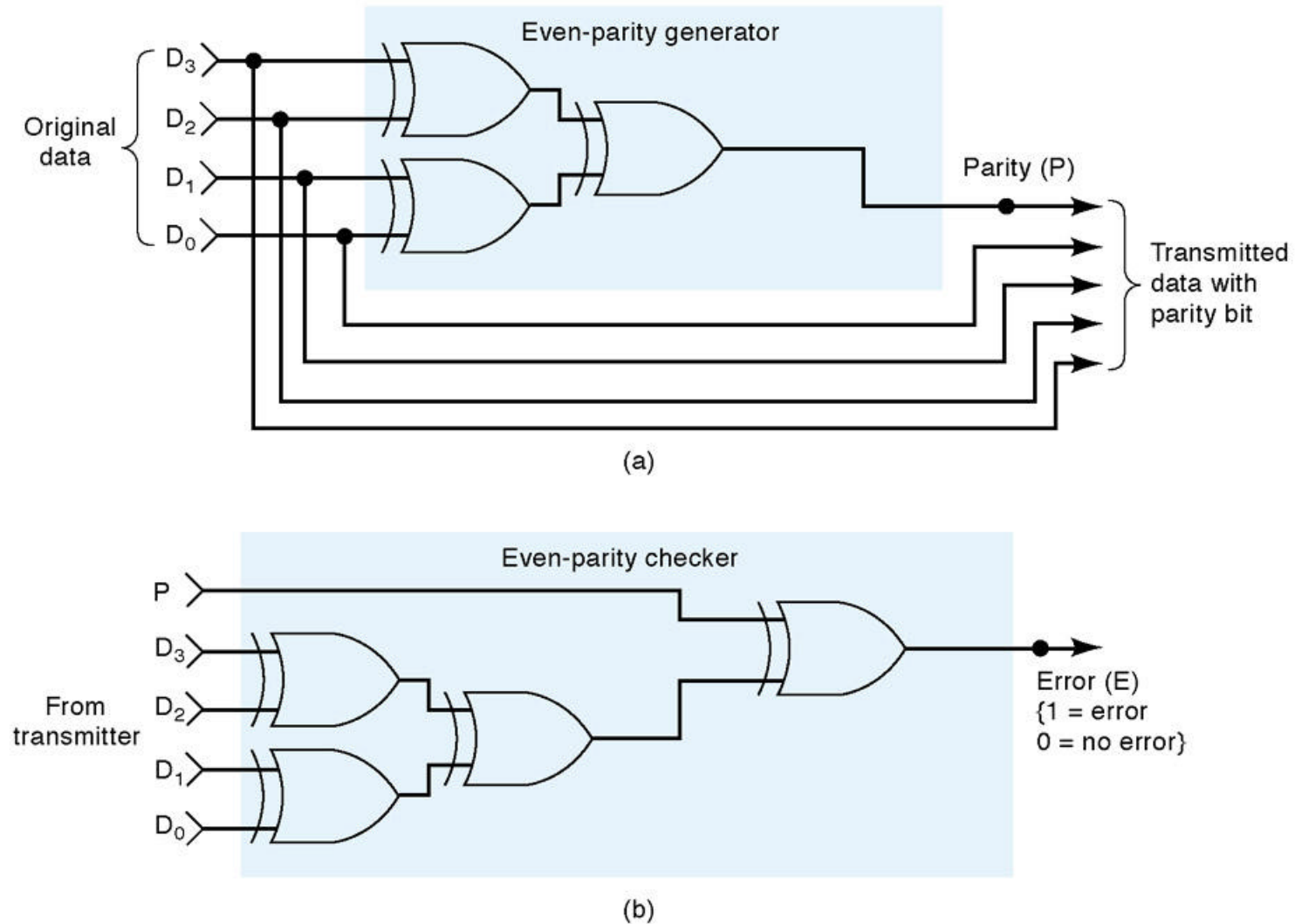

# Summary

---

- Follow rules to convert between AND/OR representation and symbols
- Conversions are based on DeMorgan's Law
- NOR gate implementations are also possible
- XORs provide straightforward implementation for some functions
- Used for parity generation and checking
  - XOR circuits could also be implemented using AND/Ors
- Next time: Hazards