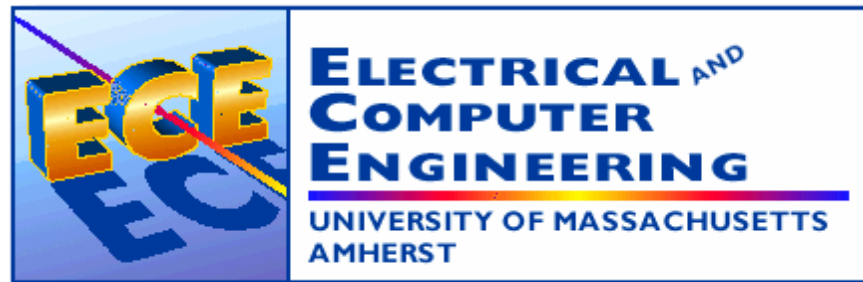


---

# ENGIN 112

## Intro to Electrical and Computer Engineering

### Lecture 13 *Combinational Design Procedure*



# Overview

---

- **Design digital circuit from specification**
- **Digital inputs and outputs known**
  - Need to determine logic that can *transform* data
- **Start in truth table form**
- **Create K-map for each output based on function of inputs**
- **Determine minimized sum-of-product representation**
- **Draw circuit diagram**

# Design Procedure (Mano)

---

## Design a circuit from a specification.

1. Determine number of required inputs and outputs.
2. Derive truth table
3. Obtain simplified Boolean functions
4. Draw logic diagram and verify correctness

$$S = A + B + C$$
$$R = ABC$$

A	B	C	R	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## Previously, we have learned...

---

- **Boolean algebra can be used to simplify expressions, but not obvious:**
  - how to proceed at each step, or
  - if solution reached is minimal.
- **Have seen five ways to represent a function:**
  - Boolean expression
  - truth table
  - logic circuit
  - minterms/maxterms
  - Karnaugh map

# Combinational logic design

---


- **Use multiple representations of logic functions**
- **Use graphical representation to assist in simplification of function.**
- **Use concept of “don’t care” conditions.**
- **Example - encoding BCD to seven segment display.**
- **Similar to approach used by designers in the field.**

## BCD to Seven Segment Display

---

- Used to display binary coded decimal (BCD) numbers using seven illuminated segments.
- BCD uses 0's and 1's to represent decimal digits 0 - 9. Need four bits to represent required 10 digits.
- Binary coded decimal (BCD) represents each decimal digit with four bits

0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
.	.	.	.	.
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

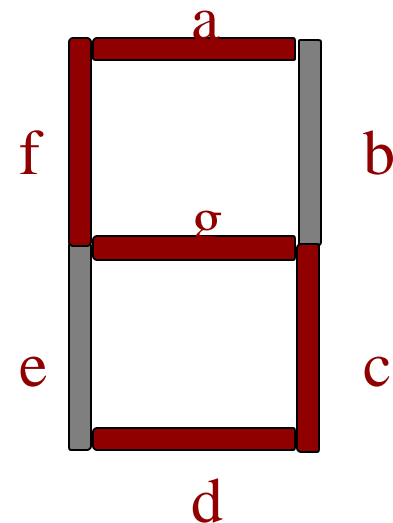


# BCD to seven segment display

---

- List the segments that should be illuminated for each digit.

0	a,b,c,d,e,f
1	b,c
2	a,b,d,e,g
3	a,b,c,d,g
4	b,c,f,g
5	a,c,d,f,g
6	a,c,d,e,f,g
7	a,b,c
8	a,b,c,d,e,f,g
9	a,b,c,d,f,g

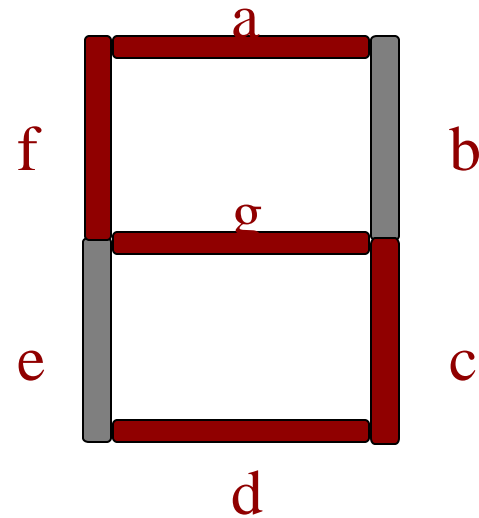

# BCD to seven segment display

---

- Derive the truth table for the circuit.
- Each output column in one circuit.

Dec	Inputs				Outputs					
	w	x	y	z	a	b	c	d	e	.
0	0	0	0	0	1	1	1	1	1	.
1	0	0	0	1	0	1	1	0	0	.
2	0	0	1	0	1	1	0	1	1	.
.	.	.	.	.	.	.	.	.	.	.
7	0	1	1	1	1	1	1	0	0	.
8	1	0	0	0	1	1	1	1	1	.
9	1	0	0	1	1	1	1	1	0	.



# BCD to seven segment display

---

- Find minimal sum-of-products representation for each **output**

For segment “a” :

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11				
	10	1	1		

Note: Have only filled in ten squares, corresponding to the ten numerical digits we wish to represent.

## Don't care conditions (BCD display) ...

---

- Fill in don't cares for **undefined** outputs.
  - Note that these combinations of inputs should never happen.
- Leads to a reduced implementation

For segment “a” :

wx \ yz	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

Put in “X” (don't care), and interpret as either 1 or 0 as desired ....

## Don't care conditions (BCD display) ...

- Circle biggest group of 1's and Don't Cares.
- Leads to a reduced implementation

For segment “a” :

wx \ yz	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

$$F_{a1} = y$$

# Don't care conditions (BCD display)

---

- Circle biggest group of 1's and Don't Cares.
- Leads to a reduced implementation

For segment “a” :

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

$$F_{a2} = w$$

# Don't care conditions (BCD display) ...

- Circle biggest group of 1's and Don't Cares.
- All 1's should be covered by at least one implicant

For segment "a" :

wx \ yz	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

$$F_{a3} = \overline{xz}$$

wx \ yz	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

$$F_{a4} = xz$$

## Don't care conditions (BCD display) ...


- Put all the terms together
- Generate the circuit

For segment “a” :

		yz			
		00	01	11	10
wx	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

$$F = y + w + \overline{\overline{xz}} + xz$$
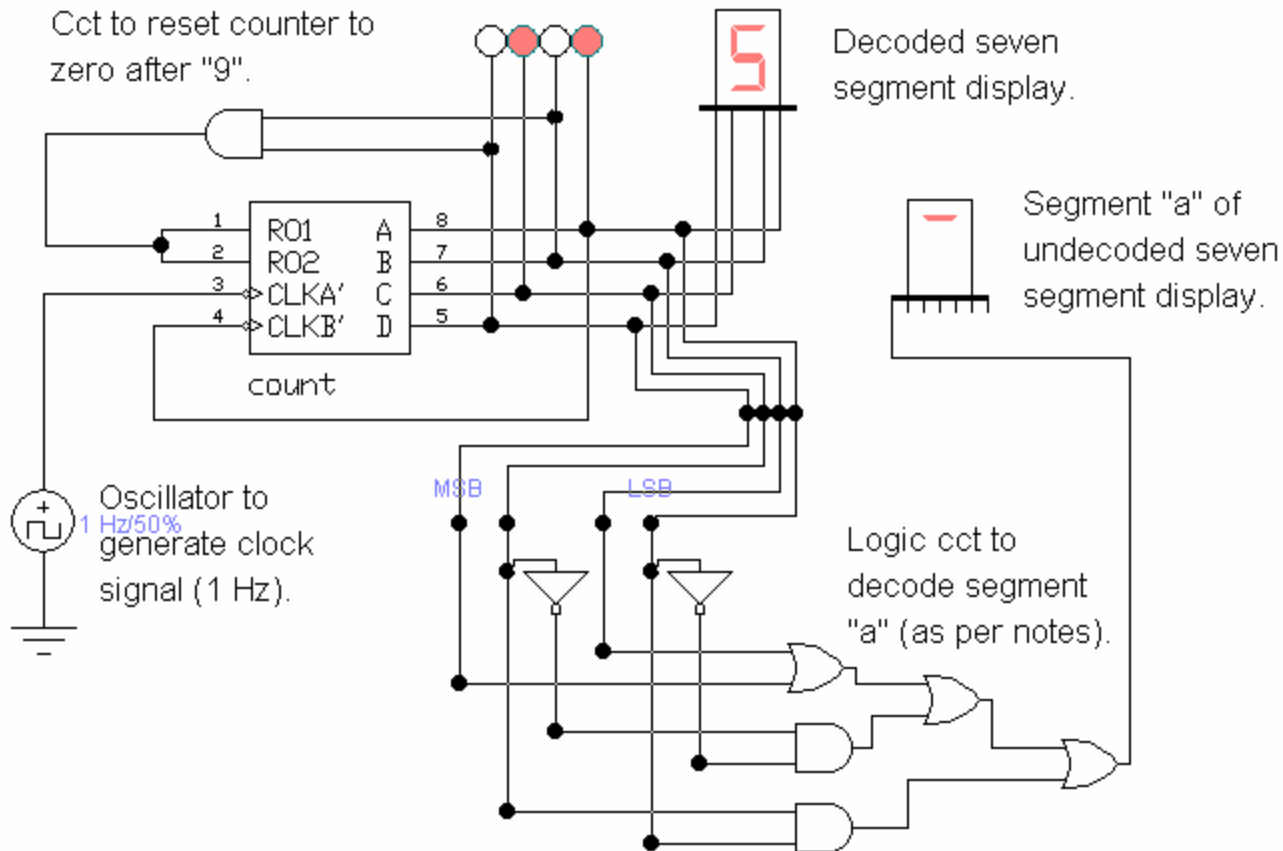
## Example of seven segment display decoding.



Hint: Select a component and then push "?" from main menu bar to get info on what that component does and how it works.

# BCD to seven segment display

---

- Derive the truth table for the circuit.
- Each output column in one circuit.

Dec	Inputs				Outputs					
	w	x	y	z	a	b	c	d	e	.
0	0	0	0	0	1	1	1	1	1	.
1	0	0	0	1	0	1	1	0	0	.
2	0	0	1	0	1	1	0	1	1	.
.	.	.	.	.	.	.	.	.	.	.
7	0	1	1	1	1	1	1	0	0	.
8	1	0	0	0	1	1	1	1	1	.
9	1	0	0	1	1	1	1	1	0	.



# BCD to seven segment display

---

- Find minimal sum-of-products representation for each **output**

For segment “b” :

		yz			
		00	01	11	10
wx	00	1	1	1	1
	01	1	0	1	0
	11				
	10	1	1		

See if you complete this example.

# Summary

---

- **Need to formulate circuits from problem descriptions**
  1. Determine number of inputs and outputs
  2. Determine truth table format
  3. Determine K-map
  4. Determine minimal SOP
- **There may be multiple outputs per design**
  - Solve each output separately
- **Current approach doesn't have **memory**.**
  - This will be covered next week.