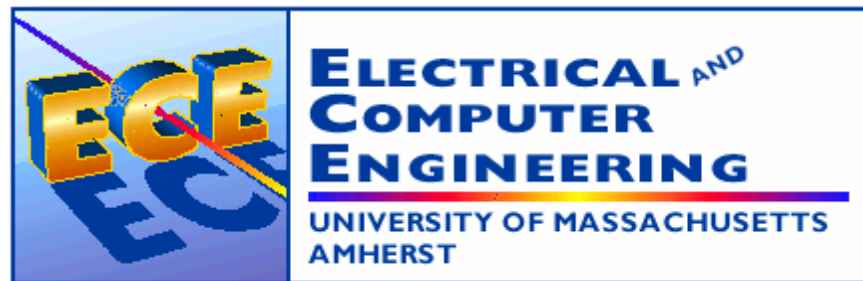

ENGIN 112

Intro to Electrical and Computer Engineering

Lecture 15

Magnitude Comparators and Multiplexers




Overview


- **Discussion of two digital building blocks**
- **Magnitude comparators**
 - Compare two multi-bit binary numbers
 - Create a single bit comparator
 - Use repetitive pattern
- **Multiplexers**
 - Select one out of several bits
 - Some inputs used for selection
 - Also can be used to implement logic

Magnitude Comparator

 - **The comparison of two numbers**
 - outputs: $A > B$, $A = B$, $A < B$
- **Design Approaches**
 - the truth table
 - 2^{2n} entries - too cumbersome for large n
 - use inherent regularity of the problem
 - reduce design efforts
 - reduce human errors



Magnitude Comparator

 


How can we find $A > B$?

How many rows would a truth table have?

$$2^8 = 256$$

Magnitude Comparator

 

Find $A > B$

If $A = 1001$ and
 $B = 0111$
is $A > B$?

Why?

Because $A_3 > B_3$
i.e. $A_3 \cdot B_3' = 1$

Therefore, one term in the
logic equation for $A > B$ is
 $A_3 \cdot B_3'$

Magnitude Comparator

If $A = 1010$ and

$B = 1001$

is $A > B$?

Why?

$$A > B = A_3 \cdot B_3'$$

$$+ C_3 \cdot A_2 \cdot B_2'$$

$$+ \dots$$

Because $A_3 = B_3$ and

$A_2 = B_2$ and

$A_1 > B_1$

i.e. $C_3 = 1$ and $C_2 = 1$ and


$$A_1 \cdot B_1' = 1$$

Therefore, the next term in the logic equation for $A > B$ is

$$C_3 \cdot C_2 \cdot A_1 \cdot B_1'$$

Magnitude Comparison

- **Algorithm -> logic**
 - $A = A_3A_2A_1A_0$; $B = B_3B_2B_1B_0$
 - $A=B$ if $A_3=B_3$, $A_2=B_2$, $A_1=B_1$ and $A_0=B_0$
- **Test each bit:**
 - equality: $x_i = A_iB_i + A_i'B_i'$
 - $(A=B) = x_3x_2x_1x_0$
- **More difficult to test less than/greater than**
 - $(A>B) = A_3B_3' + x_3A_2B_2' + x_3x_2A_1B_1' + x_3x_2x_1A_0B_0'$
 - $(A<B) = A_3'B_3 + x_3A_2'B_2 + x_3x_2A_1'B_1 + x_3x_2x_1A_0'B_0$
 - Start comparisons from **high-order** bits
- **Implementation**
 - $x_i = (A_iB_i' + A_i'B_i)'$

 


TRUTH TABLE

COMPARING INPUTS				CASCADING INPUTS			OUTPUTS		
A ₃ , B ₃	A ₂ , B ₂	A ₁ , B ₁	A ₀ , B ₀	I _{A>B}	I _{A<B}	I _{A=B}	O _{A>B}	O _{A<B}	O _{A=B}
A ₃ > B ₃	X	X	X	X	X	X	H	L	L
A ₃ < B ₃	X	X	X	X	X	X	L	H	L
A ₃ = B ₃	A ₂ > B ₂	X	X	X	X	X	H	L	L
A ₃ = B ₃	A ₂ < B ₂	X	X	X	X	X	L	H	L
A ₃ = B ₃	A ₂ = B ₂	A ₁ > B ₁	X	X	X	X	H	L	L
A ₃ = B ₃	A ₂ = B ₂	A ₁ < B ₁	X	X	X	X	L	H	L
A ₃ = B ₃	A ₂ = B ₂	A ₁ = B ₁	A ₀ > B ₀	X	X	X	H	L	L
A ₃ = B ₃	A ₂ = B ₂	A ₁ = B ₁	A ₀ < B ₀	X	X	X	L	H	L
A ₃ = B ₃	A ₂ = B ₂	A ₁ = B ₁	A ₀ = B ₀	H	L	L	H	L	L
A ₃ = B ₃	A ₂ = B ₂	A ₁ = B ₁	A ₀ = B ₀	L	H	L	L	H	L
A ₃ = B ₃	A ₂ = B ₂	A ₁ = B ₁	A ₀ = B ₀	X	X	H	L	L	H
A ₃ = B ₃	A ₂ = B ₂	A ₁ = B ₁	A ₀ = B ₀	L	L	L	H	H	L
A ₃ = B ₃	A ₂ = B ₂	A ₁ = B ₁	A ₀ = B ₀	H	H	L	L	L	L

H = HIGH Voltage Level
L = LOW Voltage Level
X = Immaterial


Magnitude Comparator

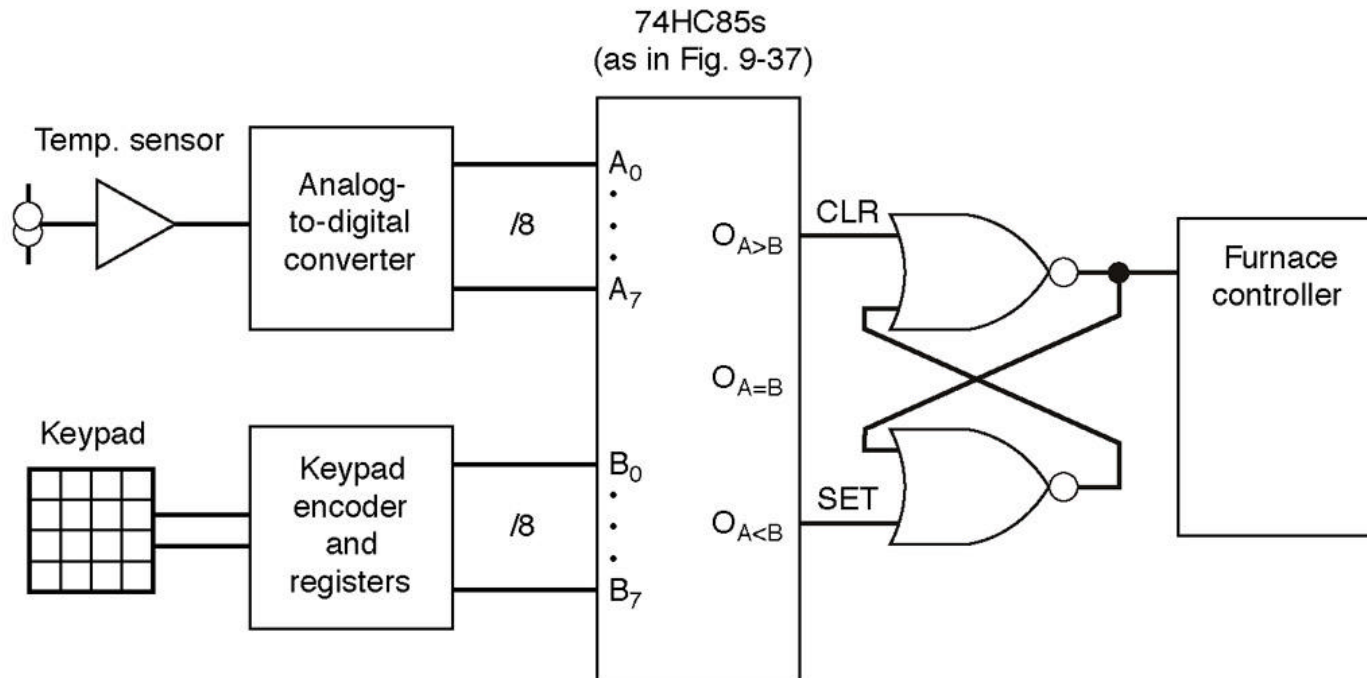- Real-world application
 - Thermostat controller




Multiplexers

 - Select an input value with one or more select bits
- Use for transmitting data
- Allows for **conditional** transfer of data
- Sometimes called a **mux**




(a) Logic diagram

 


(b) Block diagram

Fig. 4-24 2-to-1-Line Multiplexer

4-to-1-Line Multiplexer

 

Quadruple 2-to-1-Line Multiplexer

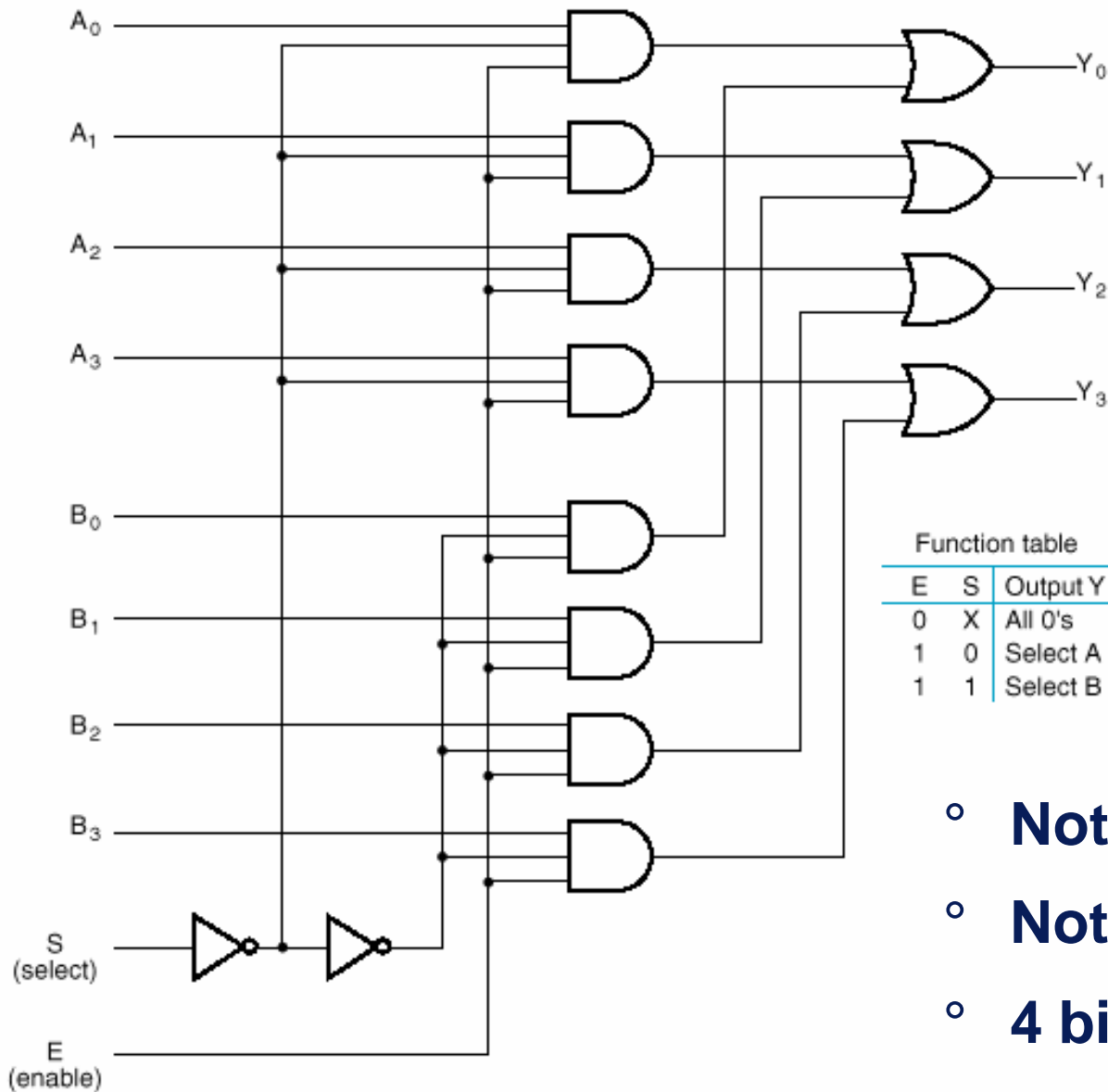


- Notice enable bit
- Notice select bit
- 4 bit inputs

Multiplexer as combinational modules

- Connect input variables to select inputs of multiplexer ($n-1$ for n variables)
- Set data inputs to multiplexer equal to values of function for corresponding assignment of select variables
- Using a variable at data inputs reduces size of the multiplexer

x	y	z	F	
0	0	0	0	
0	0	1	1	$F = z$
0	1	0	1	
0	1	1	0	$F = z'$
1	0	0	0	
1	0	1	0	$F = 0$
1	1	0	1	
1	1	1	1	$F = 1$

(a) Truth table

 


(b) Multiplexer implementation

Fig. 4-27 Implementing a Boolean Function with a Multiplexer

Implementing a Four- Input Function with a Multiplexer

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = \bar{D}$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

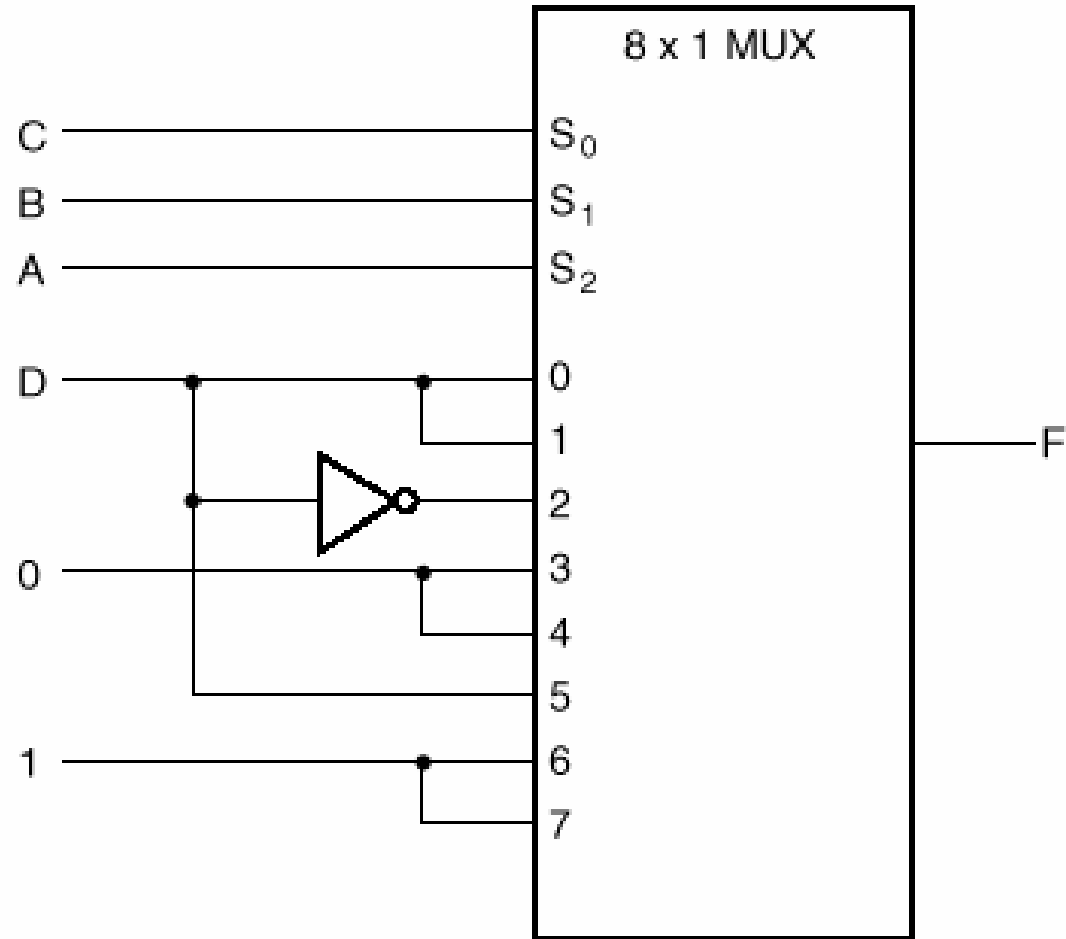

Typical multiplexer uses


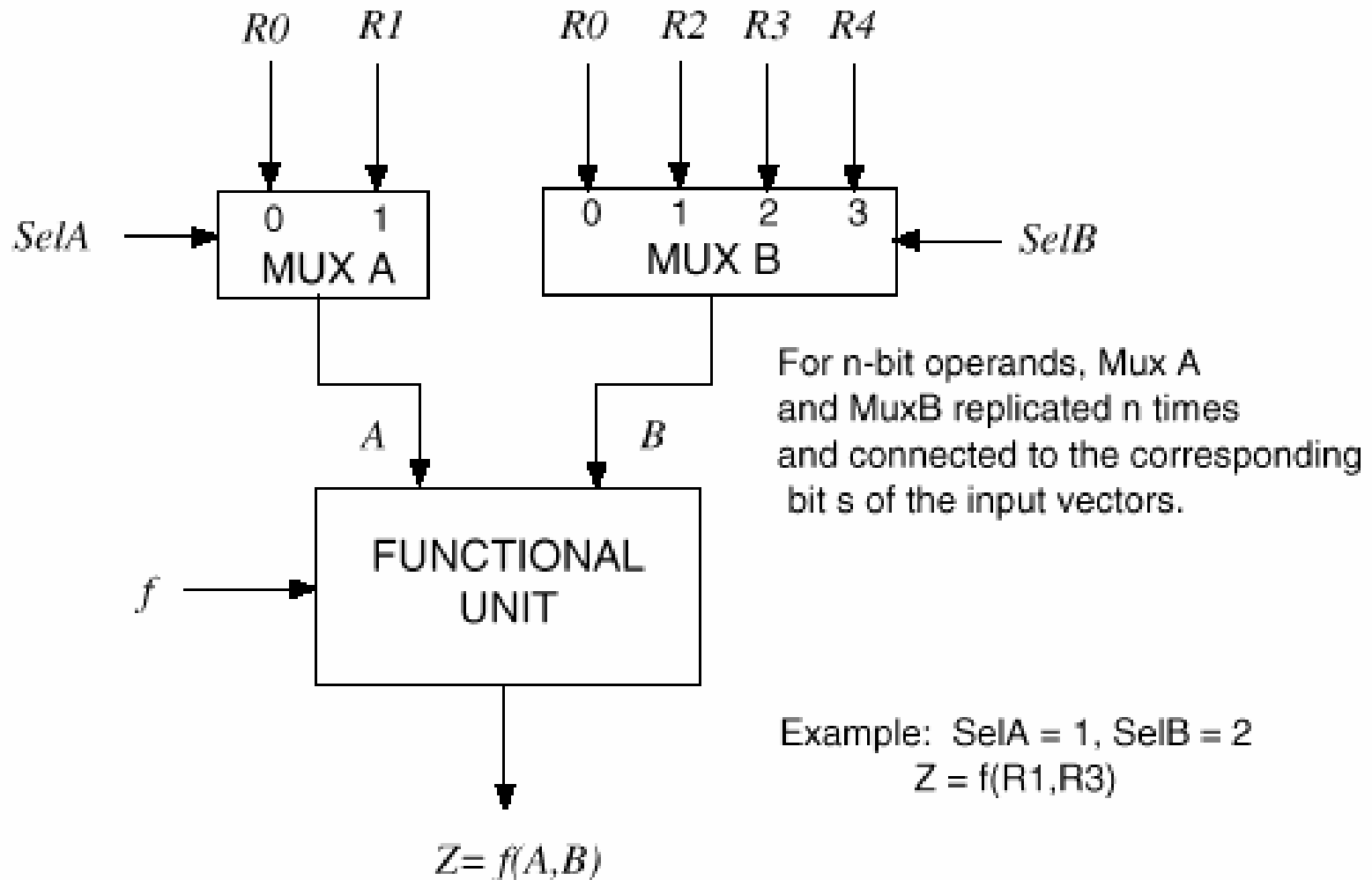
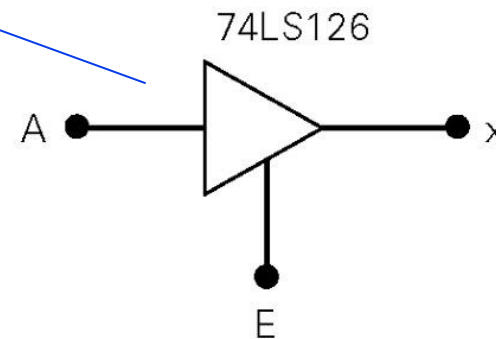


Figure 9.21: Multiplexer example of use.

Three-state gates

 - A multiplexer can be constructed with three-state gates
- Output state: 0, 1, and high-impedance (open ckts)
- If the select input (E) is 0, the three-state gate has **no output**



Opposite true here,
No output if \bar{E} is 1

\bar{E}	x
0	A
1	Hi-Z


(a)

E	x
0	Hi-Z
1	A


(b)

Three-state gates

 - A multiplexer can be constructed with three-state gates
- Output state: 0, 1, and high-impedance (open ckts)
- If the select input is low, the three-state gate has **no output**



(a) 2-to-1- line mux

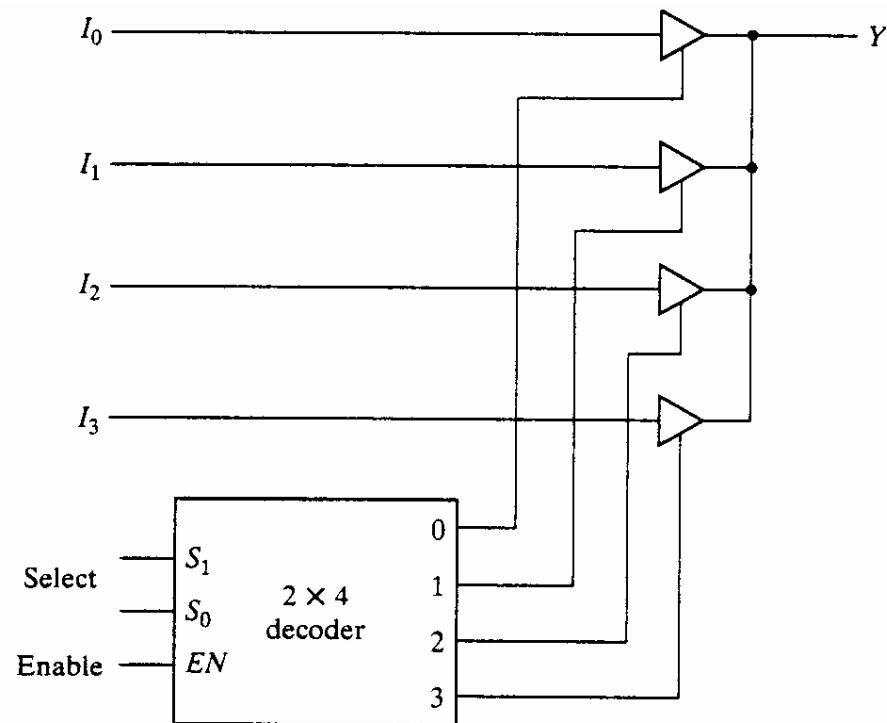

(b) 4 - to - 1 line mux

Summary

- **Magnitude comparators allow for data comparison**
 - Can be built using and-or gates
- **Greater/less than requires more hardware than equality**
- **Multiplexers are fundamental digital components**
 - Can be used for logic
 - Useful for **datapaths**
 - Scalable
- **Tristate buffers have three types of outputs**
 - 0, 1, high-impedance (Z)
 - Useful for datapaths