 


---

# ENGIN 112

## Intro to Electrical and Computer Engineering

### Lecture 17 *Encoders and Decoders*



# Overview

---

## ◦ Binary decoders

- Converts an n-bit code to a single active output
- Can be developed using AND/OR gates
- Can be used to implement logic circuits.

## ◦ Binary encoders


- Converts one of  $2^n$  inputs to an n-bit output
- Useful for compressing data
- Can be developed using AND/OR gates

## ◦ Both encoders and decoders are extensively used in digital systems
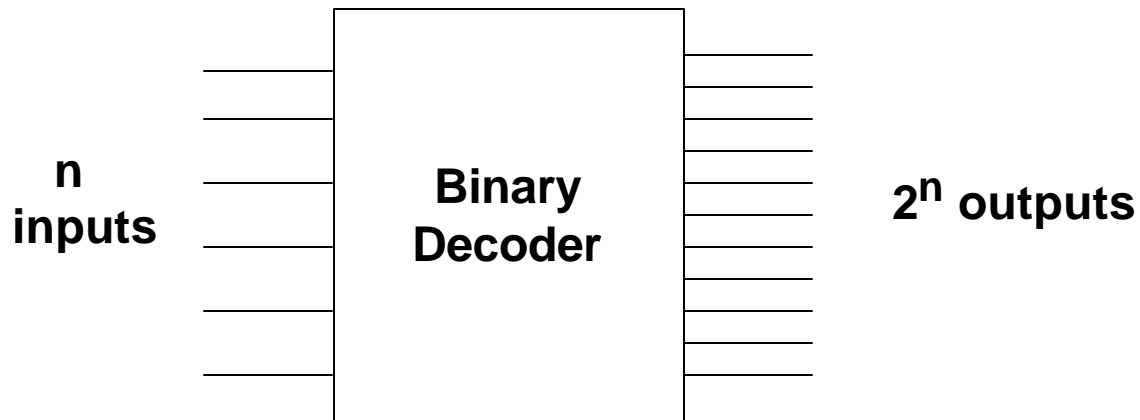
# Binary Decoder

---

- **Black box with  $n$  input lines and  $2^n$  output lines**
- **Only one output is a 1 for any given input**





# 2-to-4 Binary Decoder

## Truth Table:

| X | Y | F <sub>0</sub> | F <sub>1</sub> | F <sub>2</sub> | F <sub>3</sub> |
|---|---|----------------|----------------|----------------|----------------|
| 0 | 0 | 1              | 0              | 0              | 0              |
| 0 | 1 | 0              | 1              | 0              | 0              |
| 1 | 0 | 0              | 0              | 1              | 0              |
| 1 | 1 | 0              | 0              | 0              | 1              |

 
 
- From truth table, circuit for 2x4 decoder is:
- Note: Each output is a 2-variable minterm ( $X'Y'$ ,  $X'Y$ ,  $XY'$  or  $XY$ )



# 3-to-8 Binary Decoder

## Truth Table:

| x | y | z | F <sub>0</sub> | F <sub>1</sub> | F <sub>2</sub> | F <sub>3</sub> | F <sub>4</sub> | F <sub>5</sub> | F <sub>6</sub> | F <sub>7</sub> |
|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 1              | 0              | 0              | 0              | 0              | 0              | 0              | 0              |
| 0 | 0 | 1 | 0              | 1              | 0              | 0              | 0              | 0              | 0              | 0              |
| 0 | 1 | 0 | 0              | 0              | 1              | 0              | 0              | 0              | 0              | 0              |
| 0 | 1 | 1 | 0              | 0              | 0              | 1              | 0              | 0              | 0              | 0              |
| 1 | 0 | 0 | 0              | 0              | 0              | 0              | 1              | 0              | 0              | 0              |
| 1 | 0 | 1 | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0              |
| 1 | 1 | 0 | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0              |
| 1 | 1 | 1 | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 1              |

  

## Implementing Functions Using Decoders

---

- **Any  $n$ -variable logic function can be implemented using a single  $n$ -to- $2^n$  decoder to generate the minterms**
  - OR gate forms the sum.
  - The output lines of the decoder corresponding to the minterms of the function are used as inputs to the or gate.
- **Any combinational circuit with  $n$  inputs and  $m$  outputs can be implemented with an  $n$ -to- $2^n$  decoder with  $m$  OR gates.**
- **Suitable when a circuit has many outputs, and each output function is expressed with few minterms.**


# Implementing Functions Using Decoders

## ◦ Example: Full adder


$$S(x, y, z) = \sum (1, 2, 4, 7)$$

$$C(x, y, z) = \sum (3, 5, 6, 7)$$

| x | y | z | C | S |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

 


## 74138 (3-to-8 decoder)

 

(a)

(a) Logic circuit.

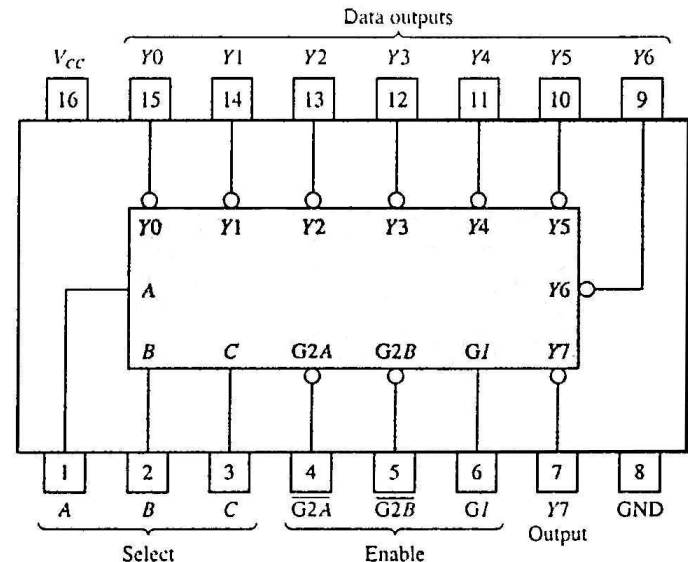

(b)

(b) Package pin configuration.

| Inputs |                   |       | Outputs |    |    |    |    |    |    |    |
|--------|-------------------|-------|---------|----|----|----|----|----|----|----|
| Enable | Select            |       | Y0      | Y1 | Y2 | Y3 | Y4 | Y5 | Y6 | Y7 |
| G1     | $\overline{G2}^*$ | C B A |         |    |    |    |    |    |    |    |
| H      | L                 | L L L | L       | H  | H  | H  | H  | H  | H  | H  |
| H      | L                 | L L H | H       | L  | H  | H  | H  | H  | H  | H  |
| H      | L                 | L H L | H       | H  | L  | H  | H  | H  | H  | H  |
| H      | L                 | L H H | H       | H  | H  | L  | H  | H  | H  | H  |
| H      | L                 | H L L | H       | H  | H  | H  | L  | H  | H  | H  |
| H      | L                 | H L H | H       | H  | H  | H  | H  | L  | H  | H  |
| H      | L                 | H H L | H       | H  | H  | H  | H  | H  | L  | H  |
| H      | L                 | H H H | H       | H  | H  | H  | H  | H  | H  | L  |
| x      | H                 | x x x | H       | H  | H  | H  | H  | H  | H  | H  |
| L      | x                 | x x x | H       | H  | H  | H  | H  | H  | H  | H  |

$$\overline{G2}^* = \overline{G2A} + \overline{G2B}$$

(c)

(c) Function table.




# Building a Binary Decoder with NAND Gates

- Start with a 2-bit decoder
  - Add an enable signal (E)

**Note: use of NANDs**

**only one 0 active!**

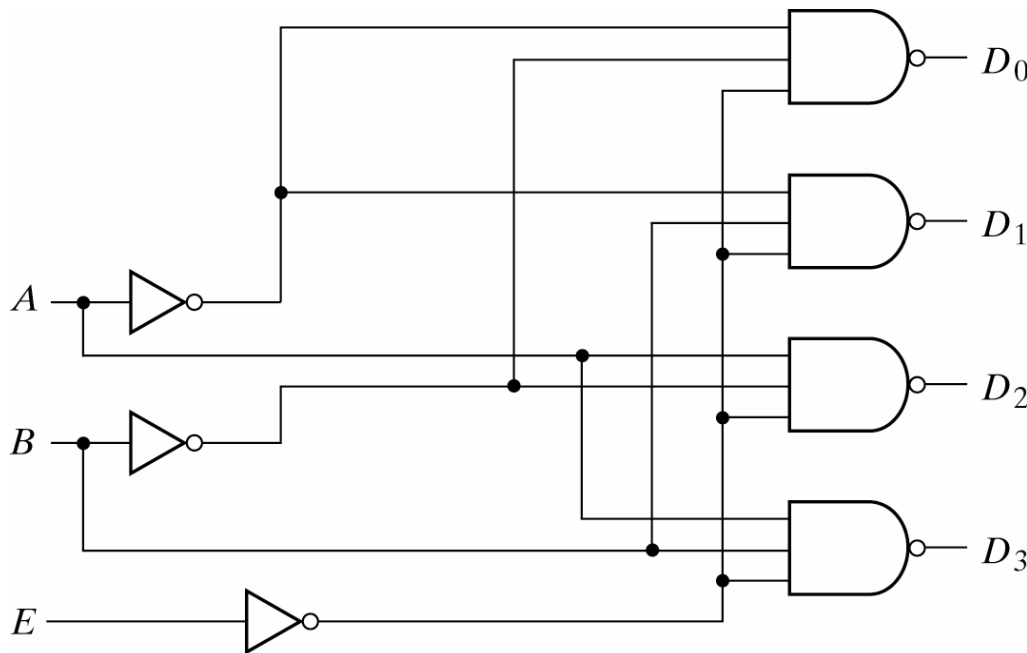

(a) Logic diagram

**if E = 0**

| <i>E</i> | <i>A</i> | <i>B</i> | <i>D</i> <sub>0</sub> | <i>D</i> <sub>1</sub> | <i>D</i> <sub>2</sub> | <i>D</i> <sub>3</sub> |
|----------|----------|----------|-----------------------|-----------------------|-----------------------|-----------------------|
| 1        | X        | X        | 1                     | 1                     | 1                     | 1                     |
| 0        | 0        | 0        | 0                     | 1                     | 1                     | 1                     |
| 0        | 0        | 1        | 1                     | 0                     | 1                     | 1                     |
| 0        | 1        | 0        | 1                     | 1                     | 0                     | 1                     |
| 0        | 1        | 1        | 1                     | 1                     | 1                     | 0                     |

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input

# Use two 3 to 8 decoders to make 4 to 16 decoder

- Enable can also be active high
- In this example, only one decoder can be active at a time.
- **x, y, z** effectively select output line for **w**

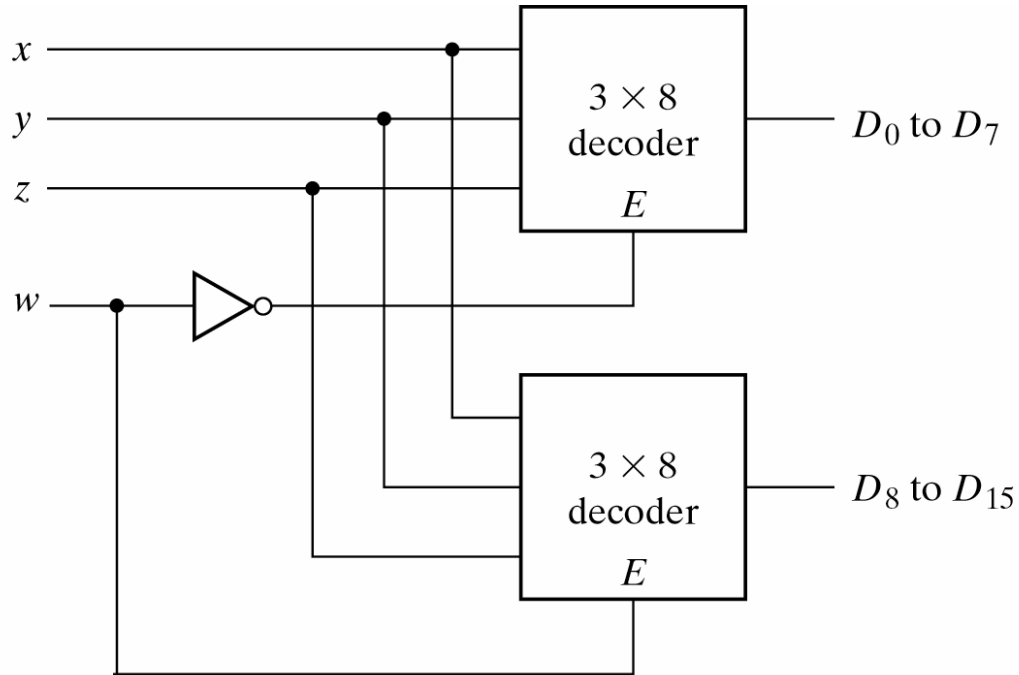


Fig. 4-20 4 × 16 Decoder Constructed with Two 3 × 8 Decoders


# Encoders

---

- If the a decoder's output code has fewer bits than the input code, the device is usually called an encoder.

e.g.  $2^n$ -to- $n$

 
- The simplest encoder is a  $2^n$ -to- $n$  binary encoder
  - One of  $2^n$  inputs = 1
  - Output is an  $n$ -bit binary number



# 8-to-3 Binary Encoder

At any one time, only one input line has a value of 1.

| Inputs |       |       |       |       |       |       |       | Outputs |       |       |
|--------|-------|-------|-------|-------|-------|-------|-------|---------|-------|-------|
| $I_0$  | $I_1$ | $I_2$ | $I_3$ | $I_4$ | $I_5$ | $I_6$ | $I_7$ | $y_2$   | $y_1$ | $y_0$ |
| 1      | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0       | 0     | 0     |
| 0      | 1     | 0     | 0     | 0     | 0     | 0     | 0     | 0       | 0     | 1     |
| 0      | 0     | 1     | 0     | 0     | 0     | 0     | 0     | 0       | 1     | 0     |
| 0      | 0     | 0     | 1     | 0     | 0     | 0     | 0     | 0       | 1     | 1     |
| 0      | 0     | 0     | 0     | 1     | 0     | 0     | 0     | 1       | 0     | 0     |
| 0      | 0     | 0     | 0     | 0     | 1     | 0     | 0     | 1       | 0     | 1     |
| 0      | 0     | 0     | 0     | 0     | 0     | 1     | 0     | 1       | 1     | 0     |
| 0      | 0     | 0     | 0     | 0     | 0     | 0     | 1     | 1       | 1     | 1     |

 

## 8-to-3 Priority Encoder

- What if more than one input line has a value of 1?
- Ignore “lower priority” inputs.
- **Idle** indicates that no input is a 1.
- Note that polarity of **Idle** is opposite from Table 4-8 in Mano

| Inputs         |                |                |                |                |                |                |                | Outputs        |                |                |      |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|------|
| I <sub>0</sub> | I <sub>1</sub> | I <sub>2</sub> | I <sub>3</sub> | I <sub>4</sub> | I <sub>5</sub> | I <sub>6</sub> | I <sub>7</sub> | y <sub>2</sub> | y <sub>1</sub> | y <sub>0</sub> | Idle |
| 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | x              | x              | x              | 1    |
| 1              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0    |
| X              | 1              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0    |
| X              | X              | 1              | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 0    |
| X              | X              | X              | 1              | 0              | 0              | 0              | 0              | 0              | 1              | 1              | 0    |
| X              | X              | X              | X              | 1              | 0              | 0              | 0              | 1              | 0              | 0              | 0    |
| X              | X              | X              | X              | X              | 1              | 0              | 0              | 1              | 0              | 1              | 0    |
| X              | X              | X              | X              | X              | X              | 1              | 0              | 1              | 1              | 0              | 0    |
| X              | X              | X              | X              | X              | X              | X              | 1              | 1              | 1              | 1              | 0    |

# Priority Encoder (8 to 3 encoder)

- Assign priorities to the inputs
- When more than one input are asserted, the output generates the code of the input with the highest priority

- Priority Encoder :

$H7=I7$  (Highest Priority)

$H6=I6.I7'$

$H5=I5.I6'.I7'$

$H4=I4.I5'.I6'.I7'$

$H3=I3.I4'.I5'.I6'.I7'$

$H2=I2.I3'.I4'.I5'.I6'.I7'$

$H1=I1.I2'.I3'.I4'.I5'.I6'.I7'$

$H0=I0.I1'.I2'.I3'.I4'.I5'.I6'.I7'$


$IDLE= I0'.I1'.I2'.I3'.I4'.I5'.I6'.I7'$

- Encoder

$Y0 = I1 + I3 + I5 + I7$


$Y1 = I2 + I3 + I6 + I7$

$Y2 = I4 + I5 + I6 + I7$

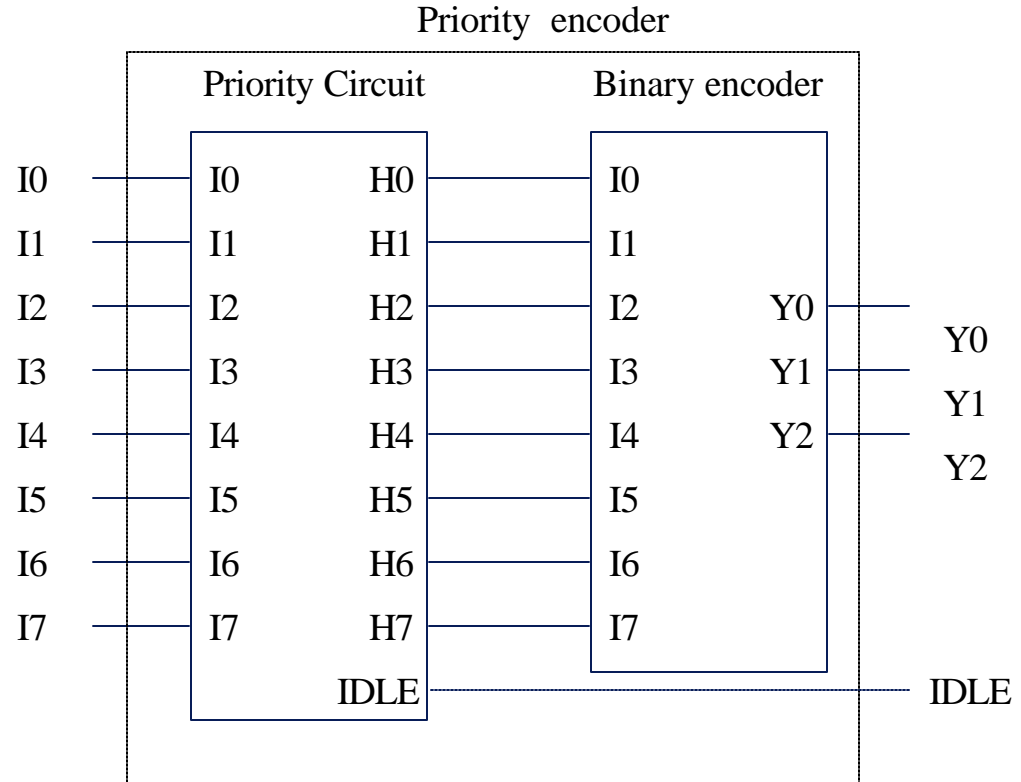
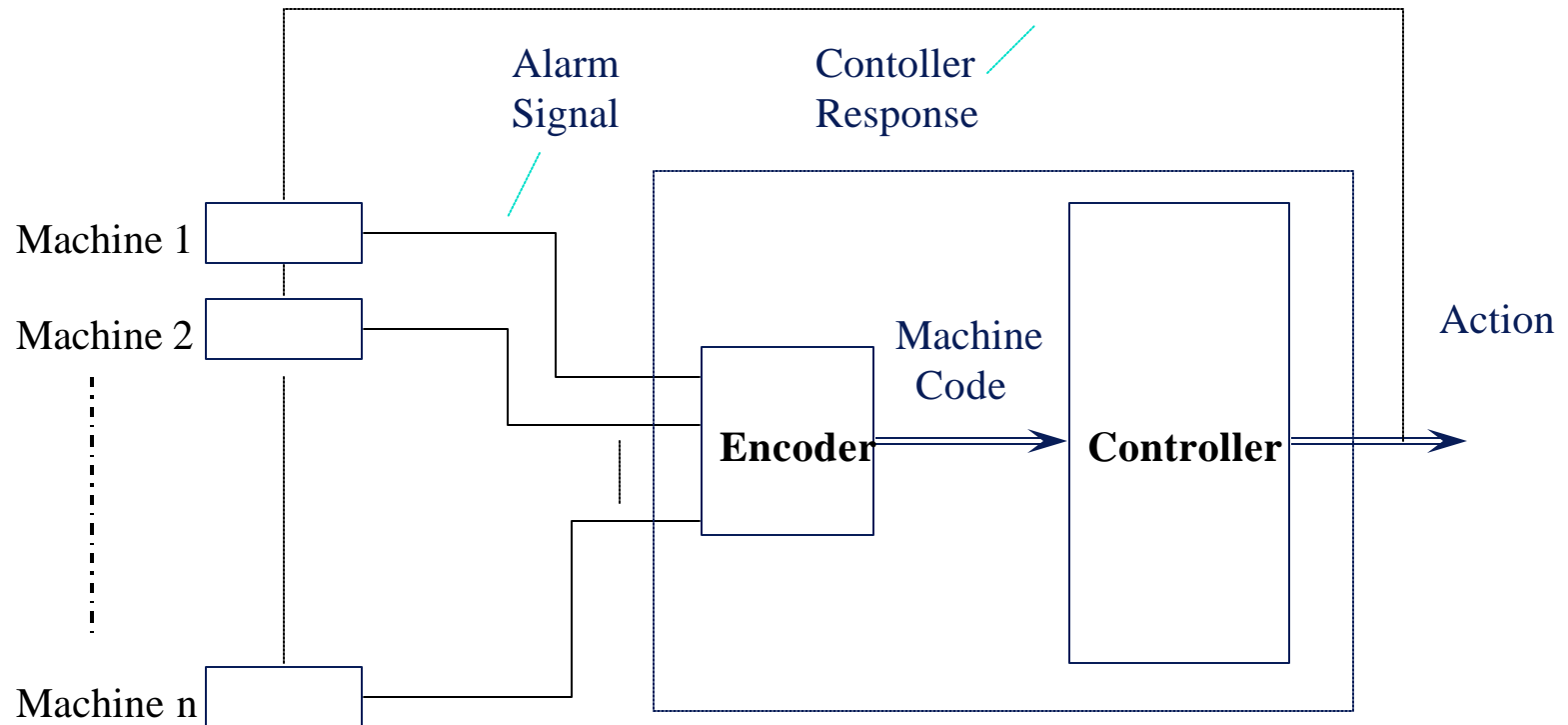
# Encoder Application (Monitoring Unit)

- Encoder identifies the requester and encodes the value
- Controller accepts digital inputs.



# Summary

---

- **Decoder allows for generation of a single binary output from an input binary code**
  - For an  $n$ -input binary decoder there are  $2^n$  outputs
- **Decoders are widely used in storage devices (e.g. memories)**
  - We will discuss these in a few weeks
- **Encoders all for data compression**
- **Priority encoders rank inputs and encode the highest priority input**
- **Next time: storage elements!**