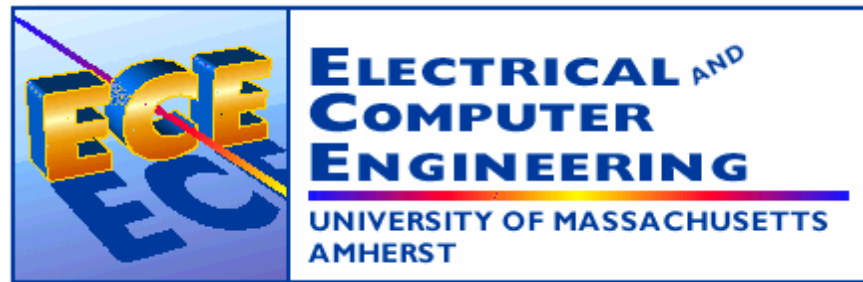

ENGIN 112

Intro to Electrical and Computer Engineering

Lecture 21 *Analyzing Sequential Circuits*




Overview

- **Understanding flip flop state:**
 - Stored values inside flip flops
- **Clocked sequential circuits:**
 - Contain flip flops
- **Representations of state:**
 - State equations
 - State table
 - State diagram
- **Finite state machines**
 - Mealy machine
 - Moore machine

Flip Flop State

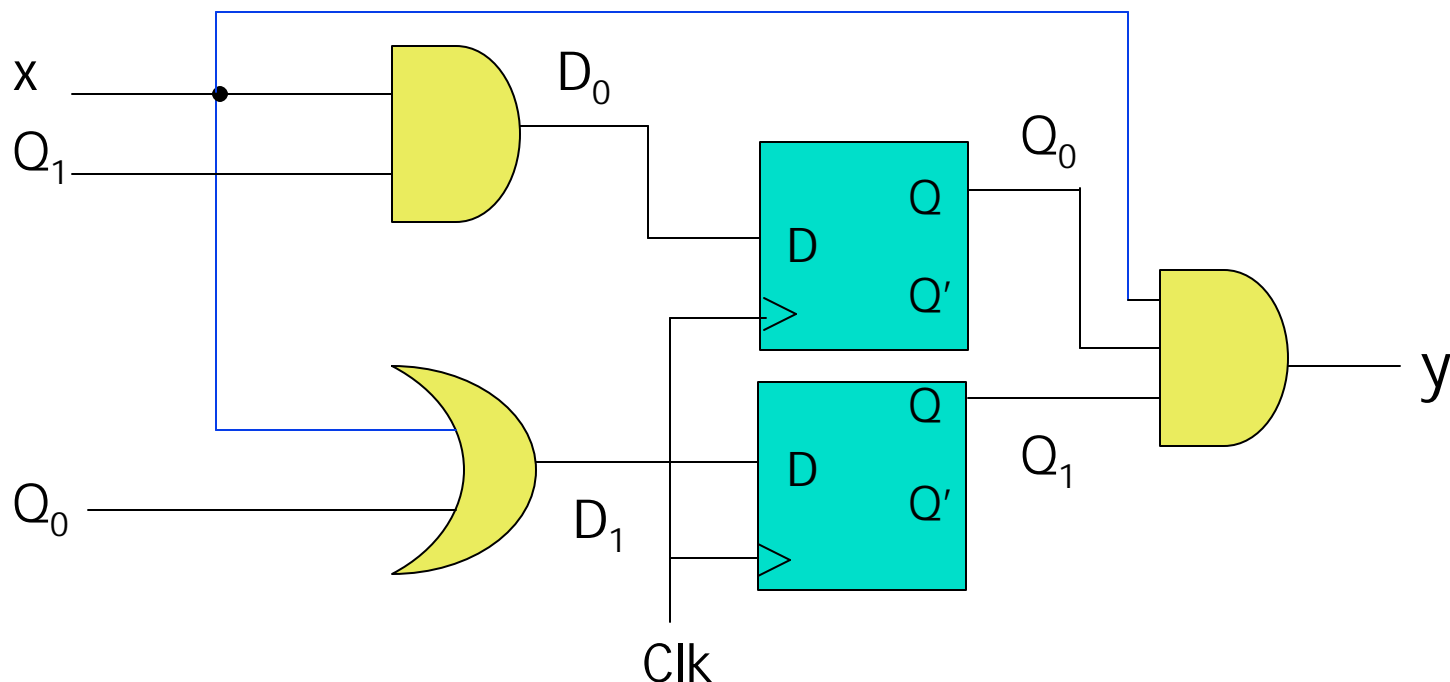
- Behavior of clocked sequential circuit can be determined from inputs, outputs and FF state



$$\begin{aligned}y(t) &= x(t)Q_1(t)Q_0(t) \\Q_0(t+1) &= D_0(t) = x(t)Q_1(t) \\Q_1(t+1) &= D_1(t) = x(t) + Q_0(t)\end{aligned}$$

Output and State Equations

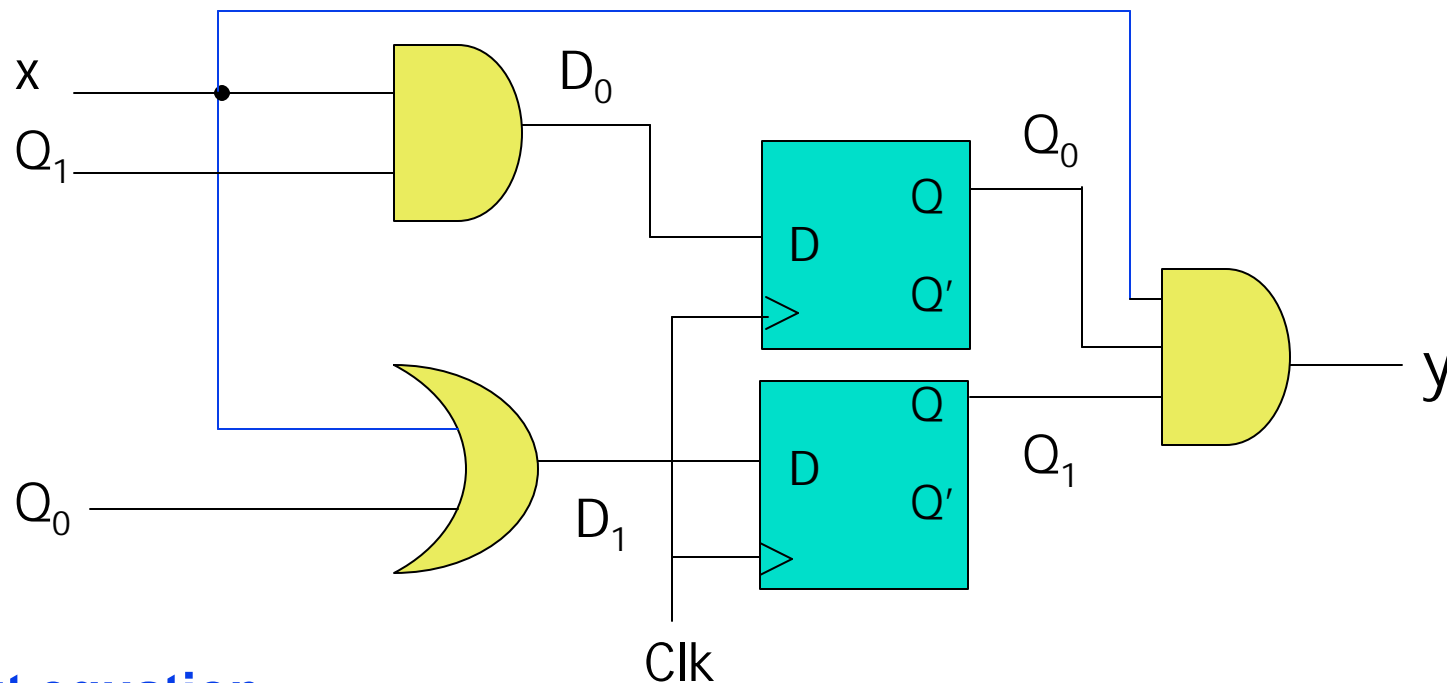- Next state dependent on previous state.



Output equation

$$y(t) = x(t)Q_1(t)Q_0(t)$$

State equations

$$Q_0(t+1) = D_0(t) = x(t)Q_1(t)$$

$$Q_1(t+1) = D_1(t) = x(t) + Q_0(t)$$

State Table

- Sequence of outputs, inputs, and flip flop states enumerated in state table
- **Present state** indicates current value of flip flops
- **Next state** indicates state after next rising clock edge
- **Output** is output value on current clock edge

State Table

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
0 0	00	10	0	0
0 1	10	10	0	0
1 0	00	11	0	0
1 1	10	11	0	1

$Q_1(t) \quad Q_0(t) \qquad Q_1(t+1) \quad Q_0(t+1)$

State Table


- All possible input combinations enumerated
- All possible state combinations enumerated
- Separate columns for each output value.
- Sometimes easier to designate a symbol for each state.

Let:	Present State	Next State		Output	
		x=0	x=1	x=0	x=1
$s_0 = 00$	s_0	s_0	s_2	0	0
$s_1 = 01$	s_1	s_2	s_2	0	0
$s_2 = 10$	s_2	s_0	s_3	0	0
$s_3 = 11$	s_3	s_2	s_3	0	1

State Diagram


- Circles indicate current state
- Arrows point to **next state**
- For **x/y**, **x** is input and **y** is output

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
0 0	00	10	0	0
0 1	10	10	0	0
1 0	00	11	0	0
1 1	10	11	0	1

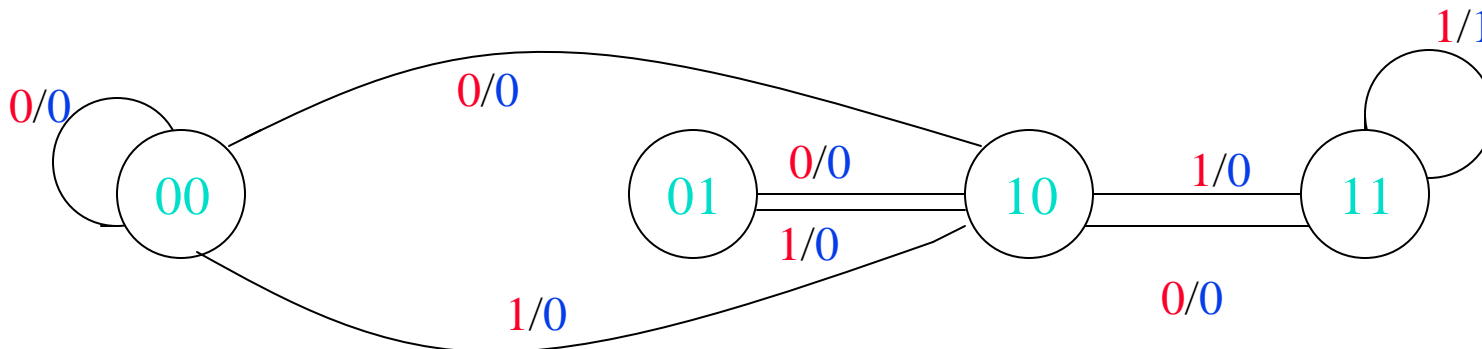


State Diagram

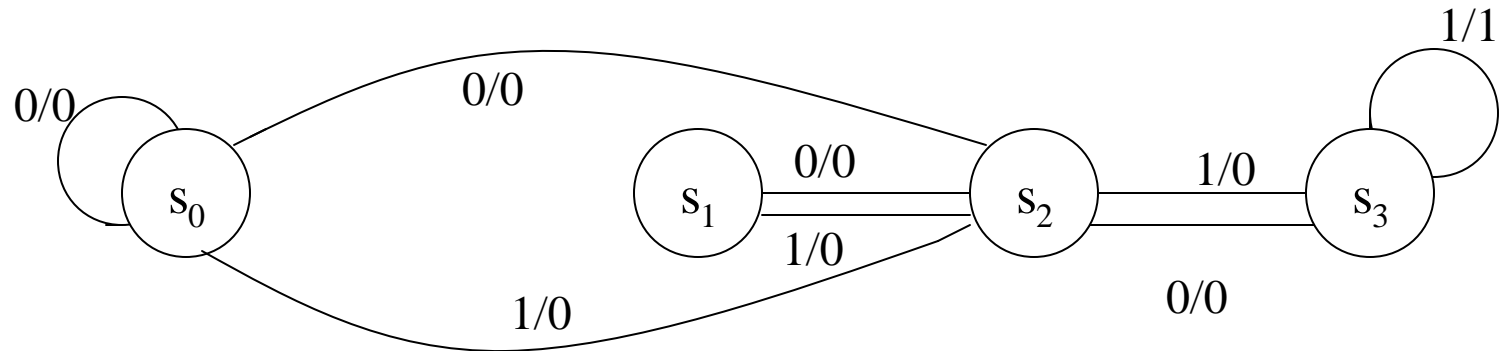- Each state has two arrows leaving
 - One for $x = 0$ and one for $x = 1$
- Unlimited arrows can enter a state
- Note use of state names in this example
 - Easier to identify



Flip Flop Input Equations

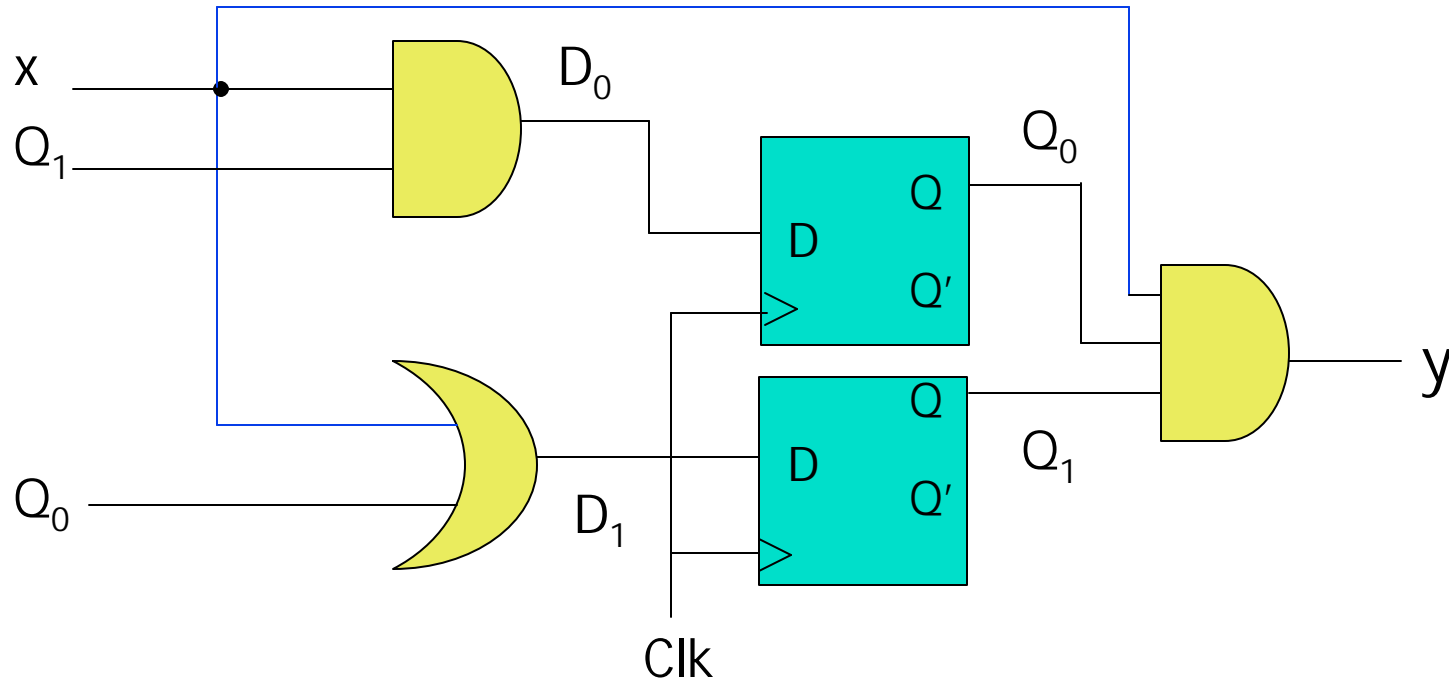- Boolean expressions which indicate the input to the flip flops.




$$D_{Q_0} = XQ_1$$

$$D_{Q_1} = X + Q_0$$

Format implies type of flop used

Analysis with D Flip-Flops

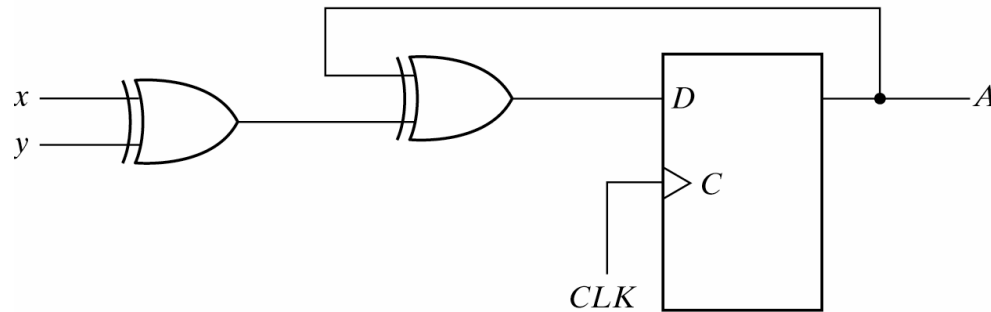
- Identify flip flop input equations
- Identify output equation



(a) Circuit diagram

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table

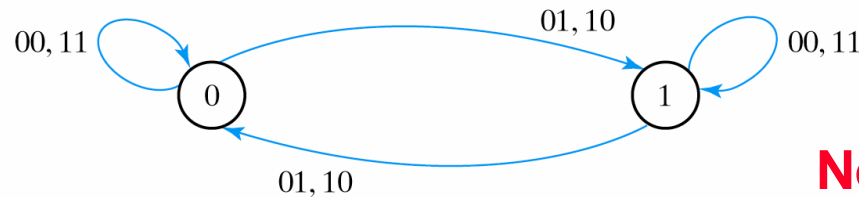


(c) State diagram

Note: this example has no output

Fig. 5-17 Sequential Circuit with D Flip-Flop


Mealy Machine

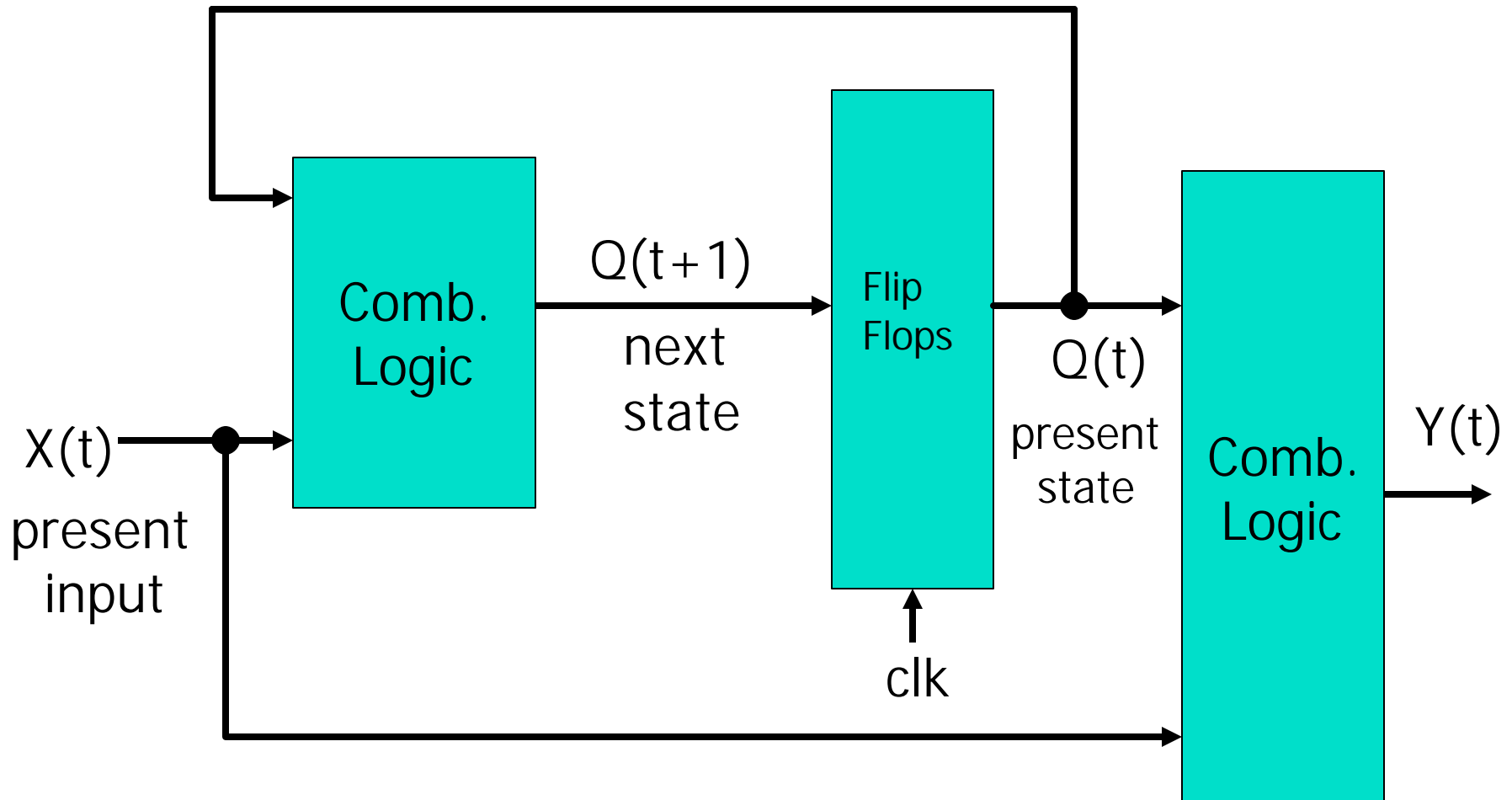- Output based on state and present input




Moore Machine

- Output based on state only

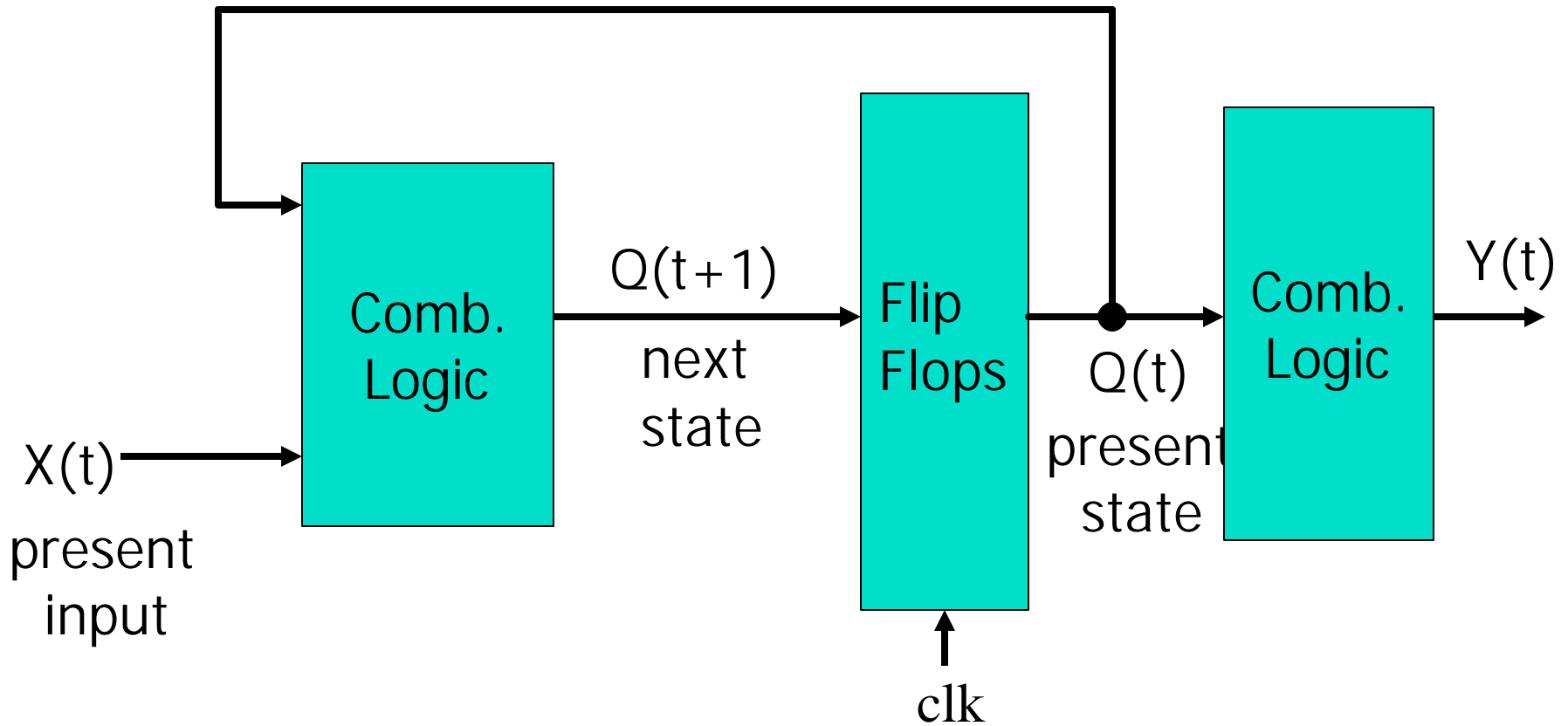


Mealy versus Moore

Mealy Model

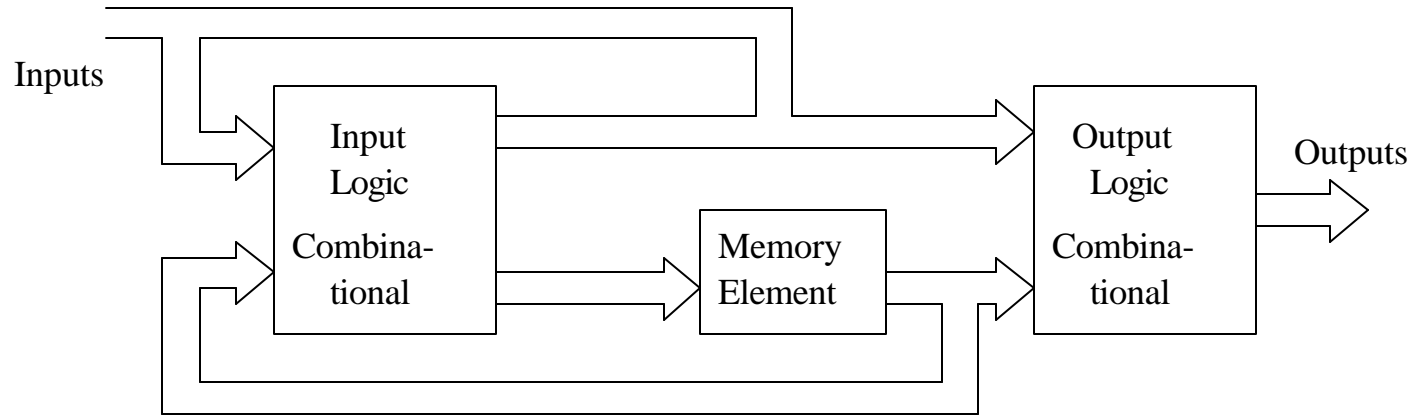


Moore Model

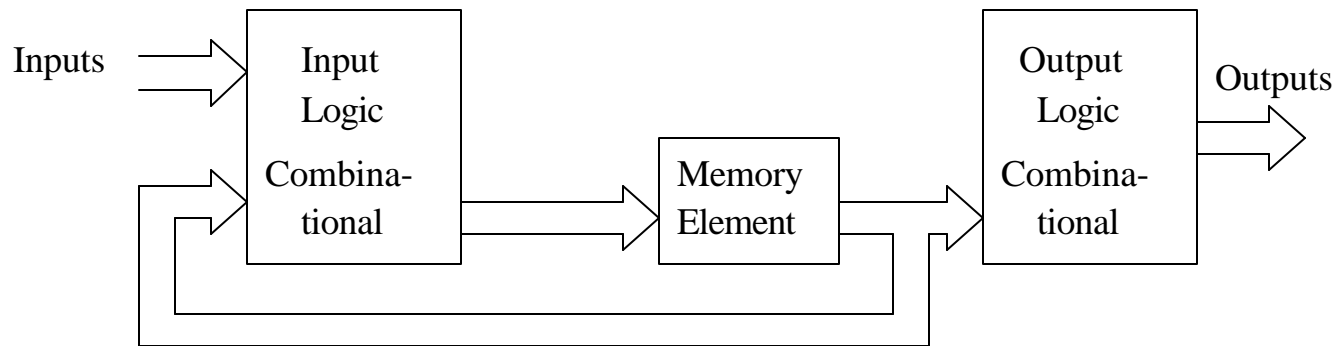

State Diagram with One Input & One Mealy Output

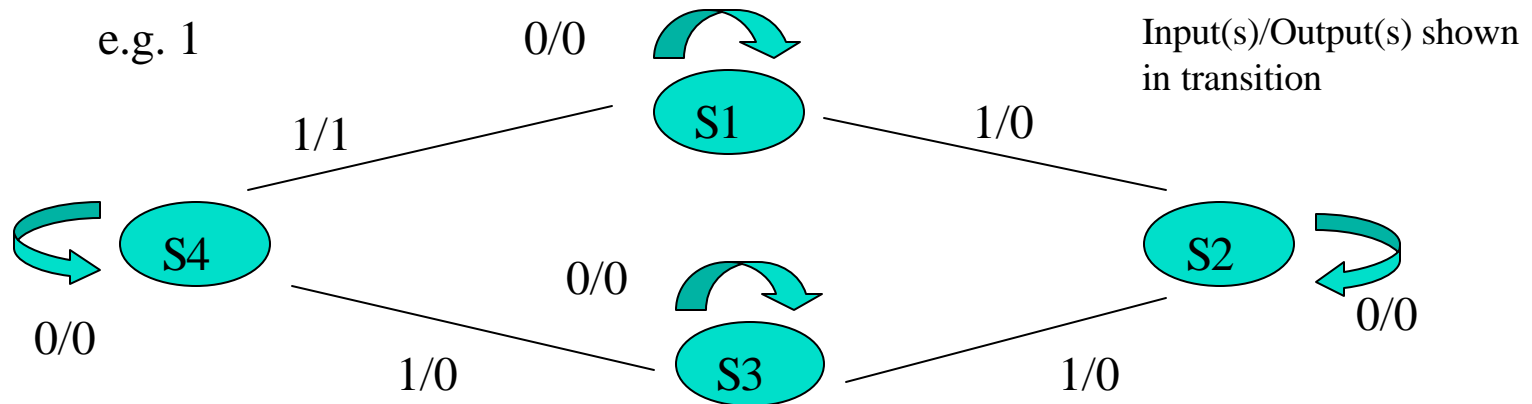- Mano text focuses on **Mealy** machines
- State transitions are shown as a function of inputs and current outputs.



State Diagram with One Input & a *Moore* Output

- **Moore machine: outputs only depend on the current state**
- **Outputs **cannot** change during a clock pulse if the input variables change**
- **Moore Machines usually have more states.**
- **No direct path from inputs to outputs**
- **Can be more reliable**

Clocked Synchronous State-machine Analysis – next class

Given the circuit diagram of a state machine:

1 Analyze the combinational logic to determine flip-flop input (excitation) equations: $D_i = F_i(Q, \text{inputs})$

- The input to each flip-flop is based upon current state and circuit inputs.

2 Substitute excitation equations into flip-flop characteristic equations, giving transition equations: $Q_i(t+1) = H_i(D_i)$

3 From the circuit, find output equations: $Z = G(Q, \text{inputs})$

- The outputs are based upon the current state and possibly the inputs.

4 Construct a state transition/output table from the transition and output equations:

- Similar to truth table.
- Present state on the left side.
- Outputs and next state for each input value on the right side.
- Provide meaningful names for the states in state table, if possible.

5 Draw the state diagram which is the graphical representation of state table.

Summary

- **Flip flops contain state information**
- **State can be represented in several forms:**
 - State equations
 - State table
 - State diagram
- **Possible to convert between these forms**
- **Circuits with state can take on a finite set of values**
 - Finite state machine
- **Two types of “machines”**
 - Mealy machine
 - Moore machine