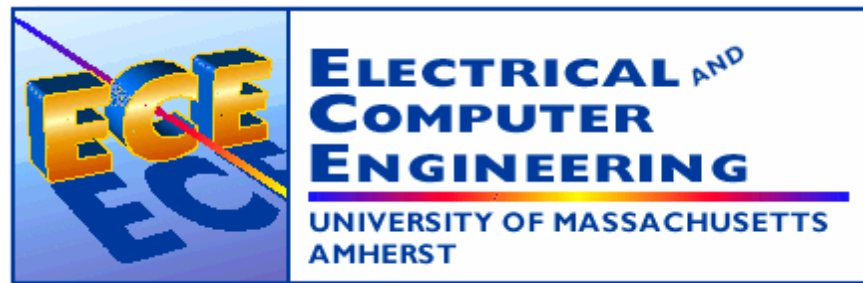

ENGIN 112

Intro to Electrical and Computer Engineering

Lecture 23

Finite State Machine Design Procedure



Overview


- Design of systems that input flip flops and combinational logic
- Specifications start with a **word** description
- Create a state table to indicate next states
- Convert next states and outputs to output and flip flop input equations
 - Reduce logic expressions using truth tables
- Draw resulting circuits.



Lots of opportunities for interesting design

Concept of the State Machine


Computer Hardware = Datapath + Control

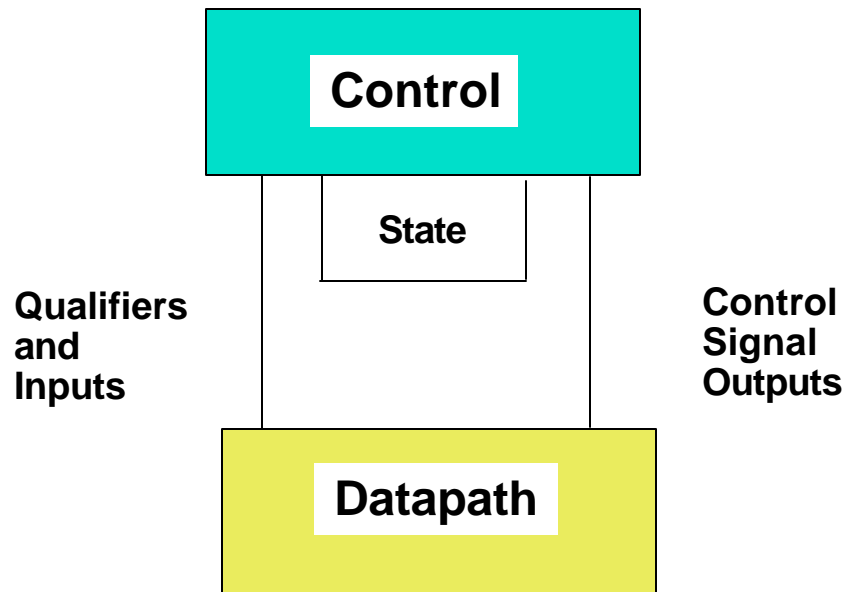

Designing Finite State Machines

- Specify the problem with words
 - *(e.g. Design a circuit that detects three consecutive 1 inputs)*
- Assign binary values to states
- Develop a state table
- Use K-maps to simplify expressions
 - Flip flop input equations and output equations
- Create appropriate logic diagram
 - Should include combinational logic and flip flops

Example: Detect 3 Consecutive 1 inputs

 

- ˆ **State S_0 : zero 1s detected**
- ˆ **State S_1 : one 1 detected**
- ˆ **State S_2 : two 1s detected**
- ˆ **State S_3 : three 1s detected**

Fig. 5-24 State Diagram for Sequence Detector

- **Note that each state has 2 output arrows**
- **Two bits needed to encode state**

State Table for Sequence Detector

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

- Sequence of outputs, inputs, and flip flop states enumerated in state table

- Present state** indicates current value of flip flops

- Next state** indicates state after next rising clock edge

- Output** is output value on current clock edge

- $S_0 = 00$

- $S_2 = 10$

- $S_1 = 01$

- $S_3 = 11$

Finding Expressions for Next State and Output Value

- Create K-map directly from state table (3 columns = 3 K-maps)
- Minimize K-maps to find SOP representations
- Separate circuit for each next state and output value

 


Fig. 5-25 Maps for Sequence Detector

Circuit for Consecutive 1s Detector

- **Note location of state flip flops**
- **Output value (y) is function of state**
- **This is a Moore machine.**


 


Fig. 5-26 Logic Diagram of Sequence Detector

Concept of the State Machine

 Example: Odd Parity Checker

Assert output whenever input bit stream has odd # of 1's



**State
Diagram**

Present State	Input	Next State	Output
Even	0	Even	0
Even	1	Odd	0
Odd	0	Odd	1
Odd	1	Even	1

Symbolic State Transition Table

Present State	Input	Next State	Output
0	0	0	0
0	1	1	0
1	0	1	1
1	1	0	1

Encoded State Transition Table


- **Note: Present state and output are the same value**
- **Moore machine**

Concept of the State Machine

 
Example: Odd Parity Checker

Next State/Output Functions

$$NS = PS \text{ xor } PI; \quad OUT = PS$$




D FF Implementation

 

Timing Behavior: Input 1 0 0 1 1 0 1 0 1 1 1 0

Mealy and Moore Machines


Solution 1: (Mealy)

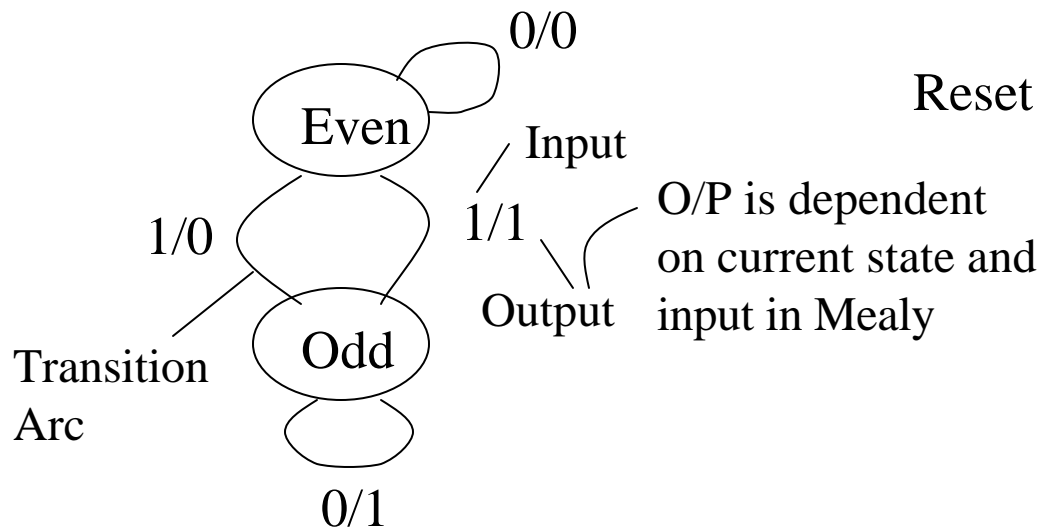

Mealy Machine: Output is associated with the state transition

- Appears before the state transition is completed (by the next clock pulse).

Solution 2: (Moore)

 


Moore Machine: Output is associated with the state

- Appears after the state transition takes place.

Vending Machine FSM


Step 1. Specify the problem

 - ❑ Deliver package of gum after 15 cents deposited
- ❑ Single coin slot for dimes, nickels
- ❑ No change
- ❑ Design the FSM using combinational logic and flip flops



Vending Machine FSM

State Diagram

 

**Reuse states
whenever possible**

Present State	Inputs		Next State	Output Open
	D	N		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	X	X
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	X	X
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	X	X
15¢	X	X	15¢	1

Symbolic State Table




Vending Machine FSM

State Encoding


How many flip-flops are needed?

Present State		Inputs		Next State		Output
Q_1	Q_0	D	N	D_1	D_0	Open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	X	X	X
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	X	X	X
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
		1	1	X	X	X
1	1	0	0	1	1	1
		0	1	1	1	1
		1	0	1	1	1
		1	1	X	X	X

Determine F/F implementation

 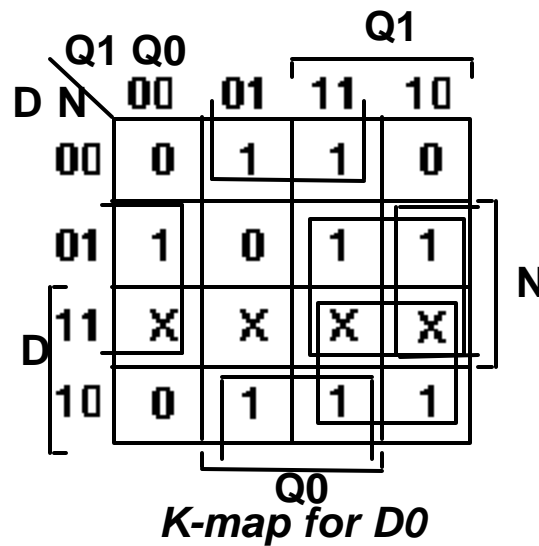 

Minimized Implementation

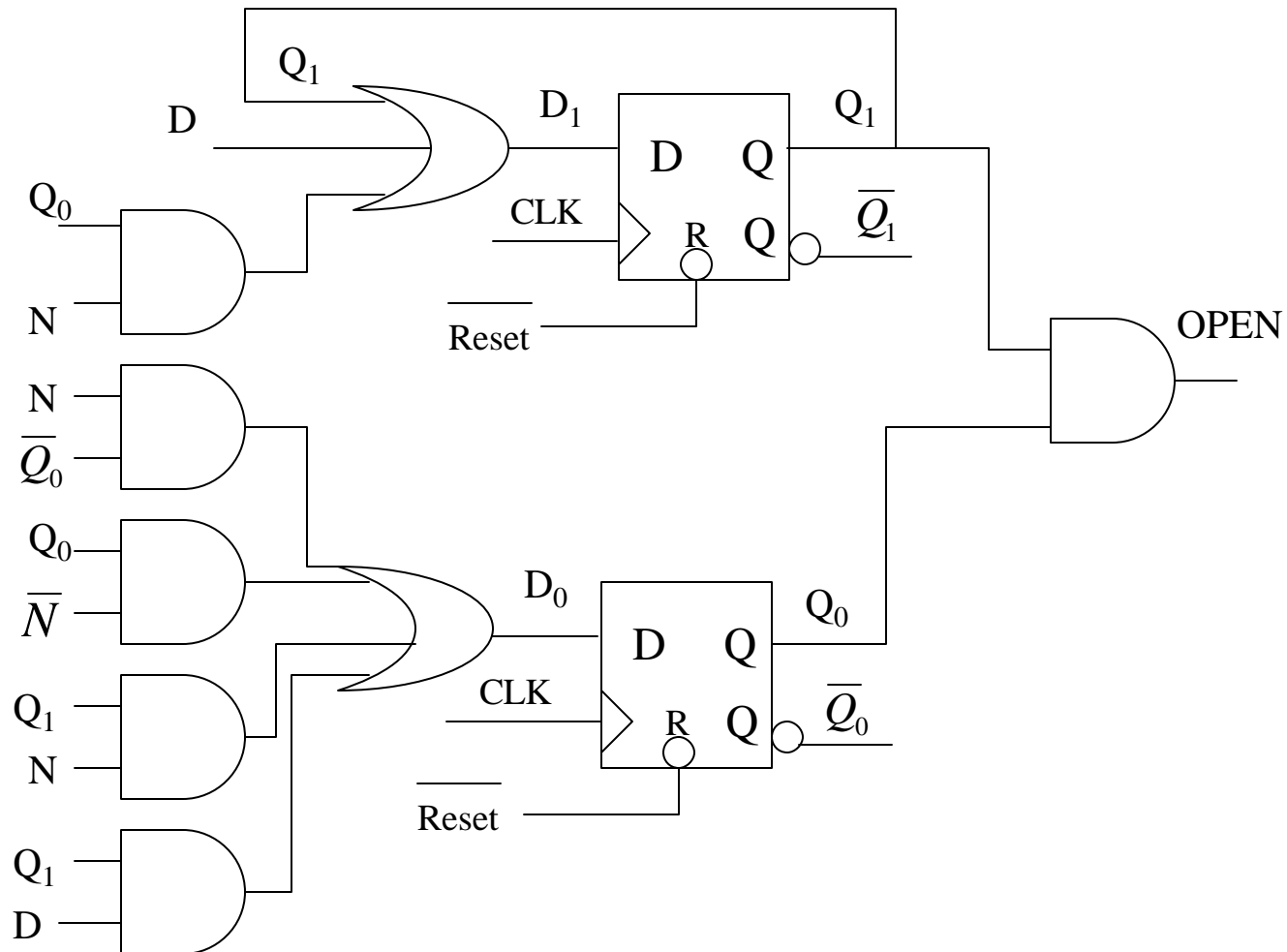

Vending machine FSM implementation based on D flip-flops(Moore).

Summary

- **Finite state machines form the basis of many digital systems**
- **Designs often start from clear specifications**
- **Develop state diagram and state table**
- **Optimize using combinational design techniques**
- **Mealy or Moore implementations possible**
 - Can model approach using HDL.

