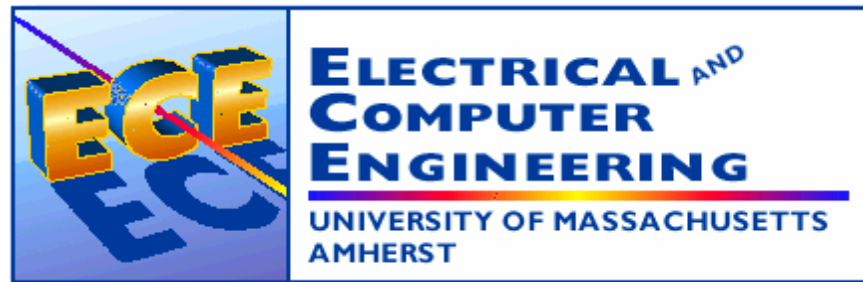

ENGIN 112

Intro to Electrical and Computer Engineering

Lecture 27

Counters



Overview


- **Counters are important components in computers**
 - The increment or decrement by one in response to input
- **Two main types of counters**
 - Ripple (asynchronous) counters
 - Synchronous counters
- **Ripple counters**
 - Flip flop output serves as a source for triggering other flip flops
- **Synchronous counters**
 - All flip flops triggered by a **clock** signal
- **Synchronous counters are more widely used in industry.**

Counters


- **Counter: A register that goes through a prescribed series of states**
- **Binary counter**
 - Counter that follows a binary sequence
 - N bit binary counter counts in binary from 0 to $2^n - 1$
- **Ripple counters triggered by initial **Count** signal**
- **Applications:**
 - Watches
 - Clocks
 - Alarms
 - Web browser refresh

Binary Ripple Counter

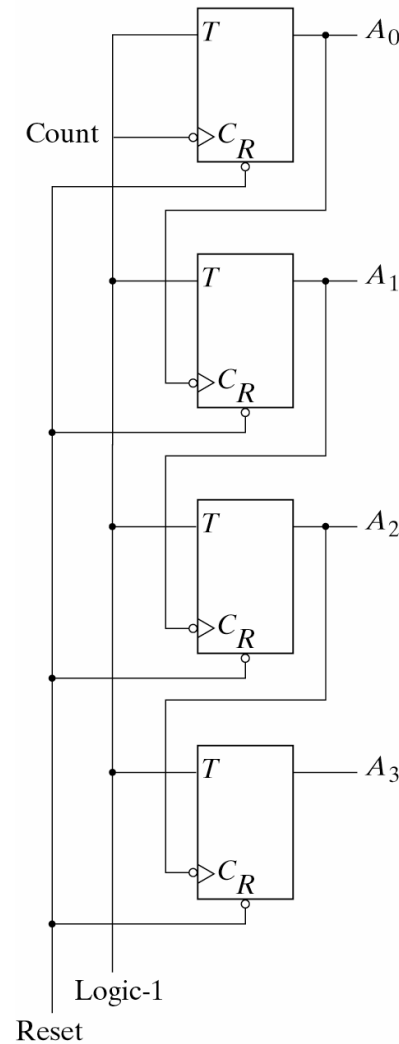- **Reset signal sets all outputs to 0**
- **Count signal toggles output of low-order flip flop**
- **Low-order flip flop provides trigger for adjacent flip flop**
- **Not all flops change value simultaneously**
 - Lower-order flops change first
- **Focus on D flip flop implementation**




(a) With T flip-flops

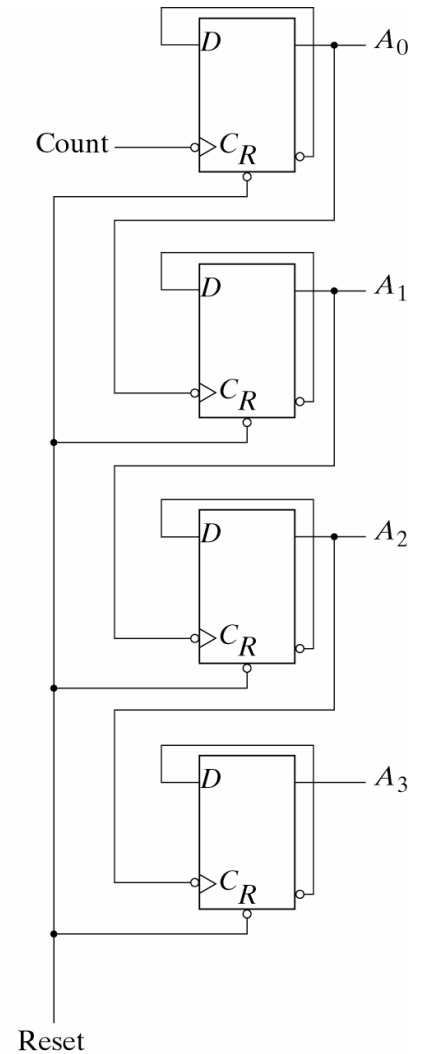


(b) With D flip-flops

Fig. 6-8 4-Bit Binary Ripple Counter

Another Asynchronous Ripple Counter

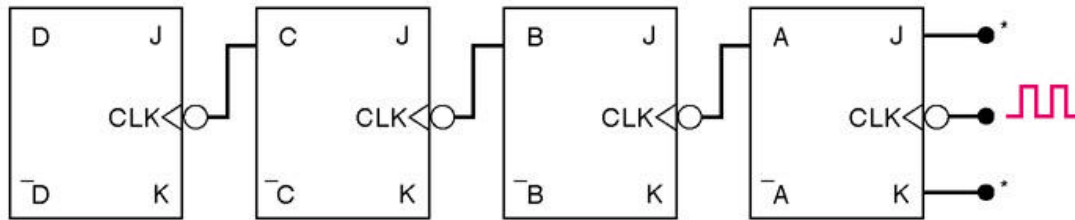

*All J and K inputs assumed to be 1.

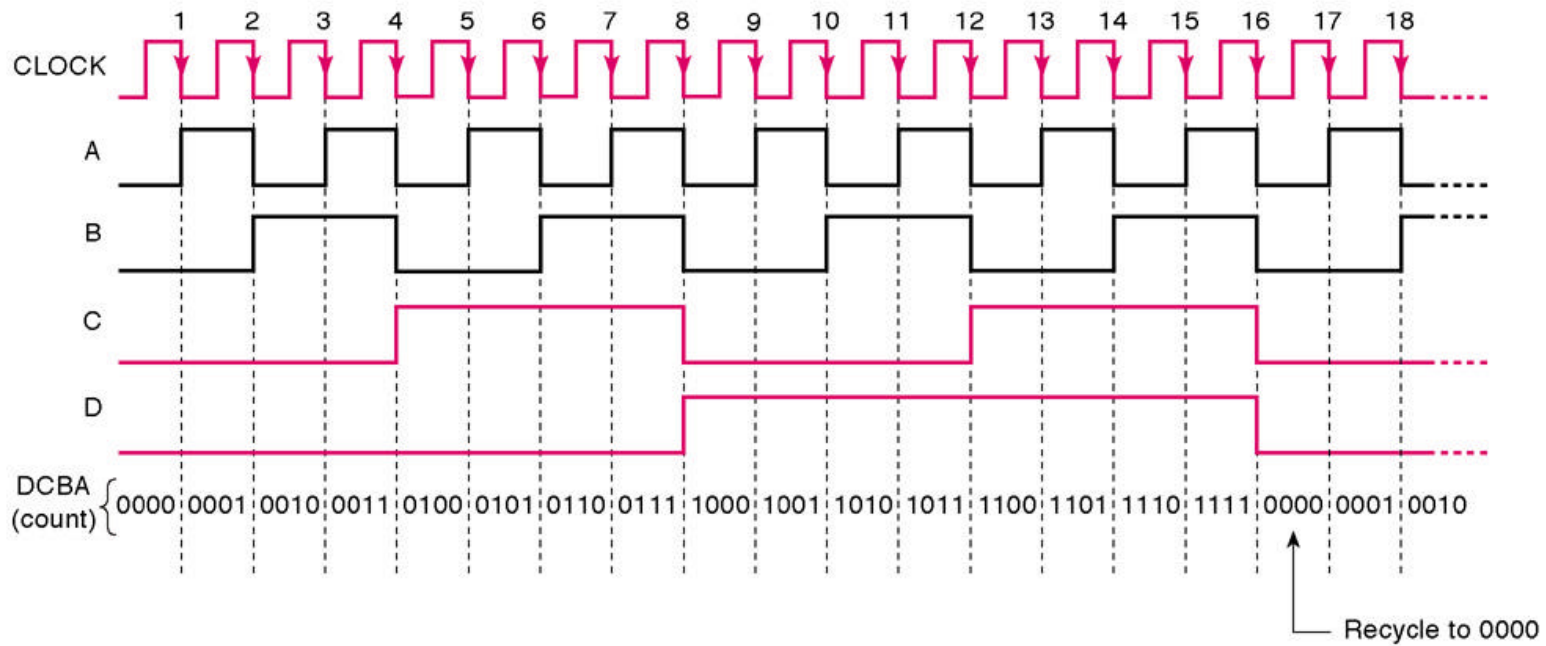

- Similar to T flop example on previous slide

Asynchronous Counters

- Each FF output drives the CLK input of the next FF.
- FFs do not change states in exact synchronism with the applied clock pulses.
- *There is delay between the responses of successive FFs.*
- *Ripple counter* due to the way the FFs respond one after another in a kind of rippling effect.

<u>A₃</u>	<u>A₂</u>	<u>A₁</u>	<u>A₀</u>
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
1	0	0	0
1	0	0	1

Synchronous counters

- **Synchronous(parallel) counters**
 - All of the FFs are triggered simultaneously by the clock input pulses.
 - All FFs change at same time
- **Remember**
 - If $J=K=0$, flop maintains value
 - If $J=K=1$, flop toggles
- **Most counters are synchronous in computer systems.**
- **Can also be made from D flops**
- **Value increments on positive edge**

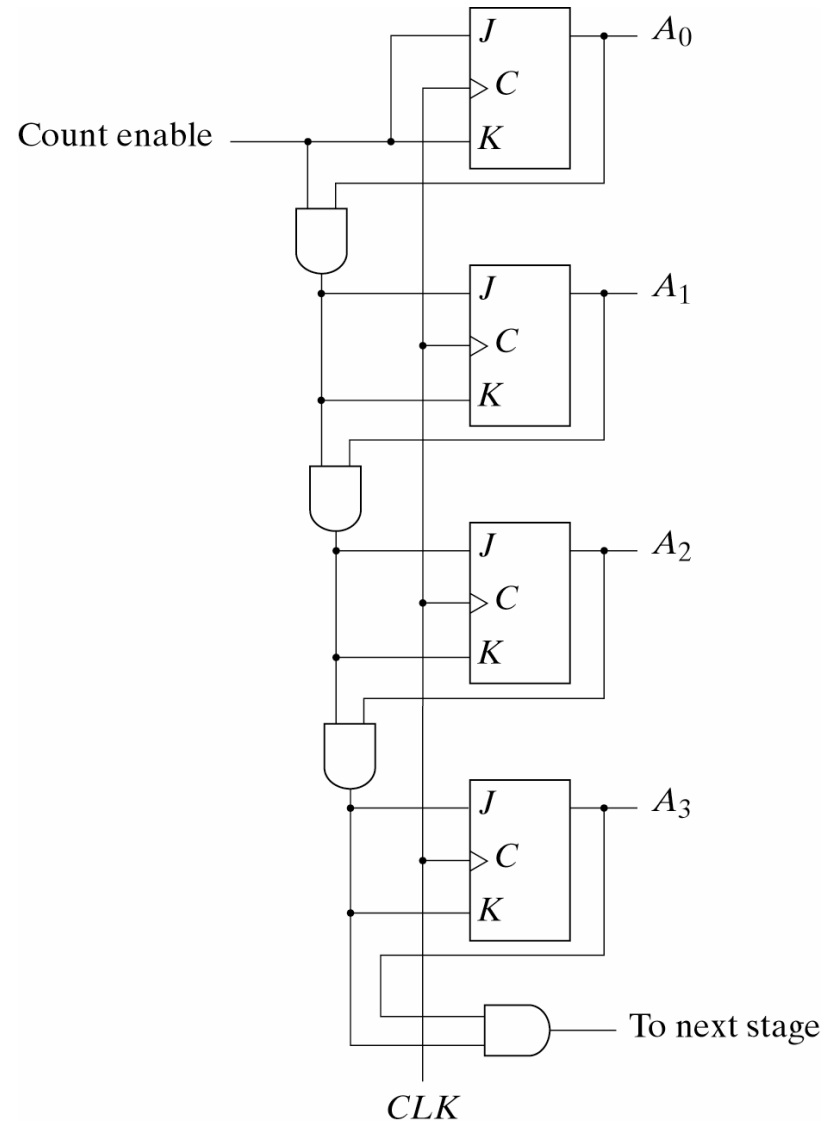



Fig. 6-12 4-Bit Synchronous Binary Counter

November 5, 2003

Synchronous counters

◦ Synchronous counters

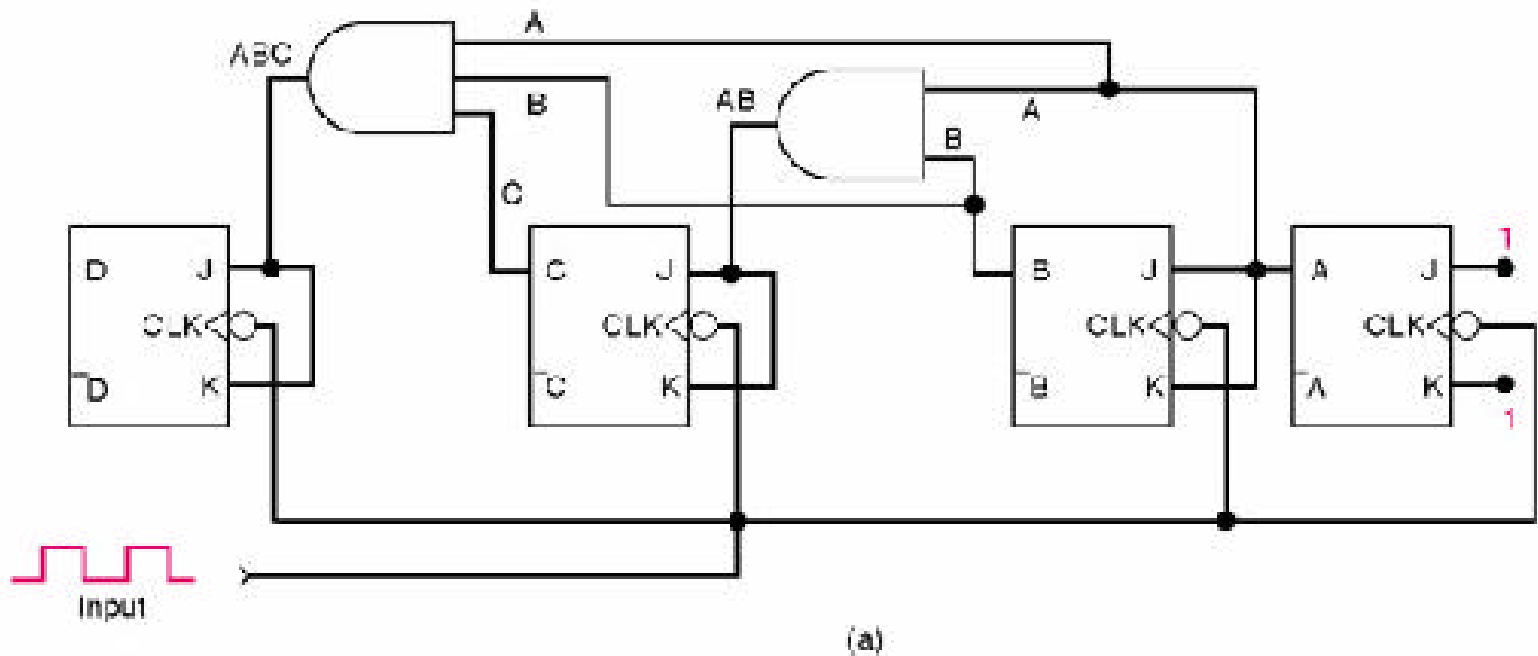- Same counter as previous slide except **Count enable** replaced by $J=K=1$
- Note that clock signal is a square wave
- Clock **fans out** to all clock inputs



Circuit operation

Count	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1
...
...	...	etc.

(b)

- Count value increments on each **negative edge**
- Note that low-order bit **(A)** toggles on each clock cycle

Synchronous UP/Down counters

- Up/Down Counter can either count **up** or **down** on each clock cycle
- Up counter counts from 0000 to 1111 and then changes back to 0000
- Down counter counts from 1111 to 0000 and then back to 1111
- Counter counts up or down each clock cycle
- Output changes occur on clock rising edge

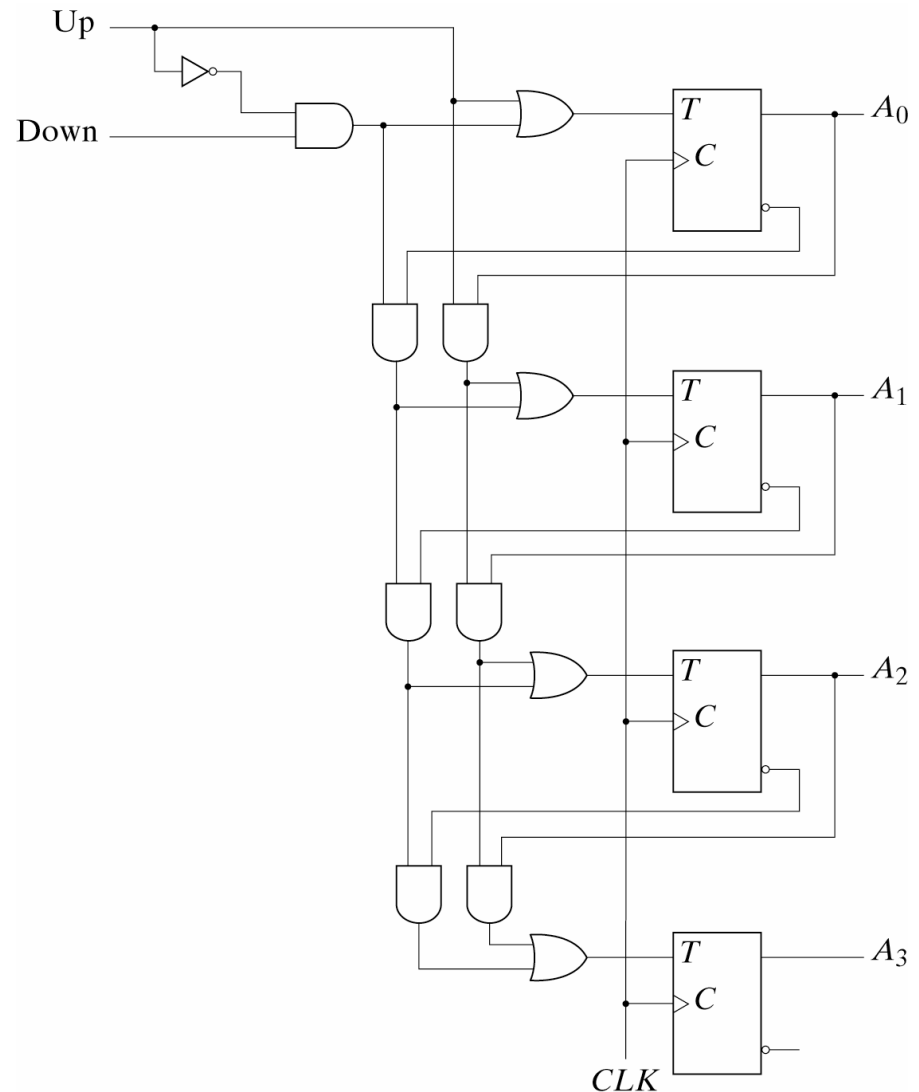


Fig. 6-13 4-Bit Up-Down Binary Counter

November 5, 2003

Counters with Parallel Load

- Counters with parallel load can have a preset value
- Load signal indicates that data ($I_3 \dots I_0$) should be loaded into the counter
- Clear resets counter to all zeros
- Carry output could be used for higher-order bits

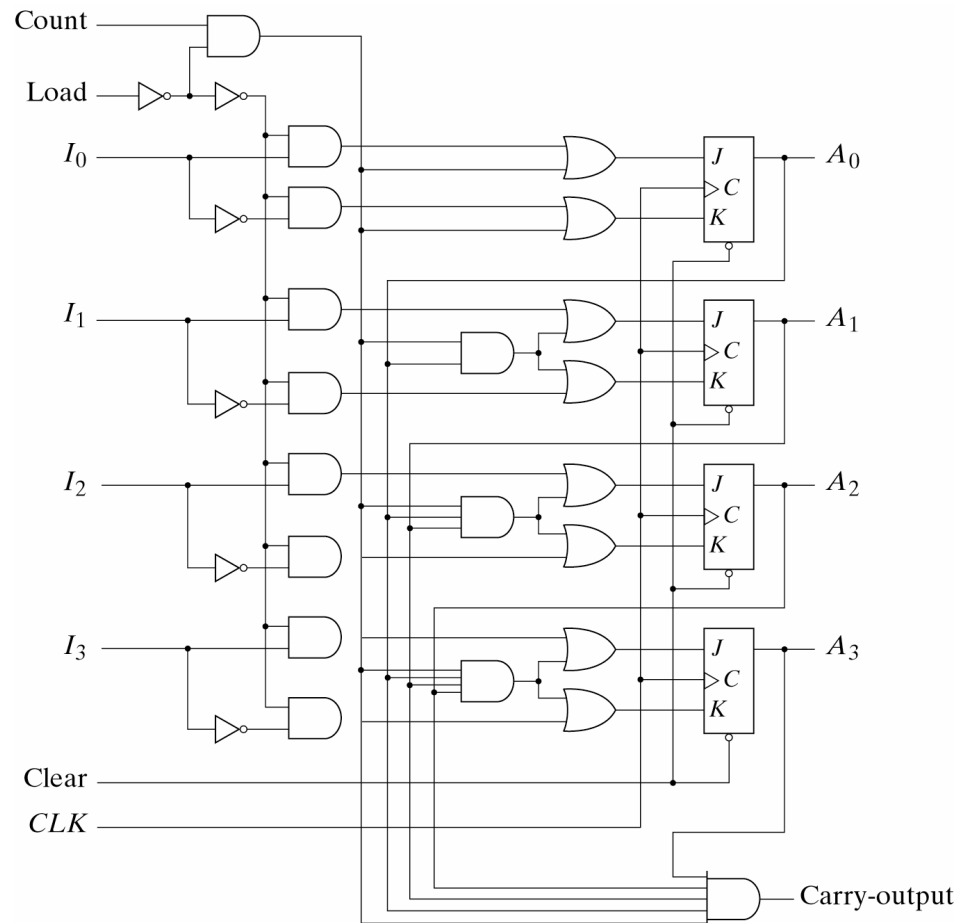


Fig. 6-14 4-Bit Binary Counter with Parallel Load

Counters with Parallel Load

Clear	Clk	Load	Count	Function
0	X	X	X	Clear to 0
1	?	1	X	Load inputs
1	?	0	1	Count
1	?	0	0	No Change

Function Table

- **If Clear is asserted (0), the counter is cleared**
- **If Load is asserted data inputs are loaded**
- **If Count asserted counter value is incremented**


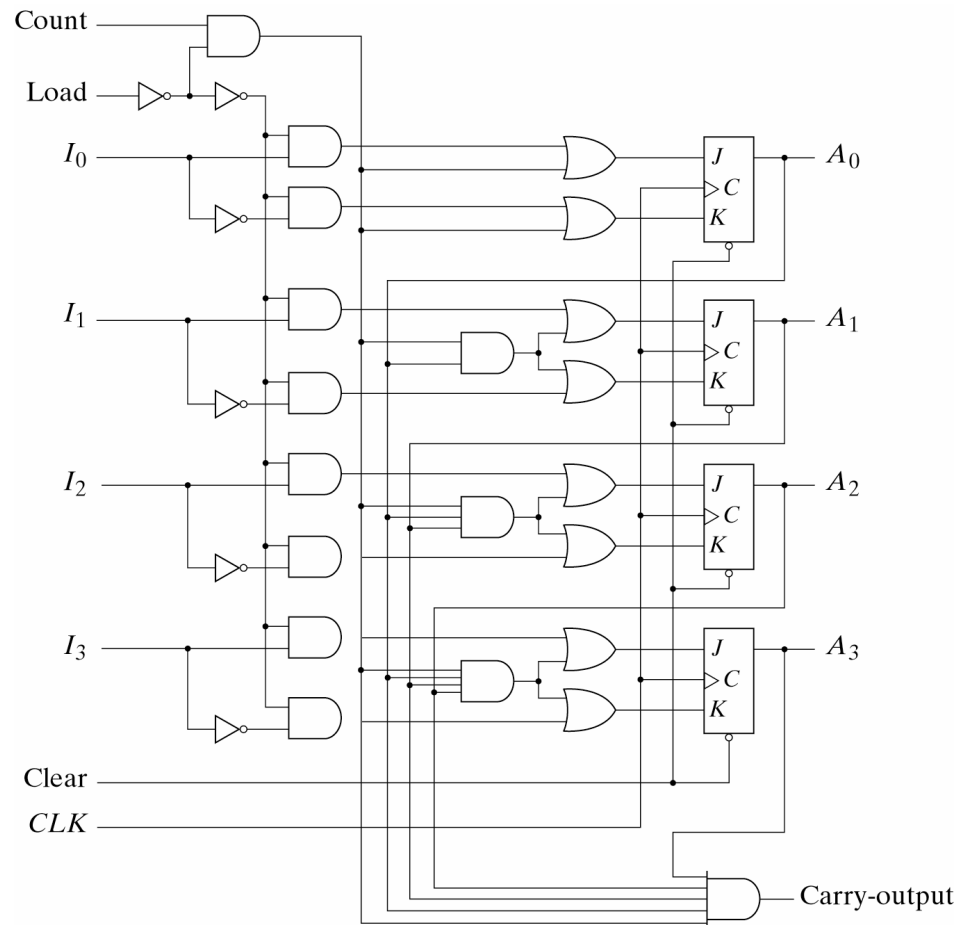


Fig. 6-14 4-Bit Binary Counter with Parallel Load


Binary Counter with Parallel Load and Preset

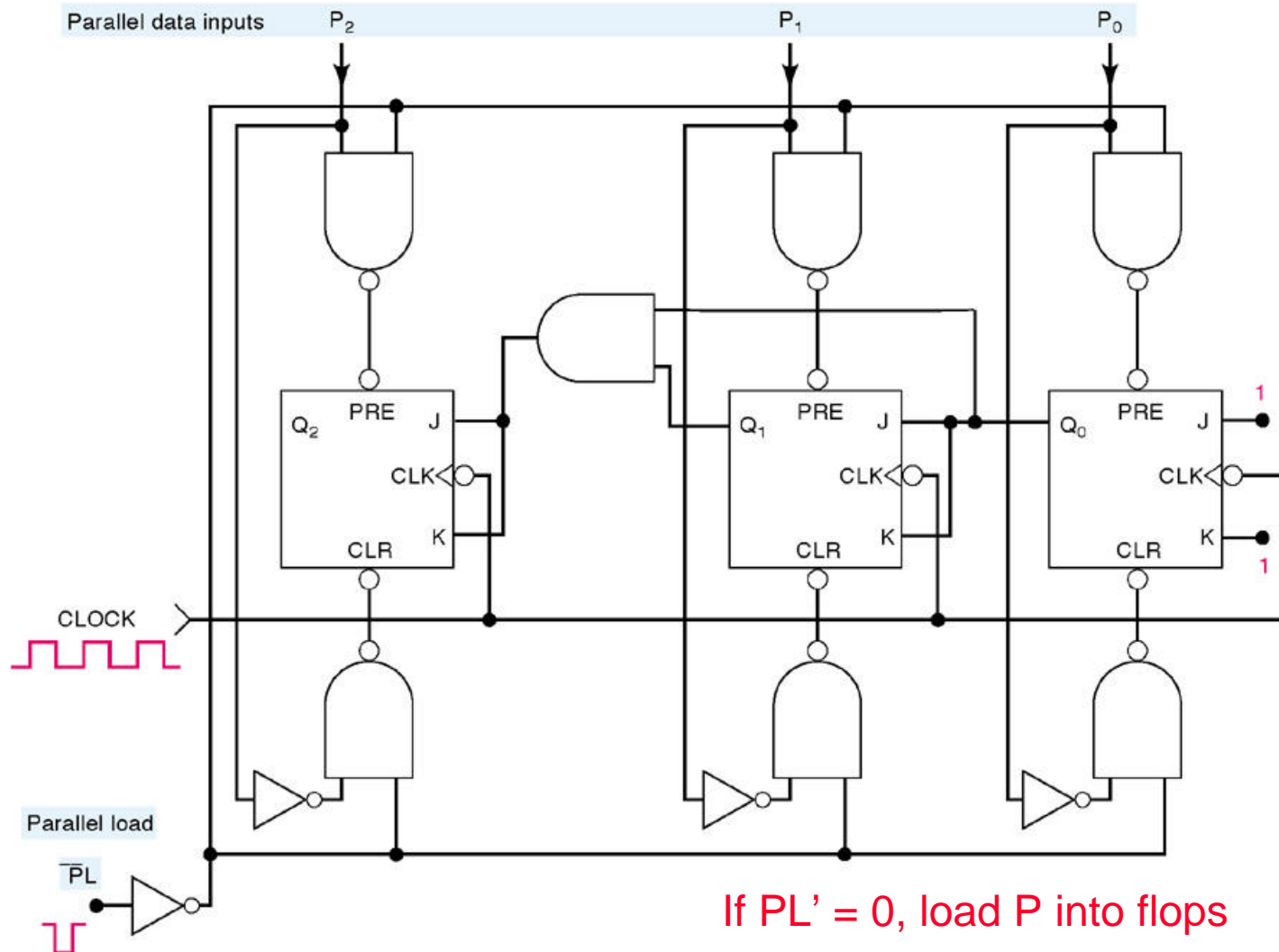- Presettable parallel counter with asynchronous preset.



Binary Counter with Parallel Load and Preset

- Commercial version of binary counter

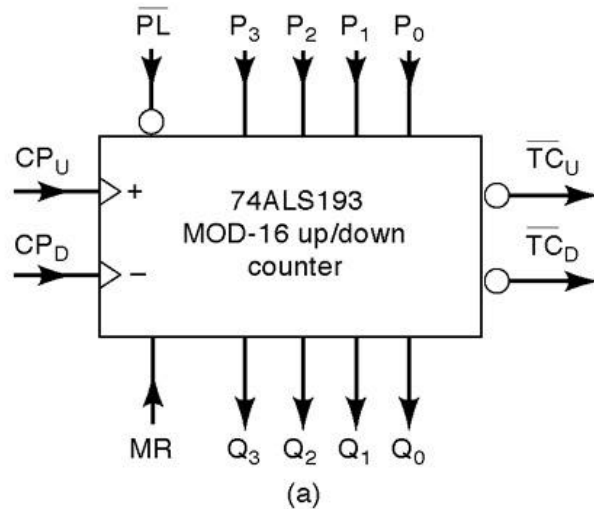

Mode Select

MR	$\overline{\text{PL}}$	CP _U	CP _D	Mode
H	X	X	X	Asynch. reset
L	L	X	X	Asynch. preset
L	H	H	H	No change
L	H	↑	H	Count up
L	H	H	↑	Count down

H = HIGH; L = LOW

X = Don't care; ↑ = PGT

(c)

Pin	Description
CP _U	Count-up clock input (active rising edge)
CP _D	Count-down clock input (active rising edge)
MR	Asynchronous master reset input (active HIGH)
$\overline{\text{PL}}$	Asynchronous parallel load input (active LOW)
P ₀ -P ₃	Parallel data inputs
Q ₀ -Q ₃	Flip-flop outputs
$\overline{\text{TC}}_{\text{D}}$	Terminal count-down (borrow) output (active LOW)
$\overline{\text{TC}}_{\text{U}}$	Terminal count-up (carry) output (active) LOW

(b)

Summary

- **Binary counters can be ripple or synchronous**
- **Ripple counters use flip flop outputs as flop triggers**
 - **Some delay before all flops settle on a final value**
 - **Do not require a clock signal**
- **Synchronous counters are controlled by a clock**
 - **All flip flops change at the same time**
- **Up/Down counters can either increment or decrement a stored binary value**
 - **Control signal determines if counter counts up or down**
- **Counters with parallel load can be set to a known value before counting begins.**