


---

# ENGIN 112

## Intro to Electrical and Computer Engineering

### Lecture 34

### *Datapath Analysis*

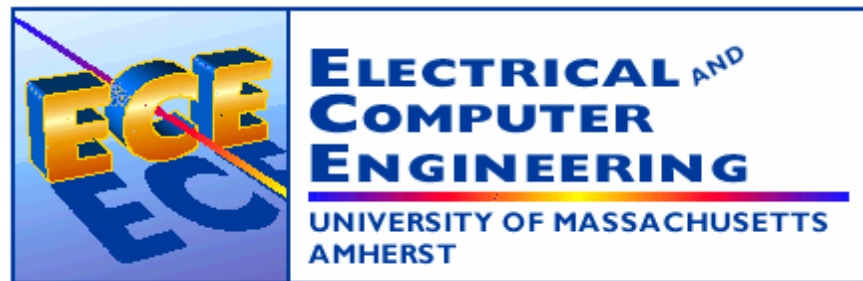


# Overview

---

- **Datapaths must deal with input and output data values**
  - Implement with tri-state buffers
- **Necessary to control external interfaces**
  - Perform repetitive operations
- **Some datapaths require decision making**
  - Control outputs implemented in ROM
- **Moving towards software**
  - Control implemented as a series of instructions
- **Understanding the data and control path**
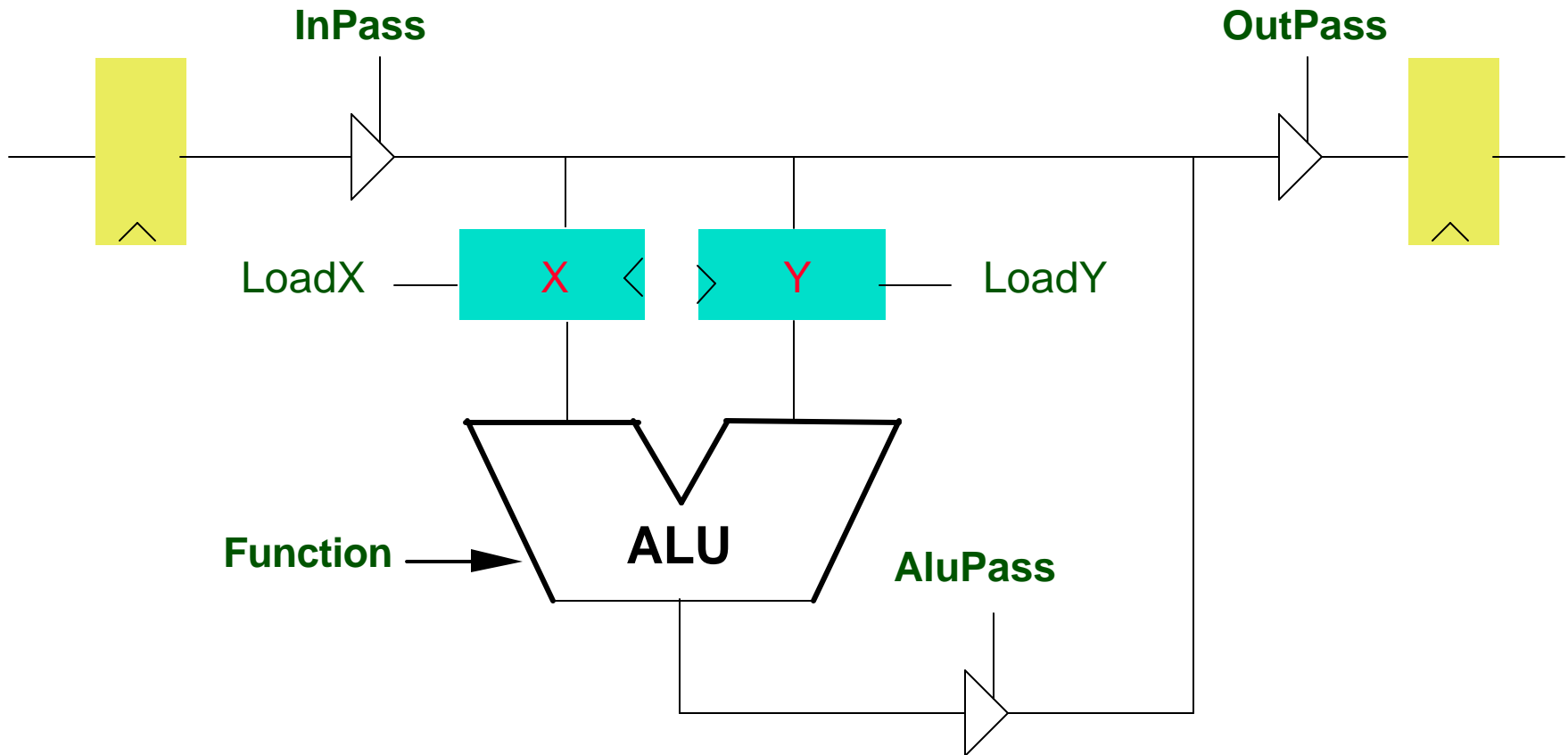
# Datapath I/O

- A wire can be driven by only one tri-state at a time
  - If InPass is active, AluPass must be inactive
  - If AluPass is active, InPass must be inactive




# Datapath I/O

## Two values enter from the left (A and B)

- Need to perform  $(A+B)+A$
- In  $\rightarrow$  X (Load A)
- In  $\rightarrow$  Y (Load B)
- $A+B \rightarrow Y$
- $(A+B)+A \rightarrow$  Out


Four steps and then repeat

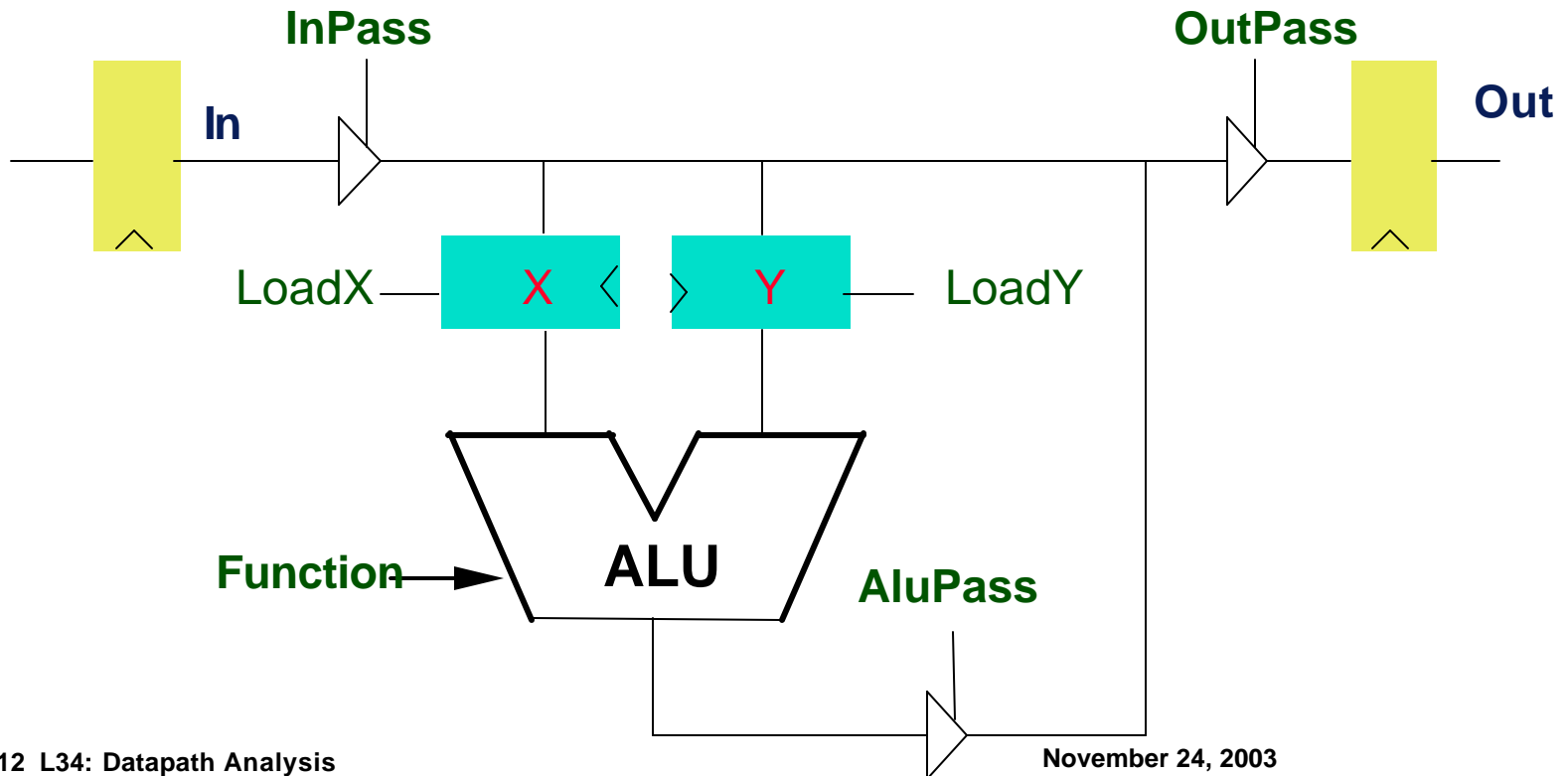

# Implementing the Control ROM
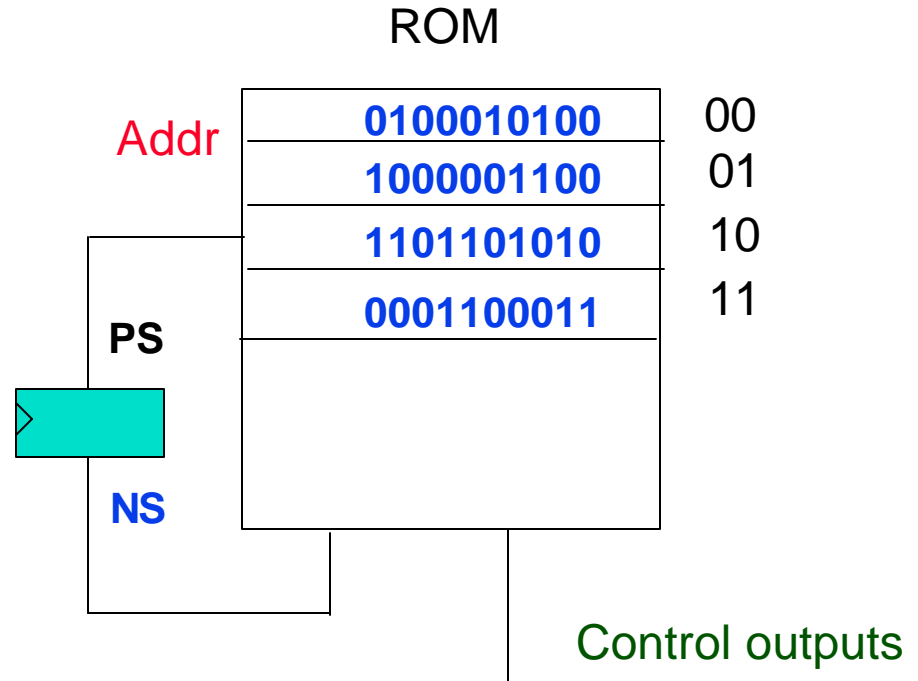
## Two values enter from the left (A and B)


- Need to perform  $(A+B)+A$
- In  $\rightarrow$  X (Load A) - State 00
- In  $\rightarrow$  Y (Load B) - State 01
- $A+B \rightarrow$  Y - State 10
- $(A+B)+A \rightarrow$  Out - State 11



PS	NS	Function	LoadX	LoadY	InPass	AluPass	OutPass
00	01	000	1	0	1	0	0
01	10	000	0	1	1	0	0
10	11	011	0	1	0	1	0
11	00	011	0	0	0	1	1
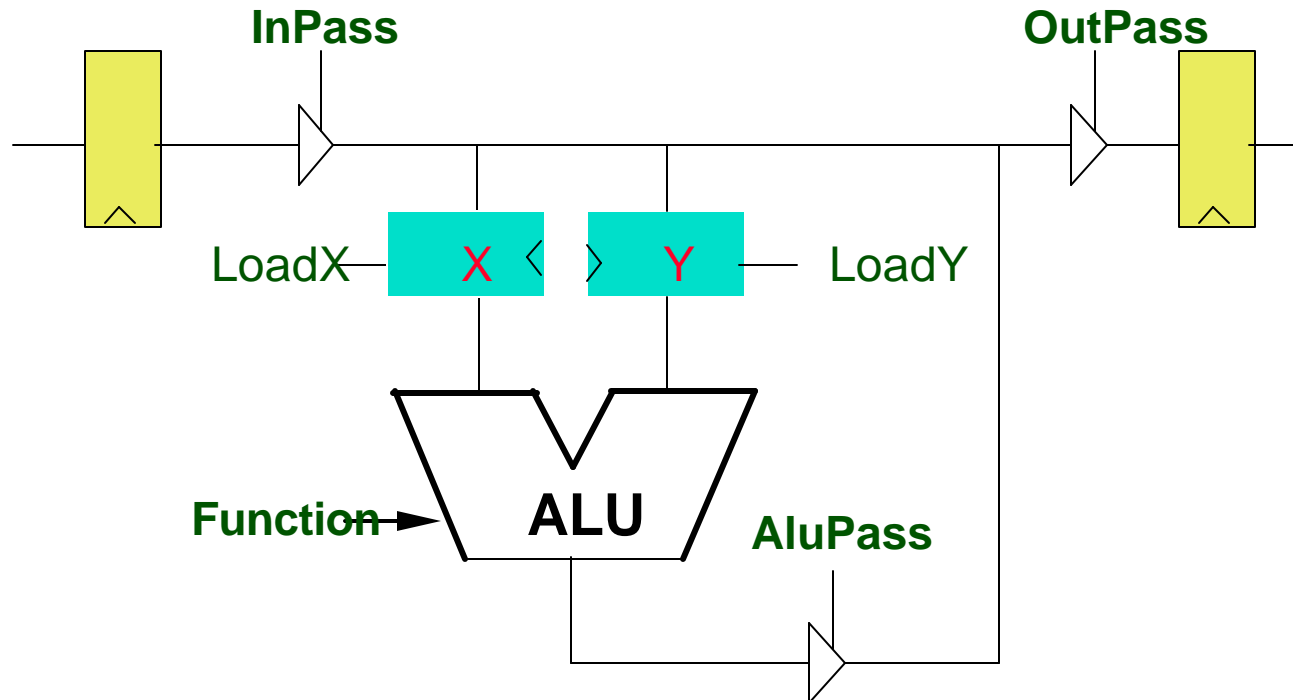
# More Complicated Example


- Can we compute  $(A+B) \cdot (A-B)$ ?
- Currently, no place for intermediate storage
- Solution: Add RAM to datapath.



# More Complicated Example

- Can we compute  $(A+B) \cdot (A-B)$ ?
  - Need to add intermediate storage.
- Typical sizes (1MB – 2GB)

Add RAM to the Datapath

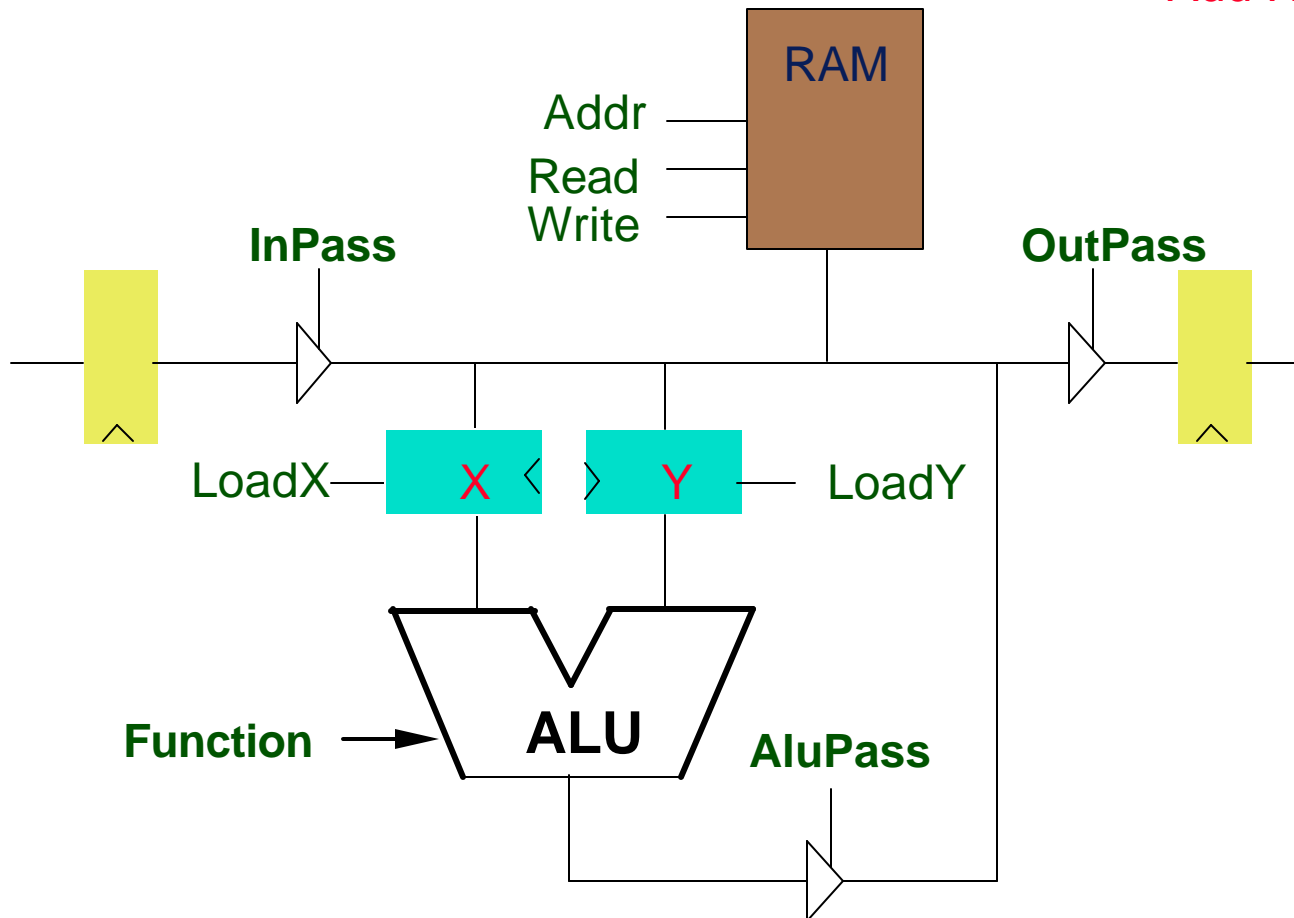

# Implementing the Control ROM


- **Two values enter from the left (A and B)**
  - Need to perform  $(A+B) \cdot (A-B)$
  - In  $\rightarrow$  X (Load A) - State 000
  - In  $\rightarrow$  Y (Load B) - State 001
  - $A+B \rightarrow$  RAM[4] - State 010
  - $A-B \rightarrow$  X - State 011
  - RAM[4]  $\rightarrow$  Y - State 100
  - $(A+B) \cdot (A-B) \rightarrow$  Out - State 101

PS	NS	Function	LoadX	LoadY	InPass	AluPass	OutPass	Addr	Read	Write
000	001	000	1	0	1	0	0	000	0	0
001	010	000	0	1	1	0	0	000	0	0
010	011	011	0	0	0	1	0	100	0	1
011	100	010	1	0	0	1	0	000	0	0
100	101	000	0	1	0	0	0	100	1	0
101	000	110	0	0	0	1	1	000	0	0



# Does the Value of the Data Matter?

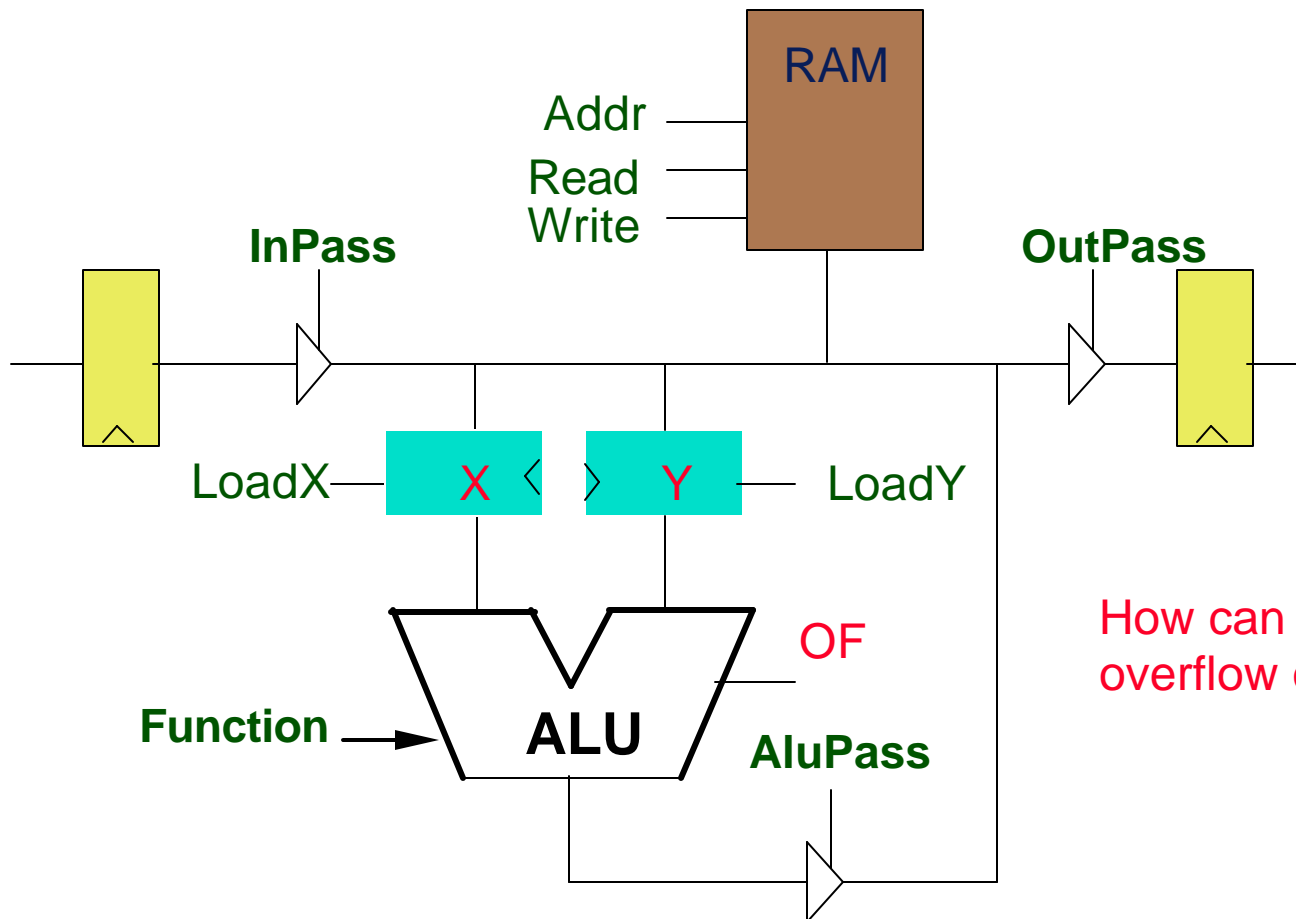- **Problem: Add A to itself until overflow occurs**
  - Amount of steps depends on A



How can we determine if overflow occurred?

# Implementing the Control ROM using Conditions

## One value enters from the left

Add A to itself until overflow occurs

- In  $\rightarrow$  X, Y (Load A, B) - State 0 - Next state 1
- X+Y  $\rightarrow$  Out, X - State 1 - Next state (1 if no overflow, 0 if overflow)

Include overflow (OF) bit as a ROM input

Note that it doubles the size of the ROM


PS	OF	NS	Function	LoadX	LoadY	InPass	AluPass	OutPass	Addr	Read	Write
0	0	1	000	1	1	1	0	0	000	0	0
0	1	1	000	1	1	1	0	0	000	0	0
1	0	1	011	1	0	0	1	1	000	0	0
1	1	0	011	1	0	0	1	1	000	0	0

Bits in the ROM

Each row indicates a ROM word
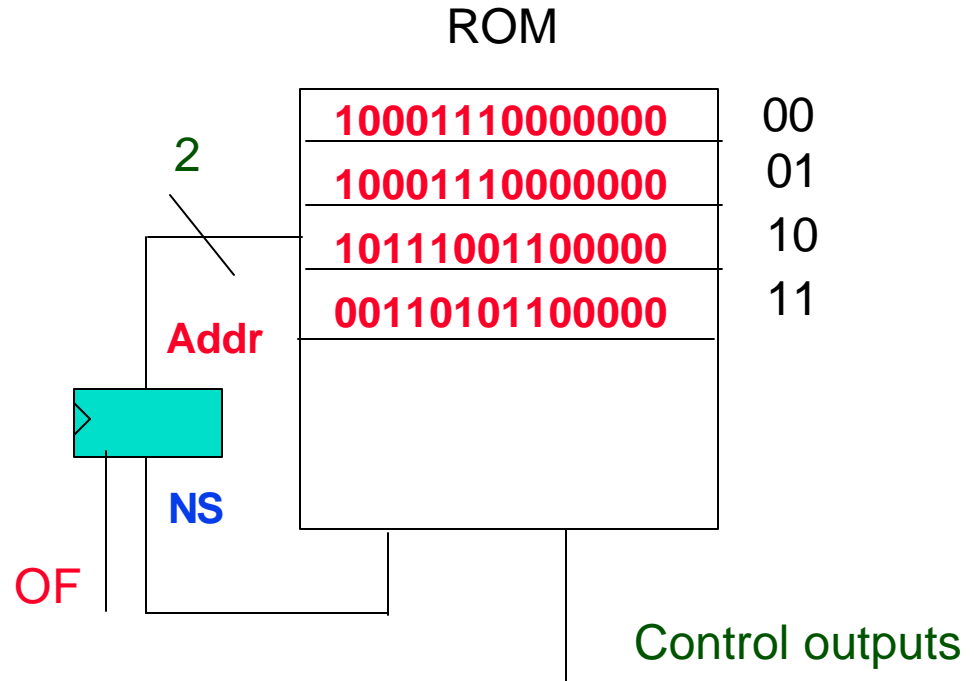
# Implementing the Control ROM with Conditionals


- Control path may have many inputs
  - Overflow, carry out, zero
- Used to perform conditional operations
- If statements and loops in programming languages



PS	OF	NS	Function	LoadX	LoadY	InPass	AluPass	OutPass	Addr	Read	Write
0	0	1	000	1	1	1	0	0	000	0	0
0	1	1	000	1	1	1	0	0	000	0	0
1	0	1	011	1	0	0	1	1	000	0	0
1	1	0	011	1	0	0	1	1	000	0	0
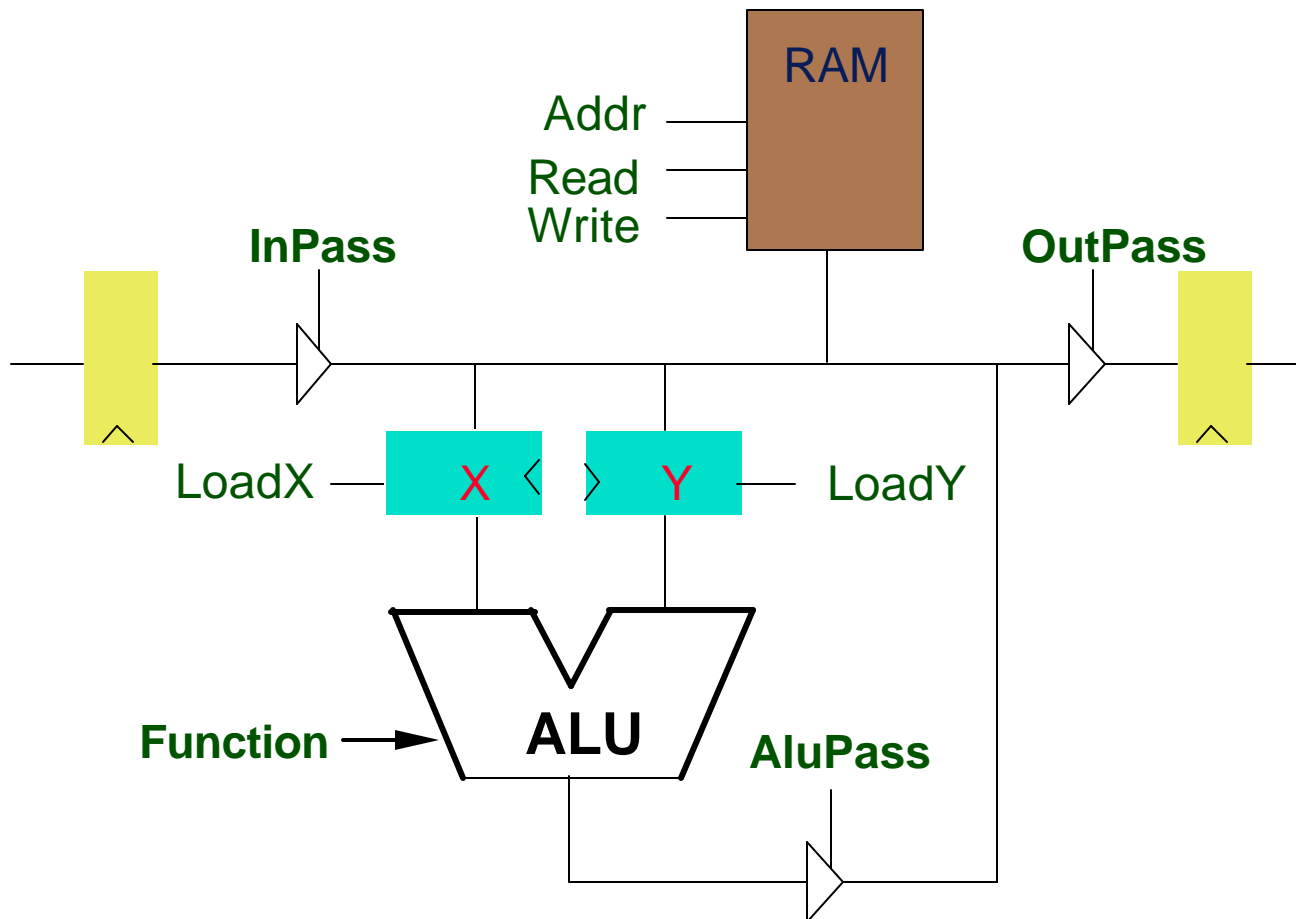
# One More Example

- Read two values from RAM (locations 0 and 1) and store to location 2.
  - Very common operation for microprocessor



# Implementing the Control ROM

---

- **Perform memory reads and writes**

- RAM[0] -> X                    - State 00
- RAM[1] -> Y                    - State 01
- X+Y -> RAM[2]                - State 10

No interaction with outside interfaces (In, Out) is required


Very similar to microprocessor operations

PS	NS	Function	LoadX	LoadY	InPass	AluPass	OutPass	Addr	Read	Write
00	01	000	1	0	0	0	0	000	1	0
01	10	000	0	1	0	0	0	001	1	0
10	00	011	0	0	0	1	0	010	0	1


*This slide marks the end of required material for this lecture!*

# Processor Construction Kit

## Subproblem 1: DATA PATHS

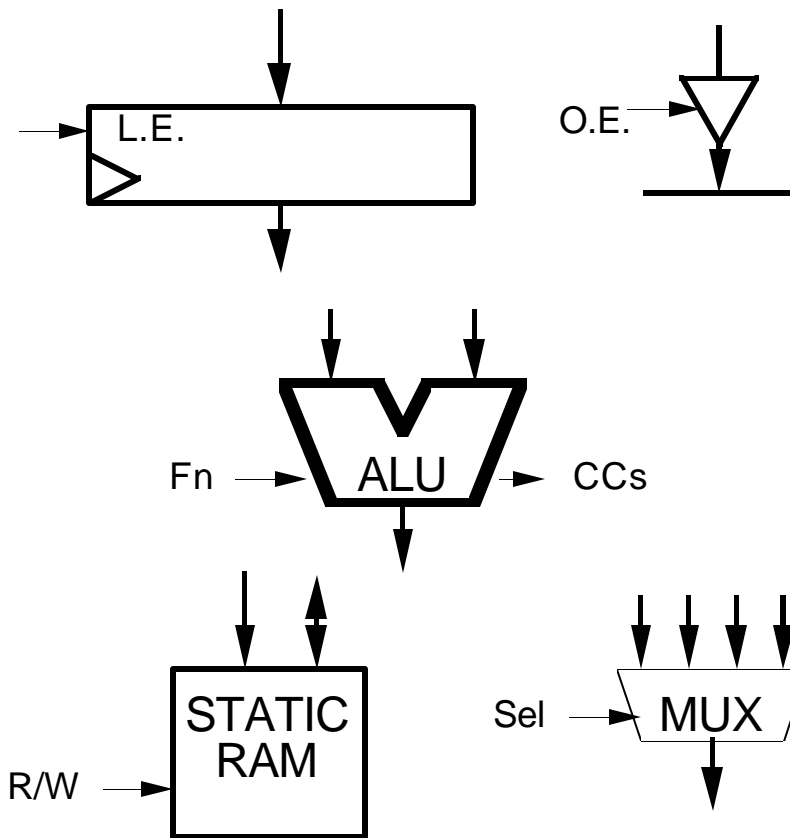

## Subproblem 2: CONTROL

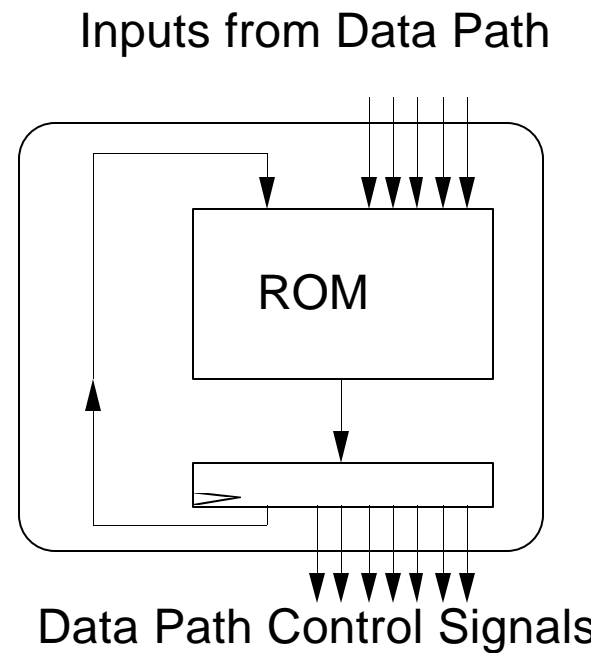

# Processor Compilation

---

- **Software engineer writes C program**
- **Compiler software converts C to assembly code**
- **Assembler converts assembly code to binary format**

## C program

```
main () {  
int A, B, C;  
  
C = A + B;  
}
```

**Compile**


---

## Assembly program

```
LD R1, A      ; load A to Reg R1  
LD R2, B      ; load B to Reg R2  
ADD R3, R1, R2 ; Add R1, R2 -> R3  
ST R3, C      ; Store result in C
```

A, B, and C are storage locations in  
main memory (DRAM)
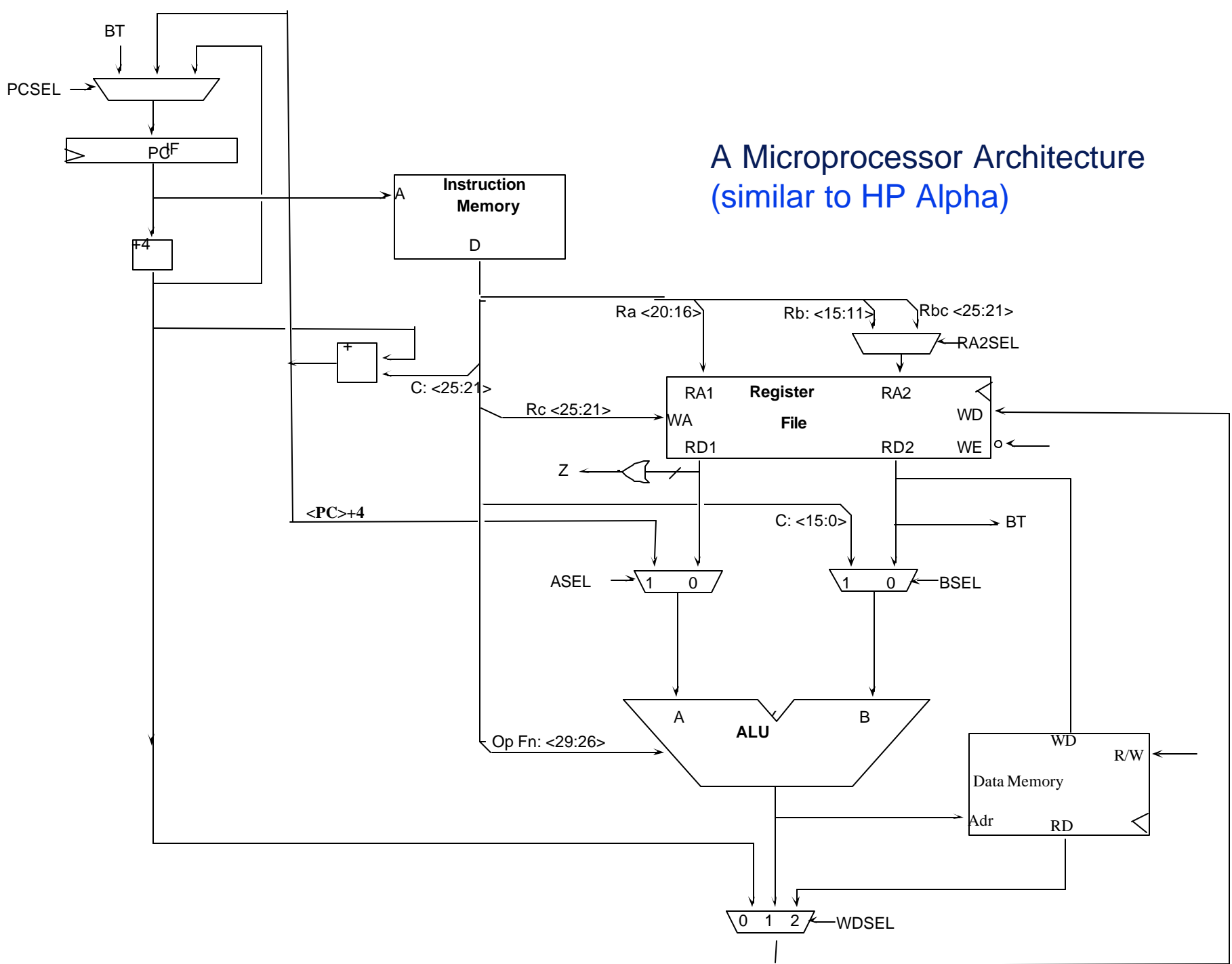
# A Microprocessor Architecture (similar to HP Alpha)





# Summary

---

- **Datapaths are important components of computer systems**
- **Interaction between control and data path determines execution time**
- **Each sequence of operations can be represented with a ROM program**
  - Each row in the state table corresponds to a word in the ROM
- **Multiple rows for each state if the ROM has a control input (e.g. ALU overflow)**
- **Next time: Notation to represent the data and control paths**