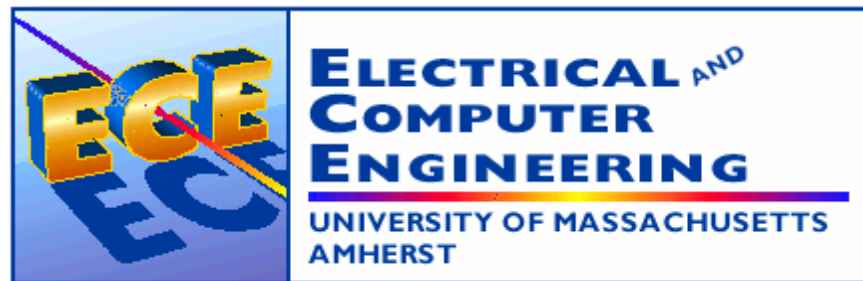

ENGIN 112

Intro to Electrical and Computer Engineering

Lecture 37

Register Transfer Level




Overview

- **System design must be modular**
 - Easier to represent designs with system-level blocks
- **Register transfer level represents transfers between clocked system registers**
 - Shifts, arithmetic, logic, etc.
- **Algorithmic state machine**
 - Alternate approach to representing state machines
- **Status signals from datapath used for control path**
- **Algorithmic state machine chart shows flow of computation**


System-level Design

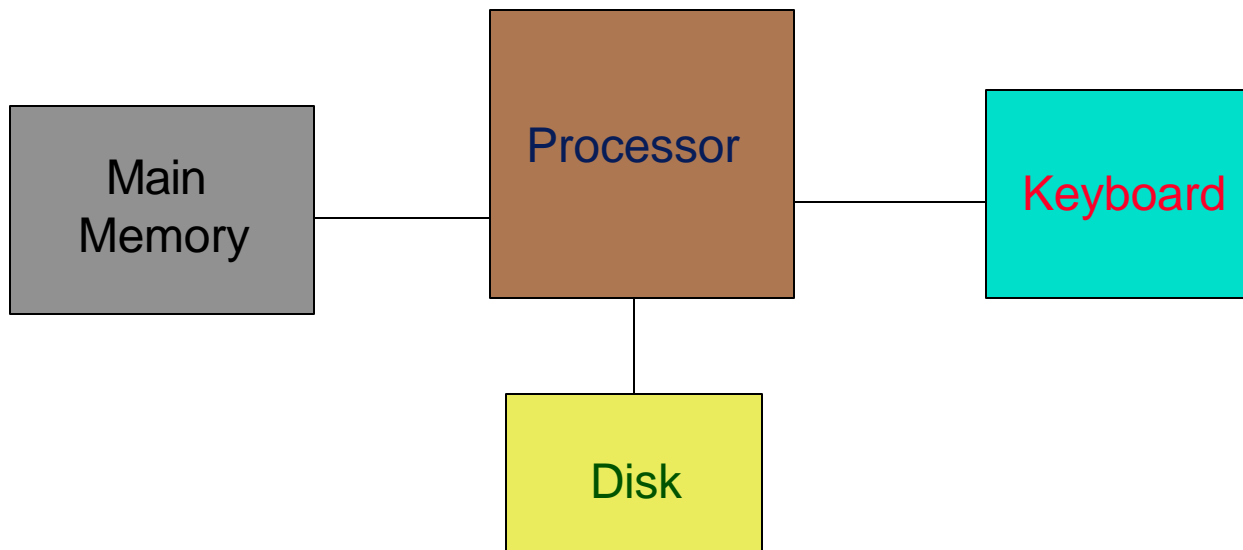- **Difficult to represent a design with just one state machine**
- **A series of control and data paths used to build computer systems**
- **Helps simplify design and allow for design changes**



Registers and Data Operations

 - **Activity and performance in computers defined on register-to-register paths**
- **Digital system at register transfer level specified by three components**
 - The set of registers in the system
 - Operations to be performed on registers
 - Control that is applied to registers and sequence of operations



Representation of Register Transfer Flow

- **Arrow indicates transfer from one register to another**
 - $R2 \leftarrow R1$
- **Conditional statements can help in selection**
 - If $(T1 = 1)$ then $R2 \leftarrow R1$
- **Clock signal is not generally included in register transfer level statement**
 - Sequential behavior is implied
- **Multiple choices also possible**
 - If $(T1 = 1)$ then $(R2 \leftarrow R1, R2 \leftarrow R2)$

How could these statements be implemented in hardware?

Other representative RTL operations

- **Addition**
 - $R1 \leftarrow R1 + R2$
- **Increment**
 - $R3 \leftarrow R3 + 1$
- **Shift right**
 - $R4 \leftarrow R4$
- **Clear**
 - $R5 \leftarrow 0$
- **Transfer doesn't change value of data begin moved**

How could these statements be implemented in hardware?

Algorithmic State Machines (ASM)

- Flowchart specifies a sequence of procedural steps and decision steps for a state machine
- Translates word description into a series of operations with conditions for execution
- Allows for detailed description of control and datapath

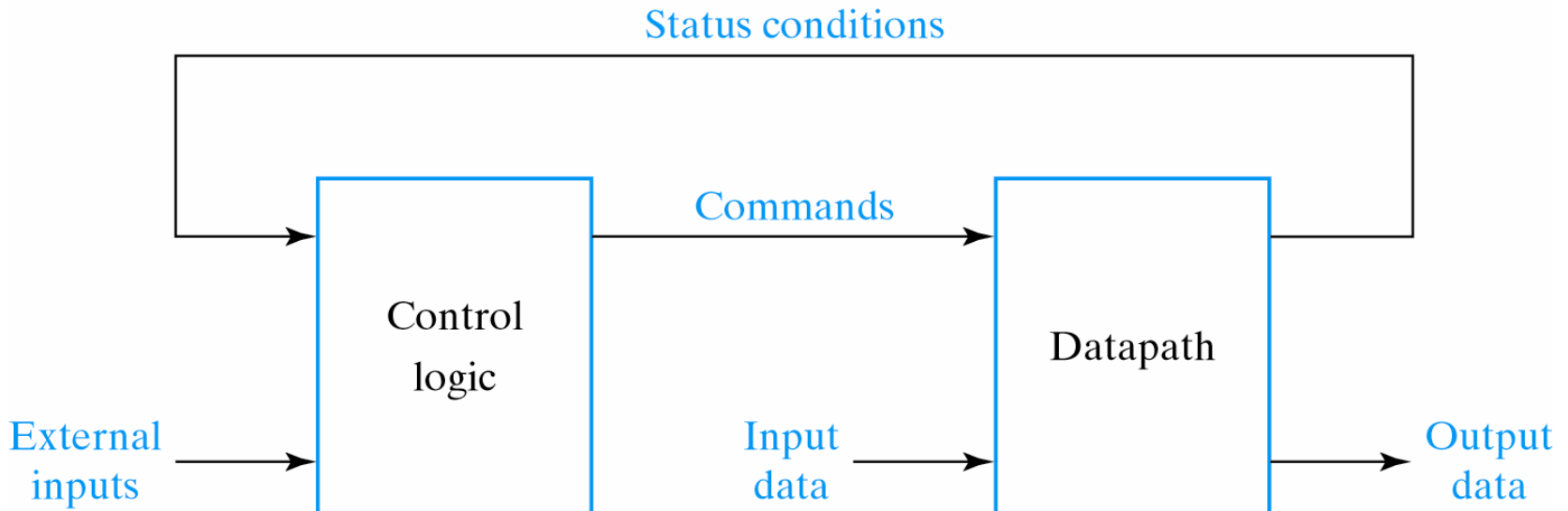


Fig. 8-2 Control and Datapath Interaction

Algorithmic State Machines – State Box

- **ASM describes operation of a sequential circuit**
- **ASM contains three basic elements**
 - **State box**
 - **Decision box**
 - **Condition box**
- **State box indicates an FSM state**
 - **Box also indicates operation to be performed**
- **Binary code and state name also included**

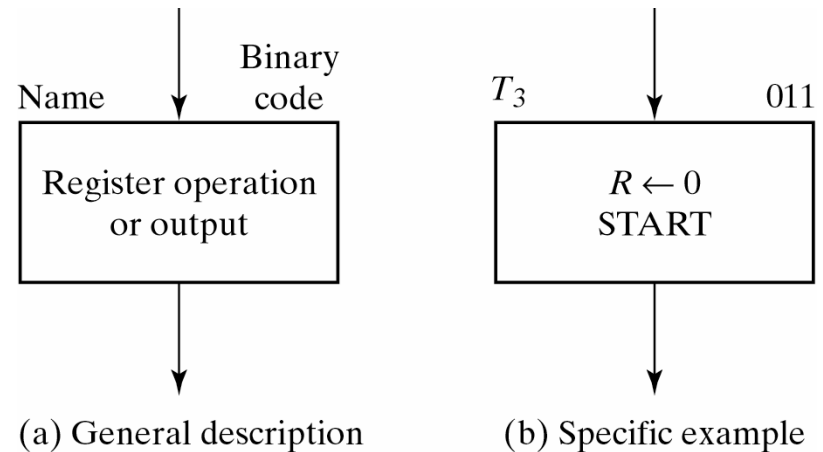


Fig. 8-3 State Box

Decision Box

- **Describes the impact of input on control system**
- **Contains two exit paths which indicate result of condition**
- **More complicated conditions possible**
- **Implemented in hardware with a magnitude comparator**

 


Fig. 8-4 Decision Box

Conditional Box

- Indicates assignments following a decision box
- Generally indicates data transfer

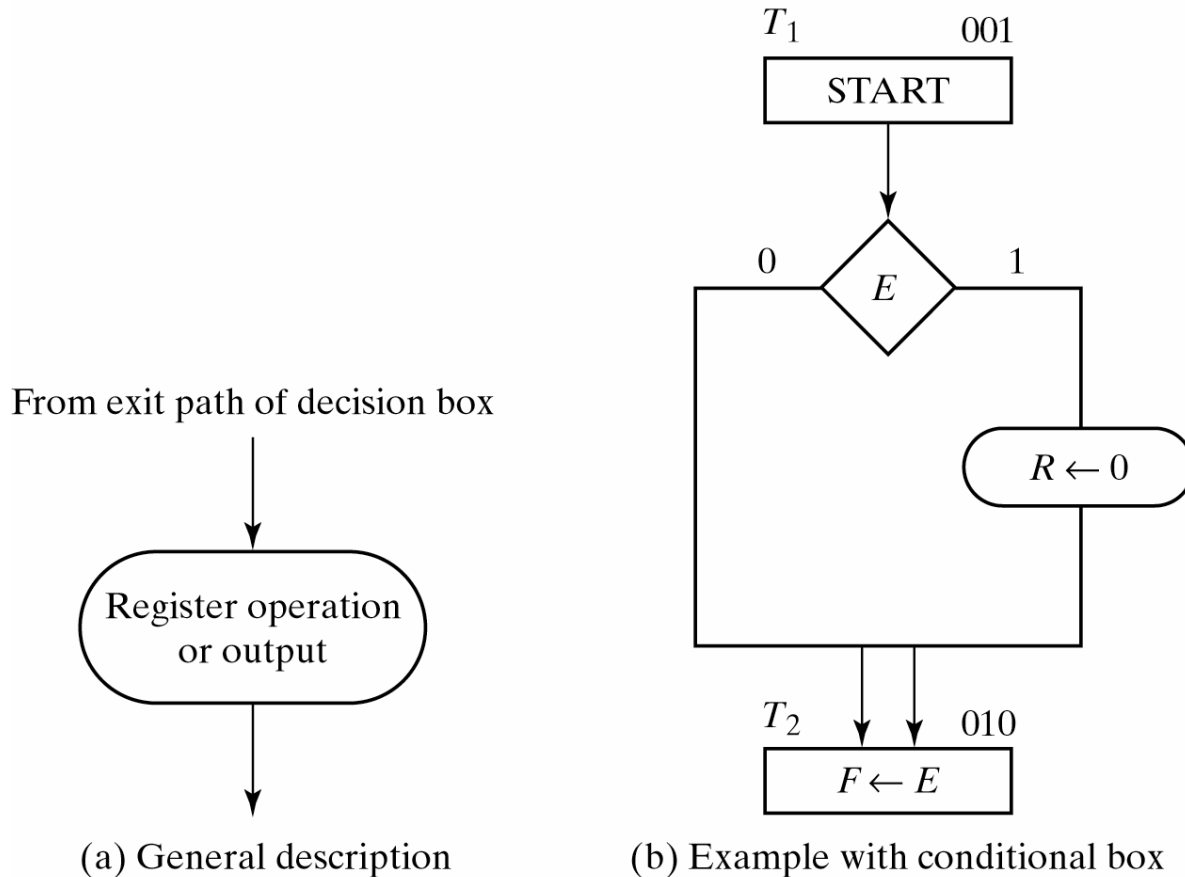


Fig. 8-5 Conditional Box

ASM Block

- Paths exist between state boxes
- Each state box equivalent to one state

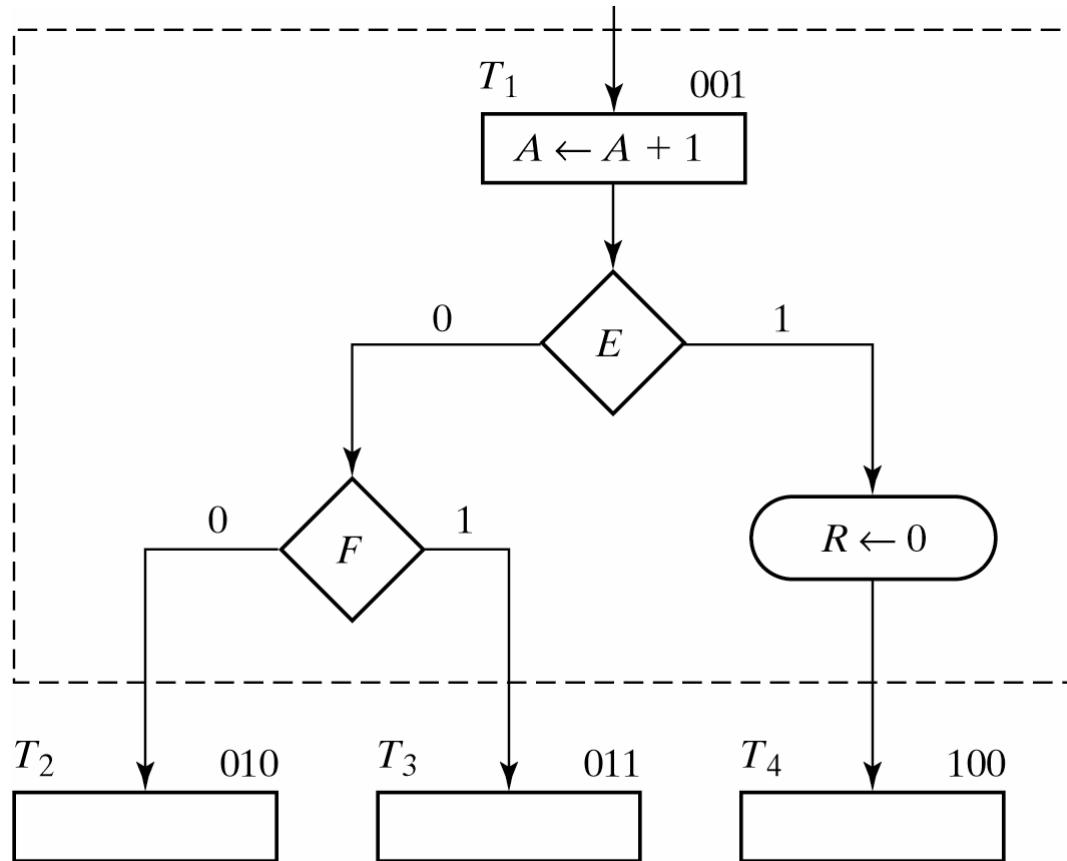


Fig. 8-6 ASM Block

ASM Block

◦ Equivalent to State Diagram

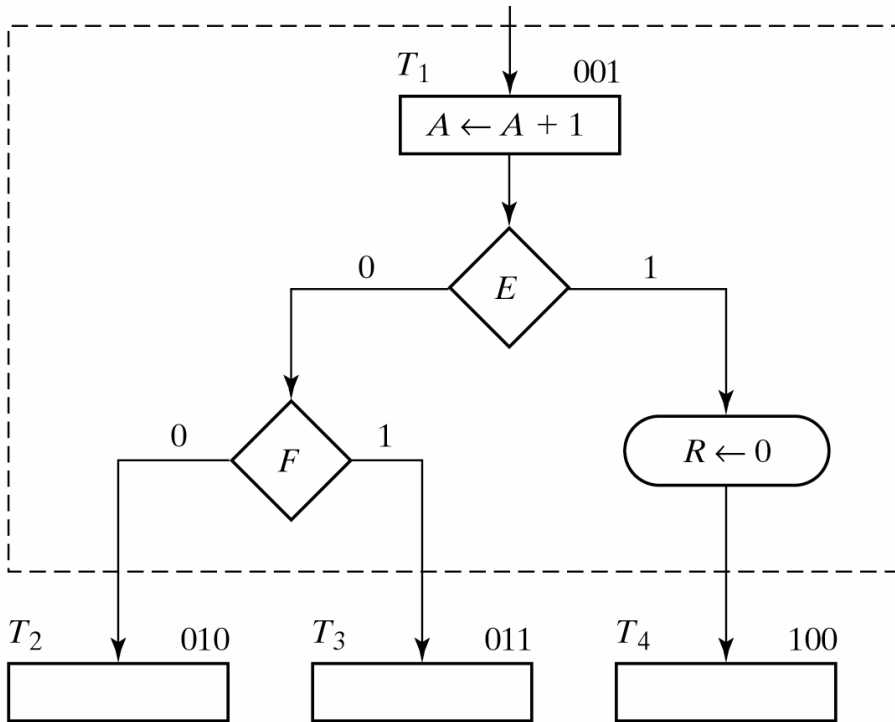


Fig. 8-6 ASM Block


 


Fig. 8-7 State Diagram Equivalent to the ASM Chart of Fig. 8-6

Concept of the State Machine

 Example: Odd Parity Checker

Assert output whenever input bit stream has odd # of 1's



State
Diagram

Present State	Input	Next State	Output
Even	0	Even	0
Even	1	Odd	0
Odd	0	Odd	1
Odd	1	Even	1

Symbolic State Transition Table

Present State	Input	Next State	Output
0	0	0	0
0	1	1	0
1	0	1	1
1	1	0	1


Encoded State Transition Table

- Note: Present state and output are the same value
- Moore machine


ASM for Odd Parity Checker

 Example: Odd Parity Checker

Assert output whenever input bit stream has odd # of 1's



State Diagram

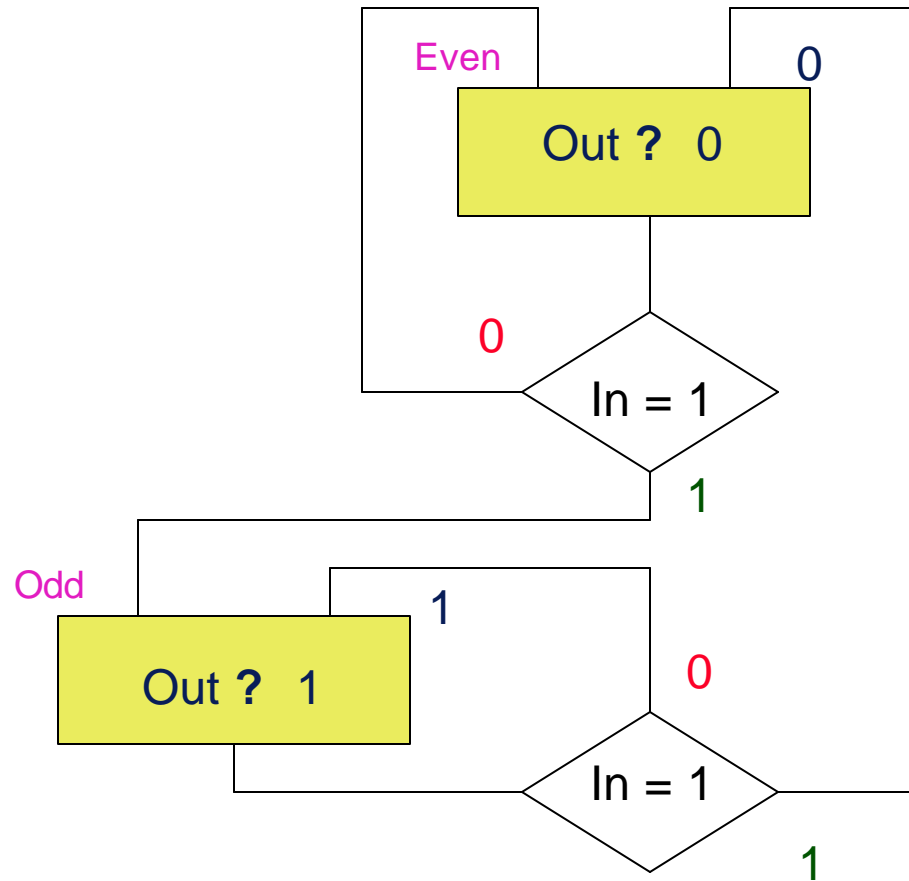

Verilog Representation for RTL

- **Conditional assignment statements**
 - **assign** $Y = S ? I1 : I0;$
- **Statement evaluation**

always @ (I1 or I2 or S)

if (S) Y = I1;

else Y = I0;

Perform evaluation only when an input changes


always @(posedge clk)

q = d;

Verilog description of a flip flop

Typical Design Flow

- It all starts with Verilog description

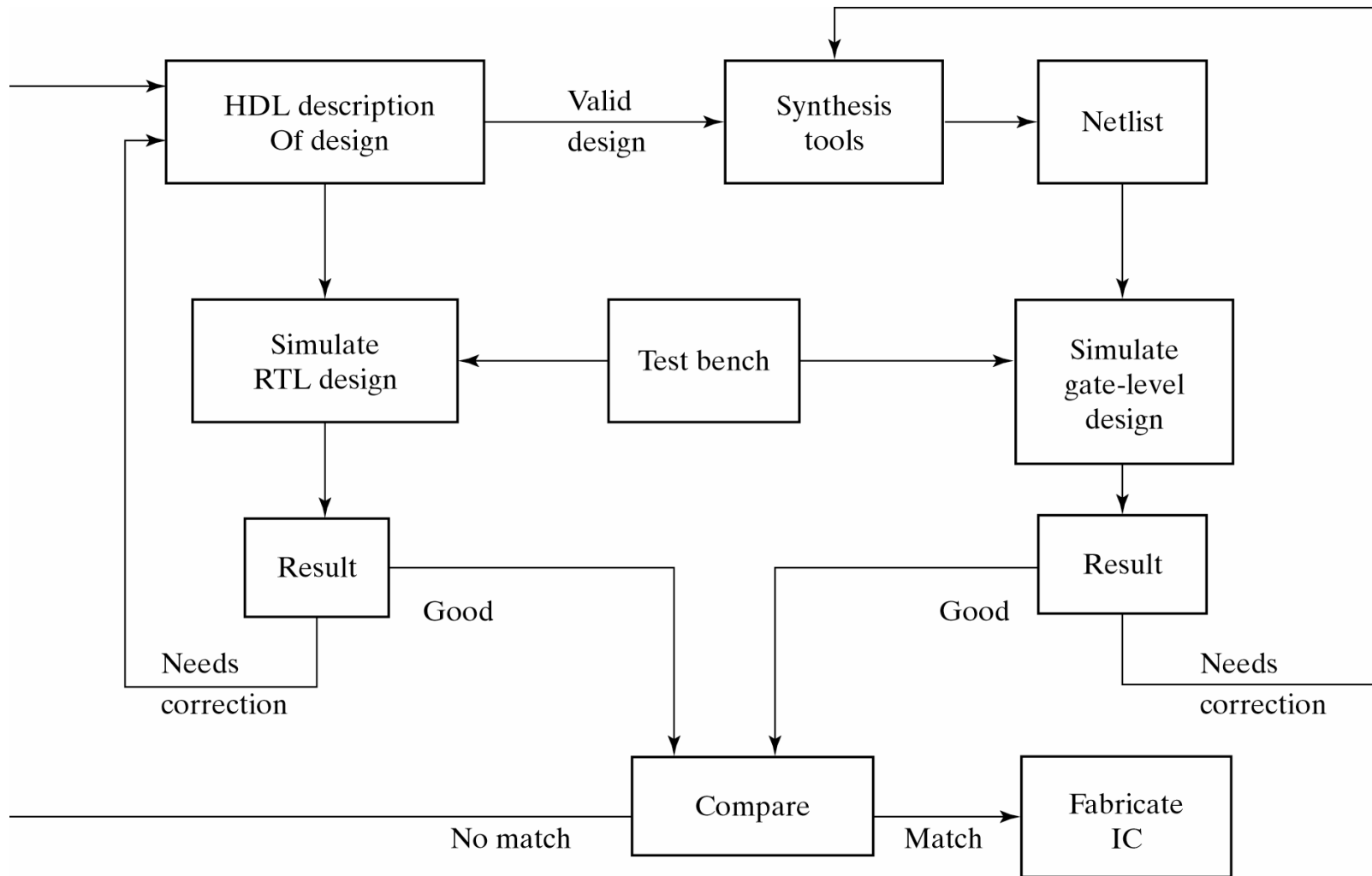

Summary

- **Register transfer level provides a simple way to describe designs**
- **A series of operations take place between registers**
- **Algorithmic state machine another way to represent a state machine**
- **Direct correspondence between state diagram and algorithmic state machine**
- **Possible to implement state machines in Verilog**
 - **Also in VHDL**
- **Next time: programmable array logic**