

---

# **ECE 354 – Computer Systems Lab II**

Memory and Indirect Addressing

# Comments

---


- Lab report for lab 1
  - Schematics
    - Label pins used on all chips
    - Use standard chip names/numbers (DB25,SP-233) from the datasheet
    - Use standard symbols for LEDs, switches, voltages, ground
    - Label clock frequencies, voltage values (eg.  $V_{dd}=5V$ )
    - Straight lines for wires
    - Show orientation of chips
- Lab 2
  - Any problems?
  - Sign up for demo time slot
  - Include logic analyzer outputs in lab report

# Lab 3 Overview

---

- Connect SRAM to PIC
  - SRAM memory extends storage of system
- Set up virtual address space
  - Spans PIC and two SRAM chips
- Memory test routine
  - Checks if write/read to memory works
  - Test result shown on terminal
- User can specify:
  - Address range
  - Test pattern to be used
- Each test reads and writes eight test patterns (rotated each time) to memory

# Lab 3 System Outline

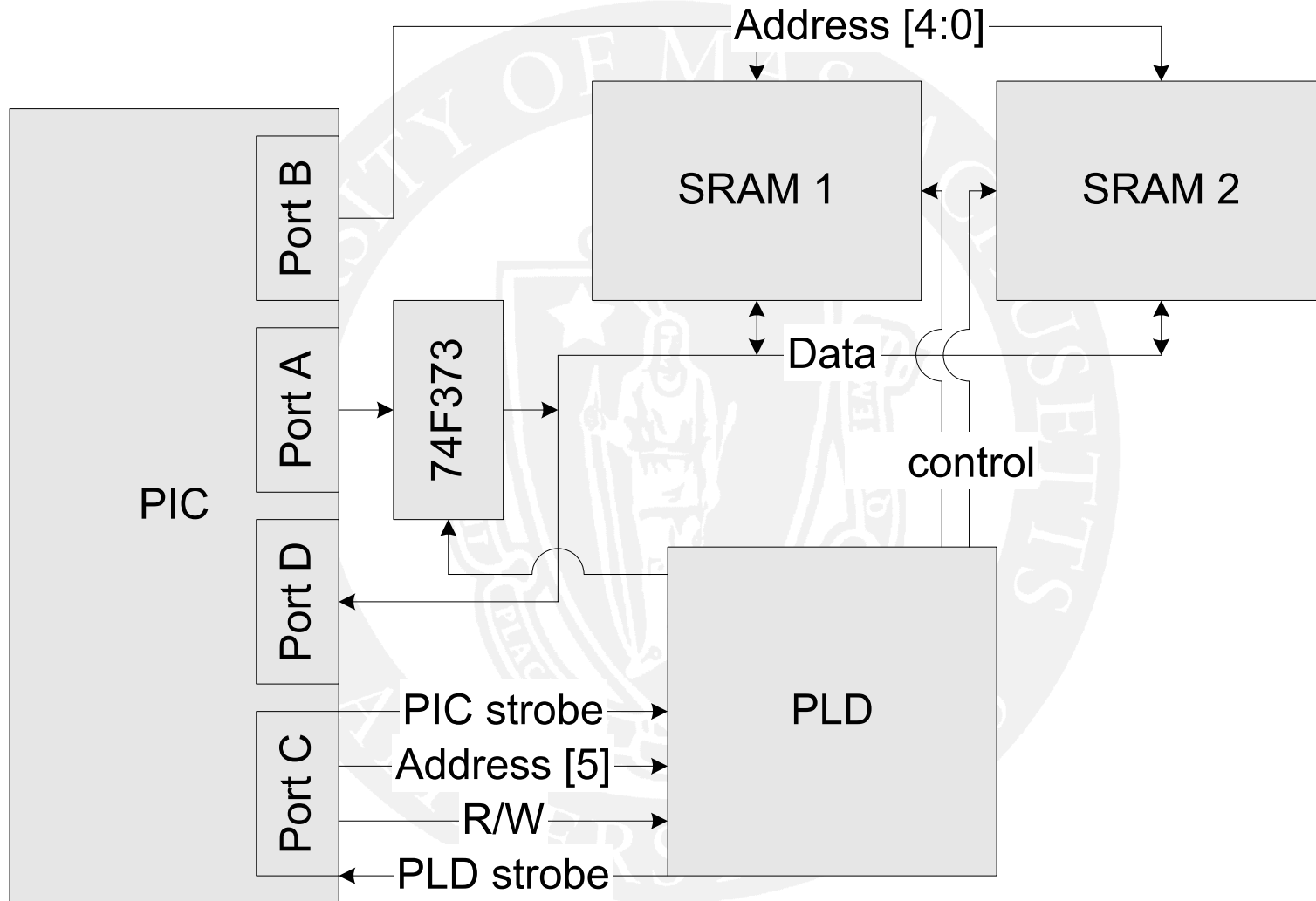


# Address Mapping

---

- Address space of Lab 3 spans three chips
  - Systems might require multiple memory chips (why?)
- Address space should be simple
  - Simpler to program
  - Independent of physical memory configuration
- “Memory Mapping”
  - Assignment of logical/virtual addresses to physical memory addresses
- Lab 3:
  - Three memories: 2 SRAM chips, internal PIC data memory
  - Address space: 128 bytes 0x00 to 0x7F

# Address Map Example

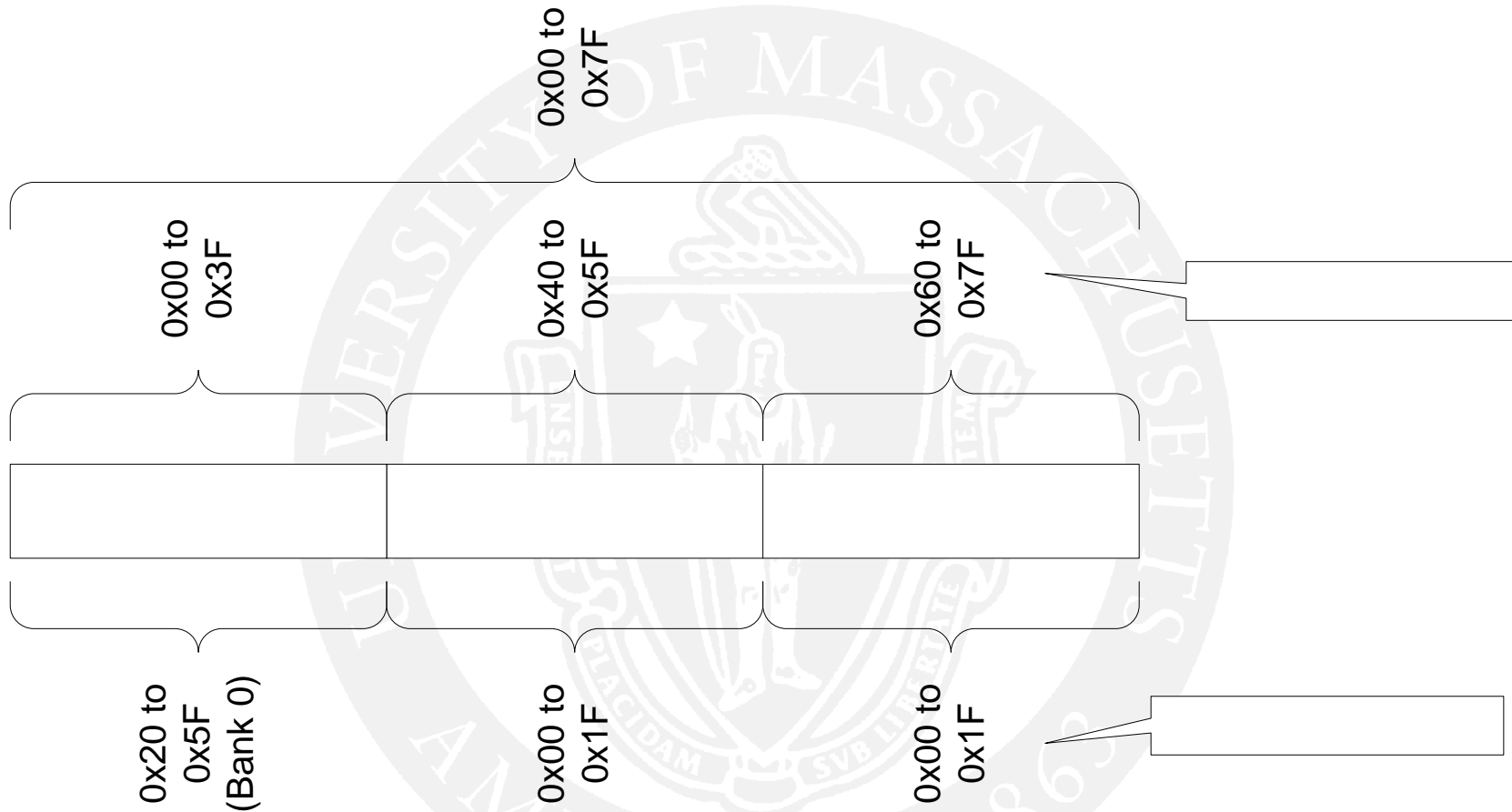

# Address Decoding

---

- Address decoding is process of determining to which device address is mapped
- Full address decoding
  - Look at every bit in the address
  - Requires more hardware
  - Possibly slower decoding
  - Can perform out-of-range checking
- Partial address decoding
  - Uses only some of the address bits to select device
  - Use some bits to select address within device
  - Cannot perform arbitrary range checking
  - Needs careful design
  - Uses fewer pins/gates
- What are we using in Lab 3?

# SRAM

- “Static Random Access Memory”
  - Memory does not need to be refreshed (unlike SDRAM)
- We are using HM6264B for Lab 3
  - 64kbit SRAM (8k x 8 bit)
  - Effectively only very small fraction of SRAM is used
- Important pins:
  - A0 to A12: address
  - I/O1 to I/O8: data input/output
  - CS1 and CS2: chip select 1 and 2
  - WE: write enable
  - OE: output enable

HM6264BLP/BLSP/BLFP Series

NC	□ 1	28	□ V <sub>CC</sub>
A12	□ 2	27	□ $\overline{WE}$
A7	□ 3	26	□ CS2
A6	□ 4	25	□ A8
A5	□ 5	24	□ A9
A4	□ 6	23	□ A11
A3	□ 7	22	□ $\overline{OE}$
A2	□ 8	21	□ A10
A1	□ 9	20	□ $\overline{CS1}$
A0	□ 10	19	□ I/O8
I/O1	□ 11	18	□ I/O7
I/O2	□ 12	17	□ I/O6
I/O3	□ 13	16	□ I/O5
V <sub>SS</sub>	□ 14	15	□ I/O4



# SRAM Functions


Function Table

$\overline{WE}$	$\overline{CS1}$	CS2	$\overline{OE}$	Mode	$V_{CC}$ current	I/O pin	Ref. cycle
x	H	x	x	Not selected (power down)	$I_{SB}, I_{SB1}$	High-Z	—
x	x	L	x	Not selected (power down)	$I_{SB}, I_{SB1}$	High-Z	—
H	L	H	H	Output disable	$I_{CC}$	High-Z	—
H	L	H	L	Read	$I_{CC}$	Dout	Read cycle (1)–(3)
L	L	H	H	Write	$I_{CC}$	Din	Write cycle (1)
L	L	H	L	Write	$I_{CC}$	Din	Write cycle (2)

Note: x: H or L

# SRAM Read (1)

- Assuming R/W\* is asserted:

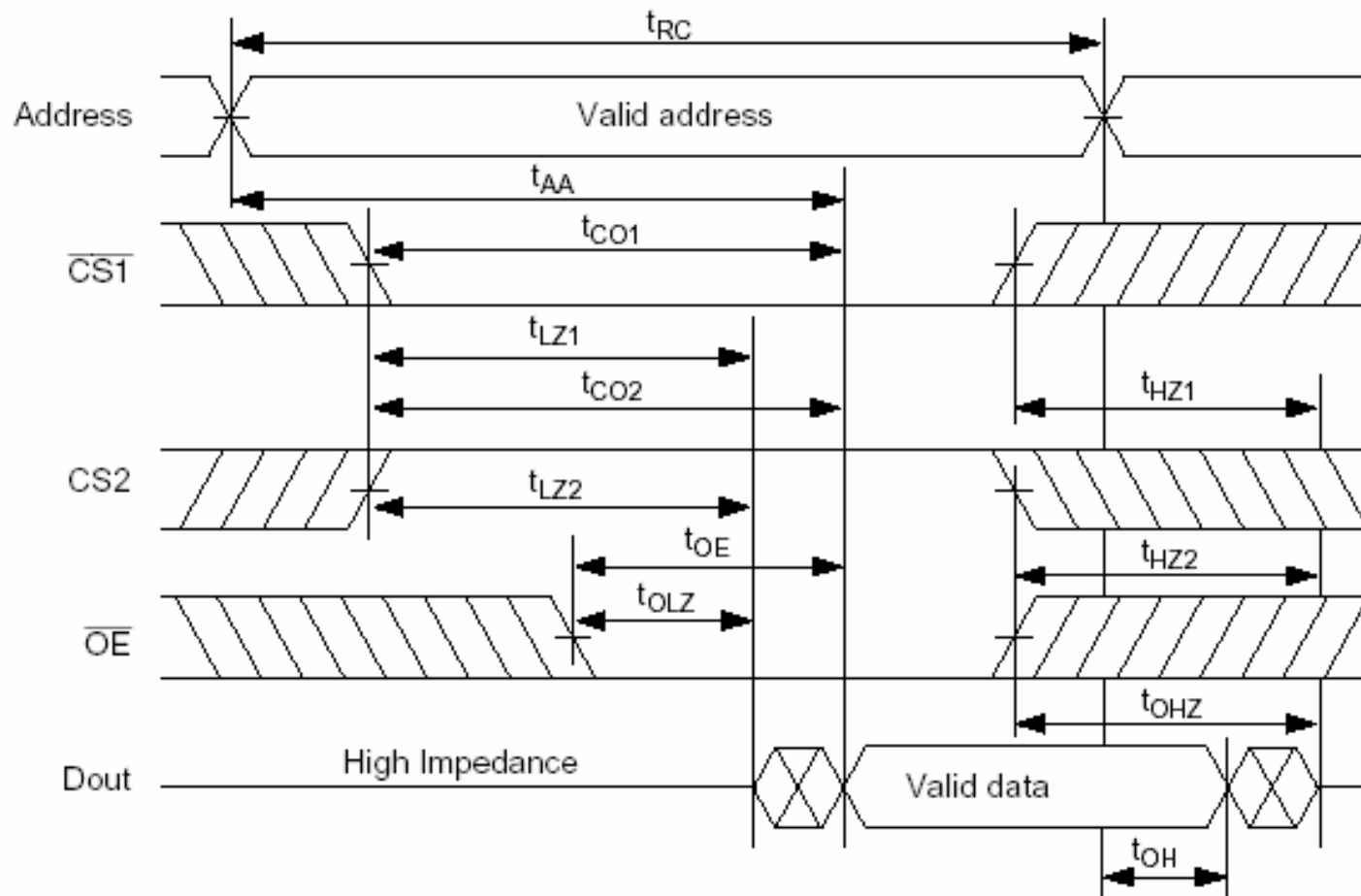


# SRAM Read (2)

---


1. WE\* asserted during transaction
2. Address asserted
3. CS\*, OE\* deasserted
4. Data available (transfer to PIC)
5. CS\*, OE\* asserted
6. Address deasserted
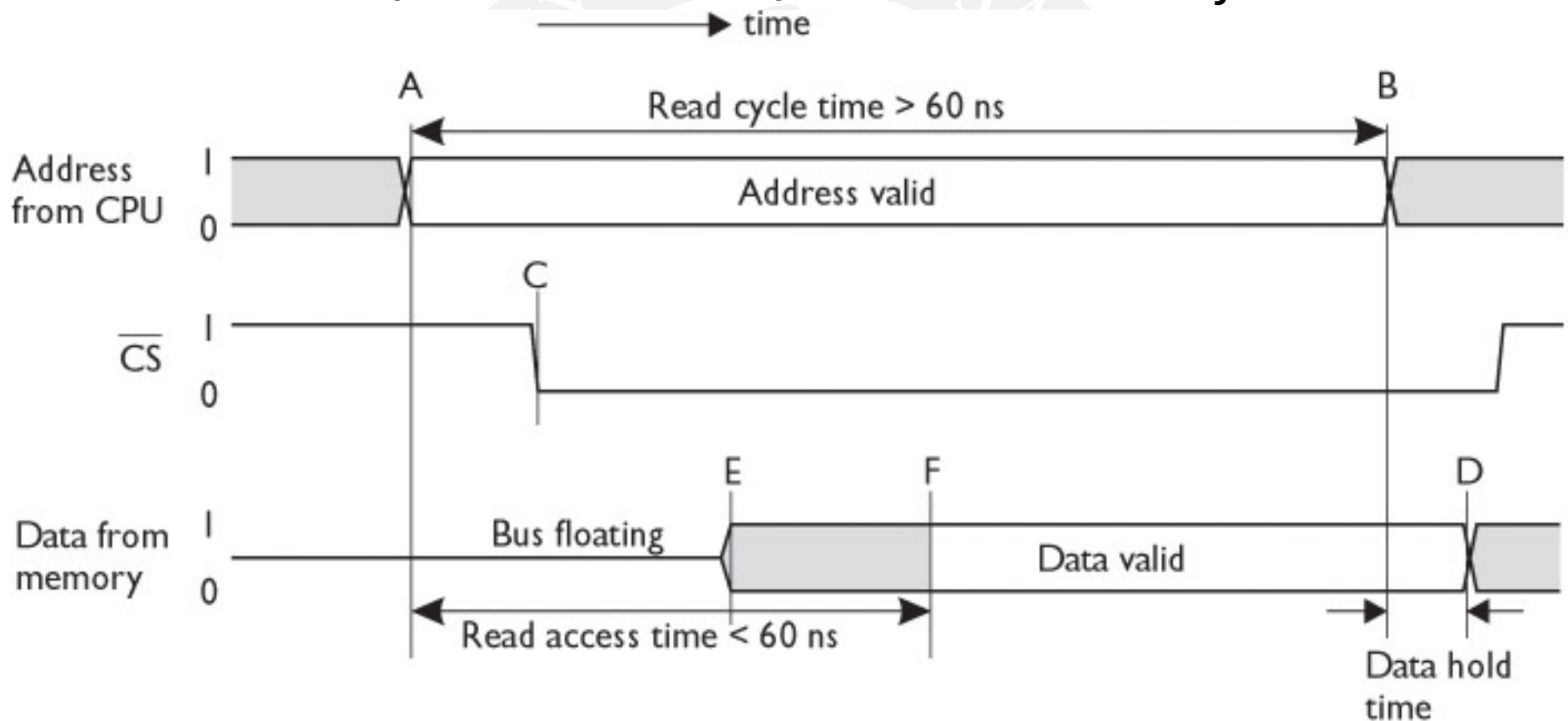
# SRAM Read (3)

- From Alan Clements: "The Principles of Computer Hardware," Third Edition, Oxford University Press



# SRAM Write (1)

 


# SRAM Write (2)

---

1. OE\* asserted during transaction
2. Address asserted
3. CS\* deasserted
4. WE\* deasserted
5. Data driven by PIC (anytime during 1-4)
6. CS\*, WE\* asserted
7. Data and address deasserted
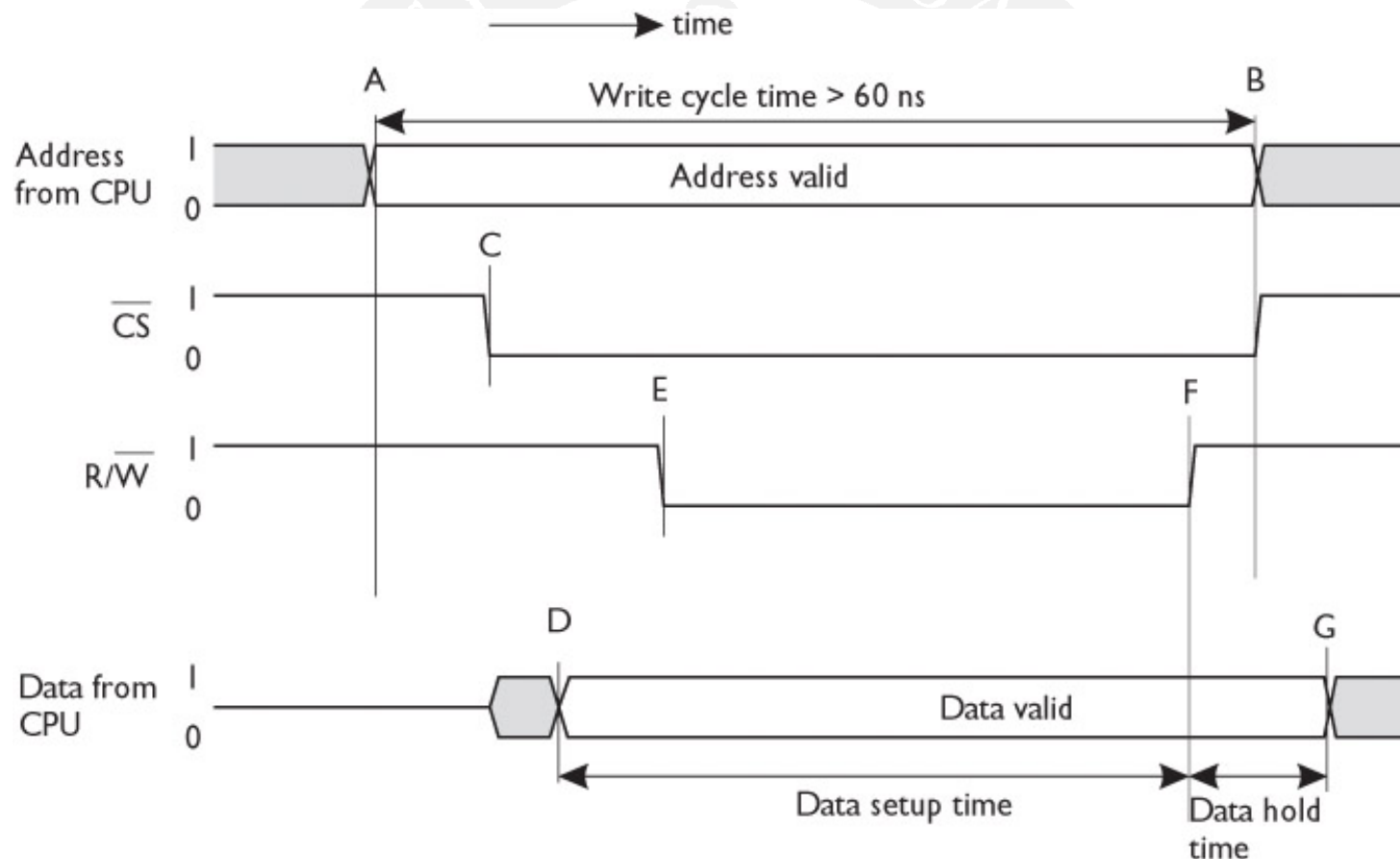
# SRAM Write (3)

- From Alan Clements: "The Principles of Computer Hardware," Third Edition, Oxford University Press



# SRAM Hints


---

- No harm in asserting address/data early
- Unused address pins
  - Drive to ground
- Unused data pins (only during test)
  - Tie to ground through 4.7k resistor
- With multiple SRAMs on one bus
  - only one OE should be enabled at any time
- I/O pins are bidirectional
  - Separate to two PIC ports
  - Isolate PIC output port with tri-state buffer (74F373 chip)
- SRAM is self-timed
- Do not confuse inverted control signals
- For details on memory interface, read Chapter 9 in Alan Clements: "The Principles of Computer Hardware," Third Edition, Oxford University Press (available online, link from course page)



 
# Putting It All Together


- SRAM is controlled by PLD
  - PLD implements control of OE\*, WE\*, CS\*
- PIC uses bus (Lab 2) to communicate with PLD
  - Data and address go directly from PIC to SRAM and back
- Address is split between PLD and SRAM



# Lab 3 Read

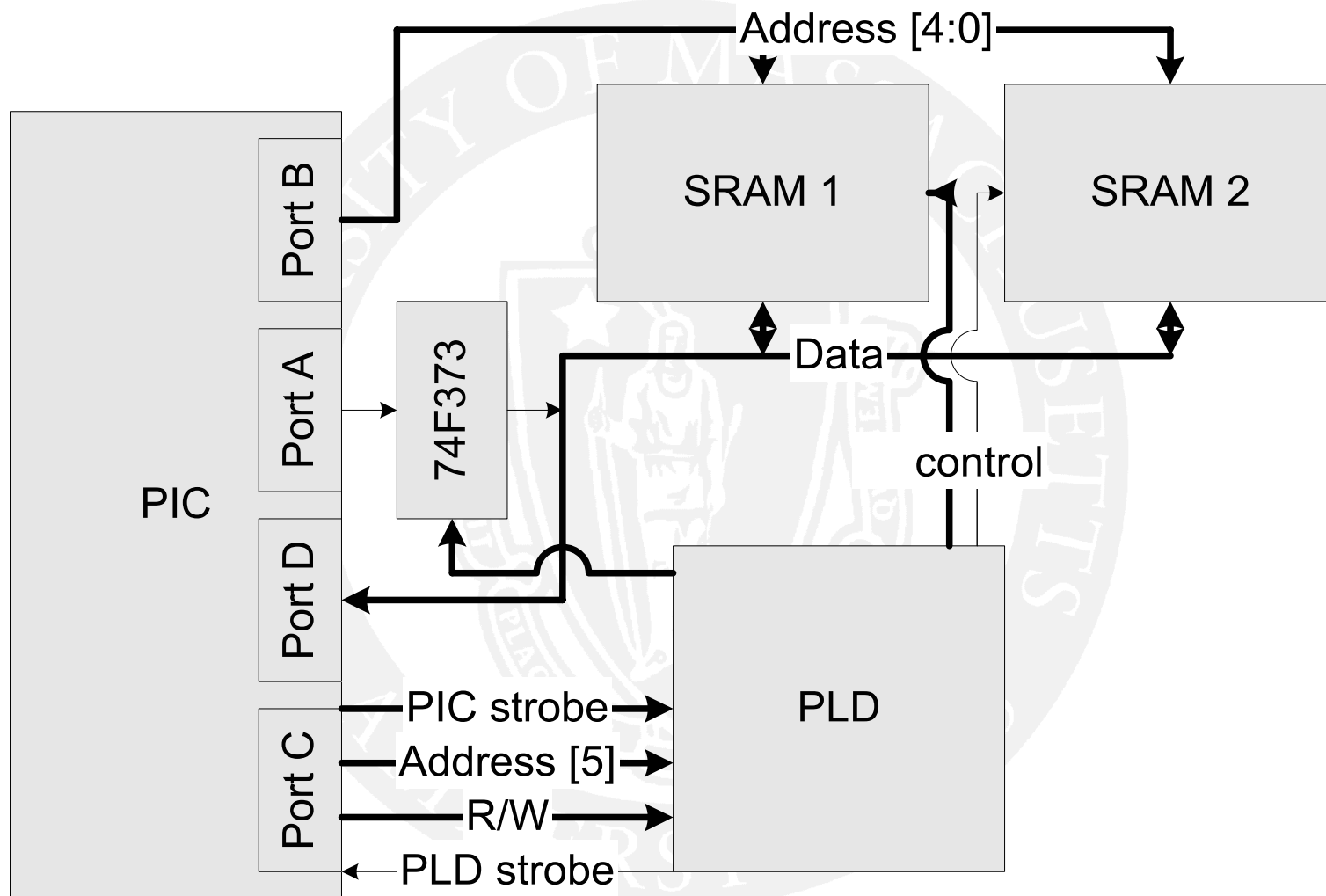


# Lab 3 Write

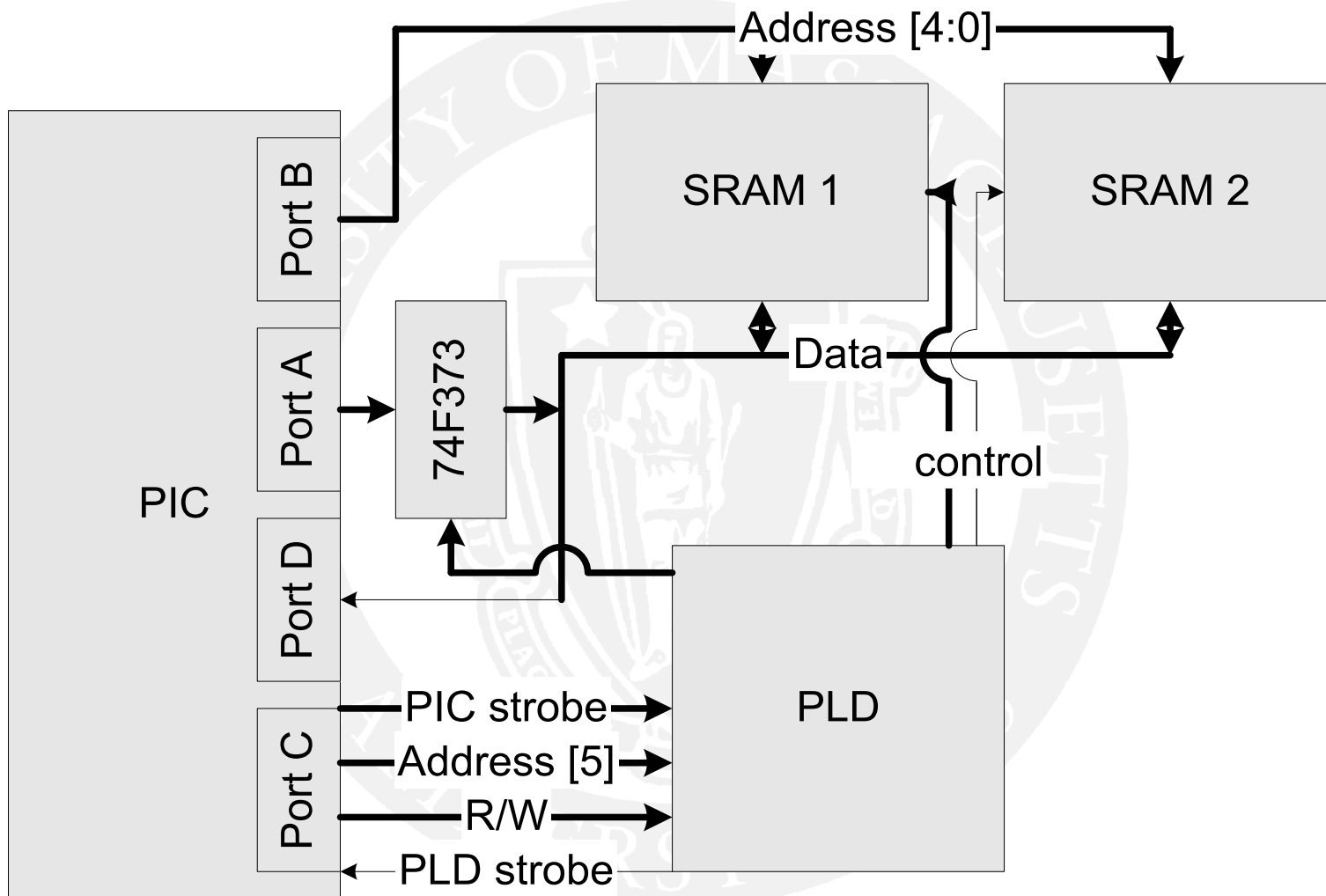
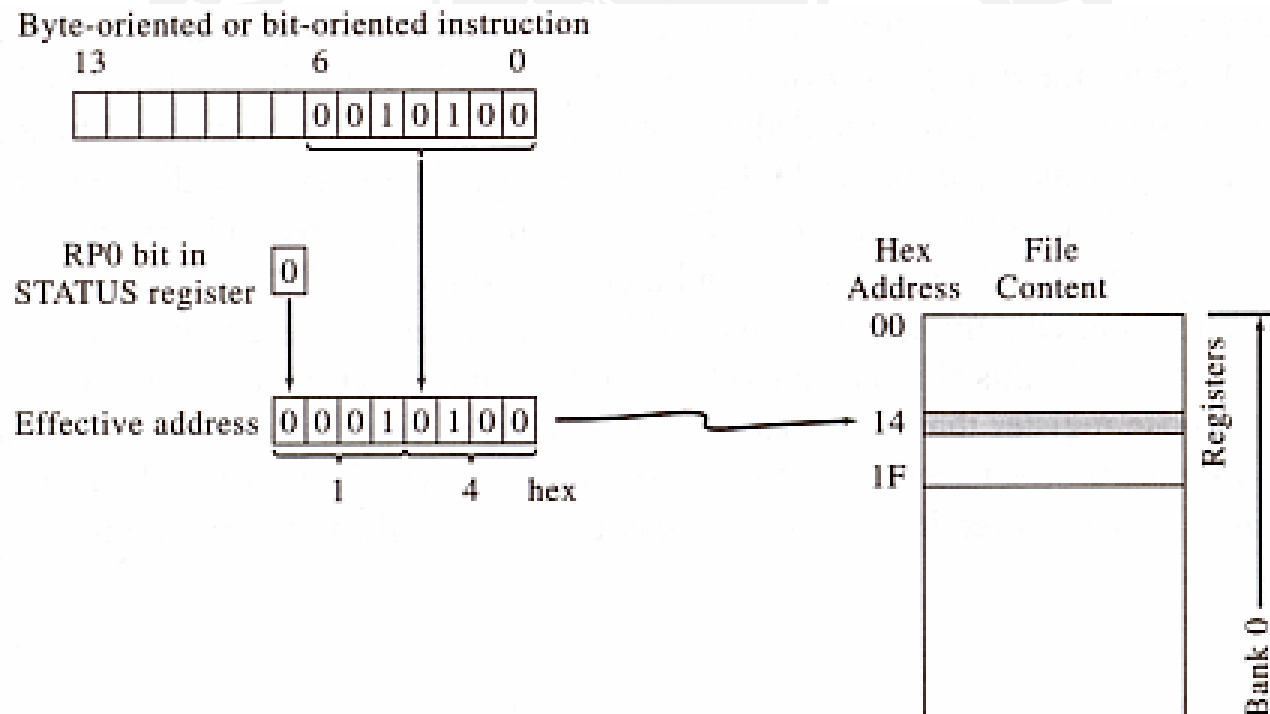
# Internal Memory Test

- Memory test needs to access range of addresses
- Problem: in programs addresses are fixed
  - Part of the instruction ("direct addressing")
  - Programmed into instruction memory



# Accessing Memory Range

- Example: write 0x42 to registers 0x20 to 0x7f

```
TEMP20 EQU 0x20
```

```
TEMP21 EQU 0x21
```

```
...
```

```
TEMP7F EQU 0x7F
```

```
main    movlw 0x42  
        movwf TEMP20  
        movwf TEMP21
```

```
...
```

```
        movwf TEMP7F
```

- Clumsy, wasteful – need better method!


# Indirect Addressing (1)

---


- Indirect Addressing:
  - Do not fix address in instruction
  - Use address given in another register
- PIC uses INDF and FSR registers
  - FSR contains address of register (8 bits)
  - IRP bit (STATUS<7>) selects bank 0/1 or bank 2/3 (1 bit)
  - Read or write to INDF register will automatically perform indirect access
 
# Indirect Addressing (2)


Byte-oriented or bit-oriented instruction



 address of INDF  
says to use FSR as a pointer



 Access to anywhere in  
entire file address space



# Accessing Memory Range

- Example: write 0x42 to registers 0x20 to 0x7f

```
    movlw 0x20    ; initialize first address
    movwf FSR    ; set indirection register
main  movlw 0x42  ; move test value to W register
      movwf INDF ; move value to indirect reg
      incf  FSR,F ; point to next data location
      ....      ; test if 0x80 reached
      btfss STATUS, Z ; if yes, then leave loop
      goto  main  ; restart loop
      ....      ; rest of code here
```



# Final Comments

---

- Start early – really!
  - Demos are on April 15<sup>th</sup> and 16<sup>th</sup>
  - Rob Vice’s lab hours will end after this week
- Use logic analyzer from the start
- Lab is difficult, because many components involved
  - Structure your breadboard layout
- Spend some time on your design
  - Don’t reuse Lab 2 bus blindly
- It’s the most difficult project – it’ll get easier after this